

# Recent SolidState PA Projects

Microwave Update 2011

Dave Robinson WW2R

## Topics

W6PQL 400W 1296MHz

Toshiba 100W 3400MHz


Spectrian 13cm Single

Spectrian 13cm Dual


IOJXX 500W 144MHz

## W6PQL 1296 AMP

## Previous 1296MHz PA

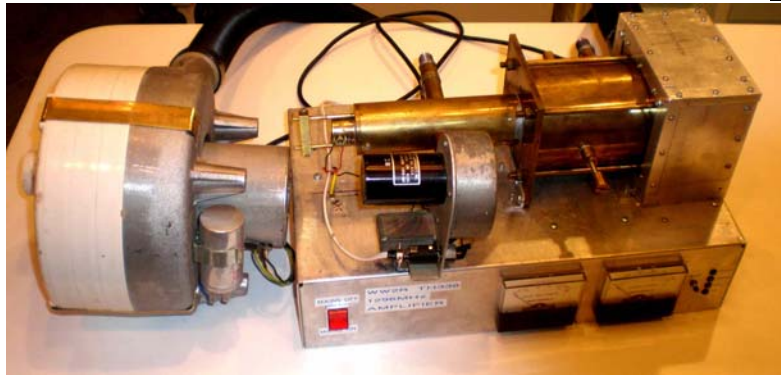

## W6PQL 400W 1296PA

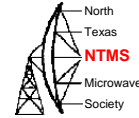

Was looking to replace TH338


Saw W6PQL board with 2 x MRF286 = 170W

No devices then saw EBAY listing from a local! Got some devices. Note they were genuine Motorola devices NOT Far east copies.



Got two kits, input and output combiner and copper heat spreaders from W6PQL

BIG heatsink from Ebay



## W6PQL 400W 1296PA

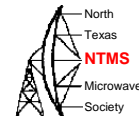

# W6PQL Circuit

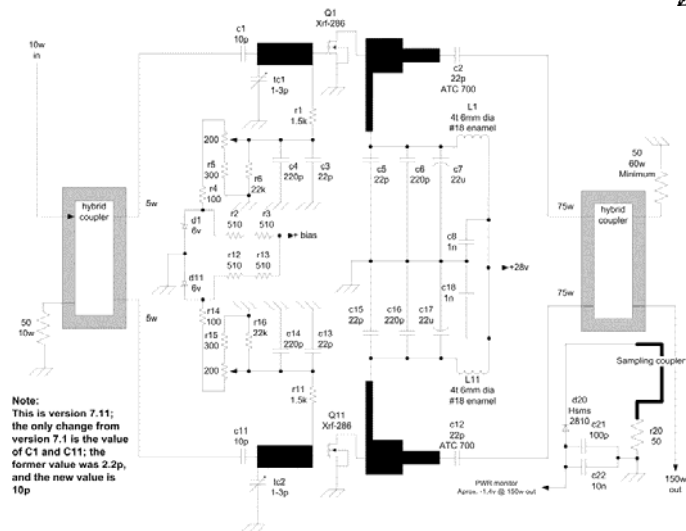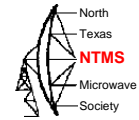


## W6PQL AMP Initial Test

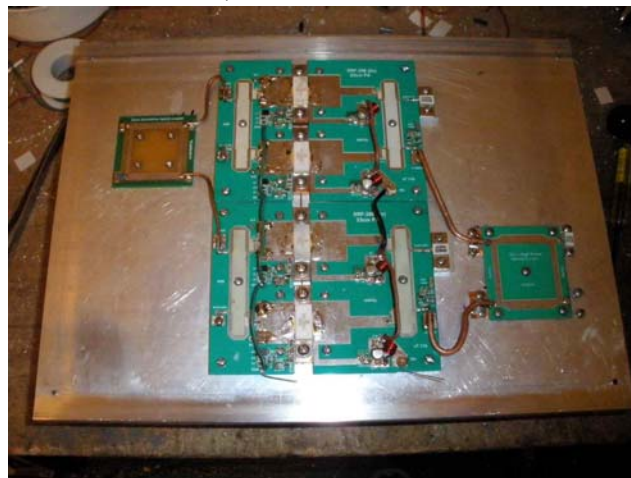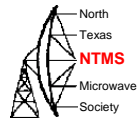

Worked well:-20W Input 350W output 28V

# W6PQL PA Controller needs

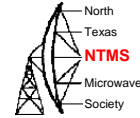

Status display

Fan control (enable fan at trigger temp, needs hysteresis)

SWR protection (error if rev power = 20W)



Monitor O/p of each module (error if either power=0 with drive)

Overcurrent protection (error if either module >18A)

Over Voltage (error if volts > 29V)

Need Microchip PIC with an LCD display

# W6PQL AMP Controller

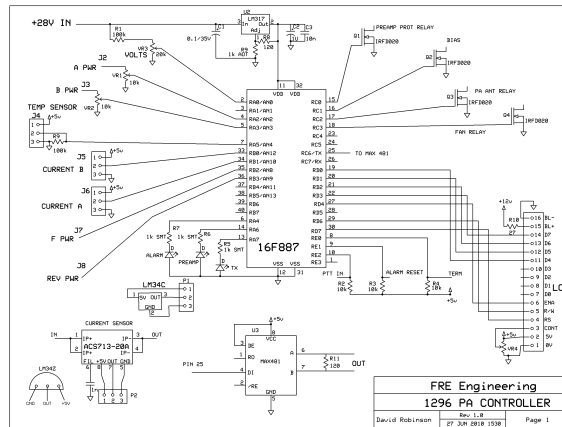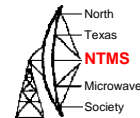


Note RS422 output for remote Display: put PA out at dish, monitor in shack! Use 50' premade keyboard extension cable (6 pin minidin to 6 pin minidin )


## W6PQL Amp Front



## W6PQL Amp Controller


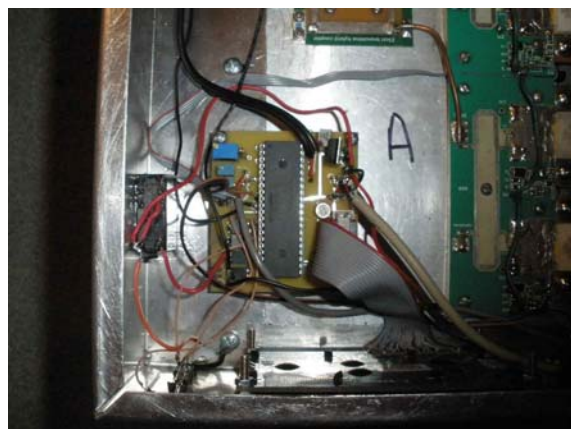


## W6PQL AMP Current monitor

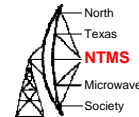

Allegro micro Hall  
effect ACS512

## W6PQL AMP Finished

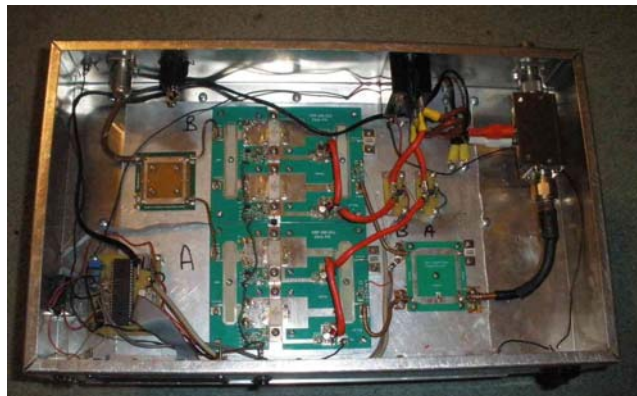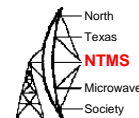


With Extra protection could now “tune it up”: 20W gives 400W  
Tried HB9BBD mods (7.20 board, MUD 2010) didn't help my 7.11  
board.





WSHN

## W6PQL Amp LCD

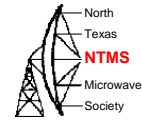

WSHN


## W6PQL Remote monitor

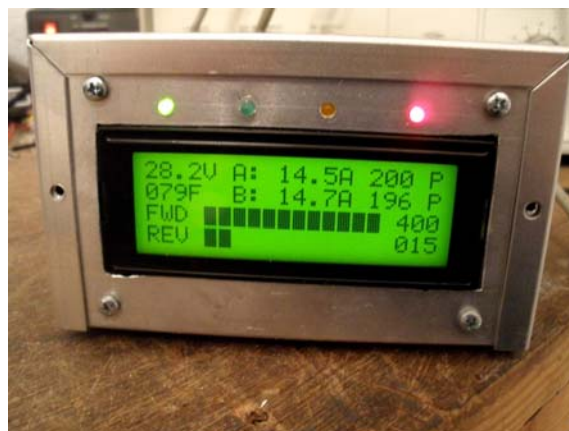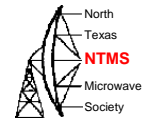

LCD in amplifier mounted out at dish disabled




## W6PQL Remote monitor Inners

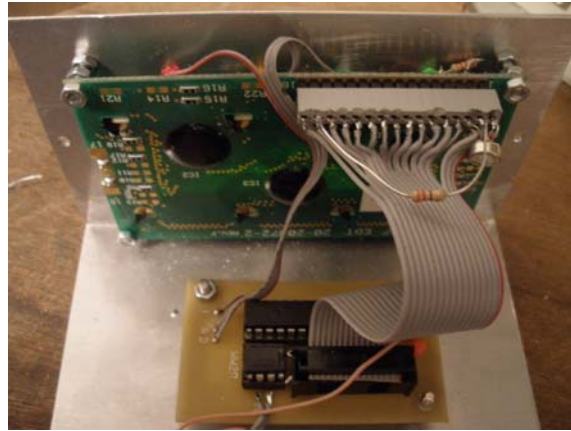

## TOSHIBA 100W 3400MHz AMP

## Dual Toshiba 9cm PA

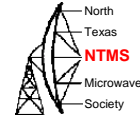


Have single amp. 5mW in 45W

Decided needed to combine two amplifiers

12V operation. Around 37A max

10mW In 100W output at 3400MHz

## Dual Toshiba Output Hybrid

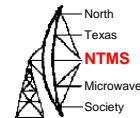

0.82 to 4.2 GHz



### Type N Coaxial 90° Hybrids

- Broadband Coverage
- Signal Isolation Over a Complete Band
- Low VSWR
- Flat Frequency Response
- 200 Watt Power Handling
- Cellular Band 500W Model 3322



### Specifications

FREQUENCY RANGE GHz	MODEL	COUPLING (Nominal)	VSWR dB	INSERTION LOSS dB (max)	ISOLATION dB (max)	AMP BAL dB	PHASE BAL Degrees	POWER Avg Watts	POWER Peak kW	WEIGHT lbs	WEIGHT kg
0.82-0.98	3322	3	1.25	0.20	20	±0.25	5	500	10	2	0.9
.99-2.0	3032	3	1.20	0.30	20	±0.25	5	200	5	1.5	.68
1.7-4.2	3033B*	3	1.25	0.35	20	±0.25	5	200	5	1	.5

## Dual Toshiba Combining

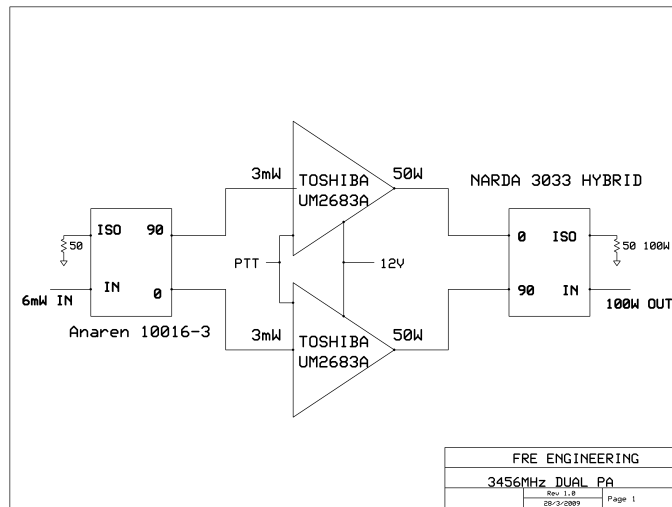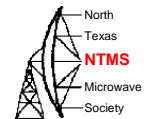

## Dual Toshiba 9cm PA

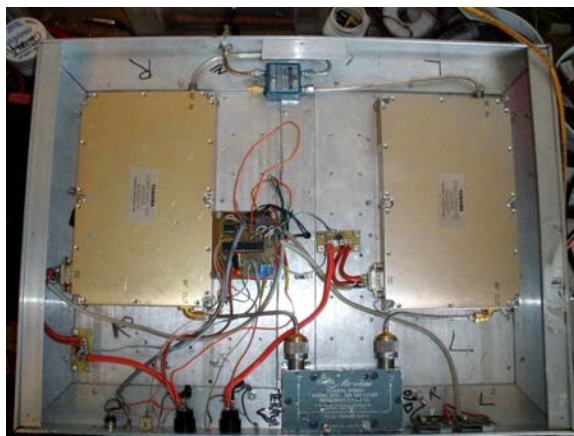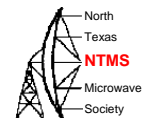

## 9cm amp location




In Infamous kennel at base of Dish


## Dual Toshiba Controller needs

- Status display
- Fan control
- Reverse power protection
- Overcurrent protection
- Bias control

# 9cm Amp remote unit

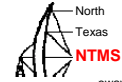


owave  
ety

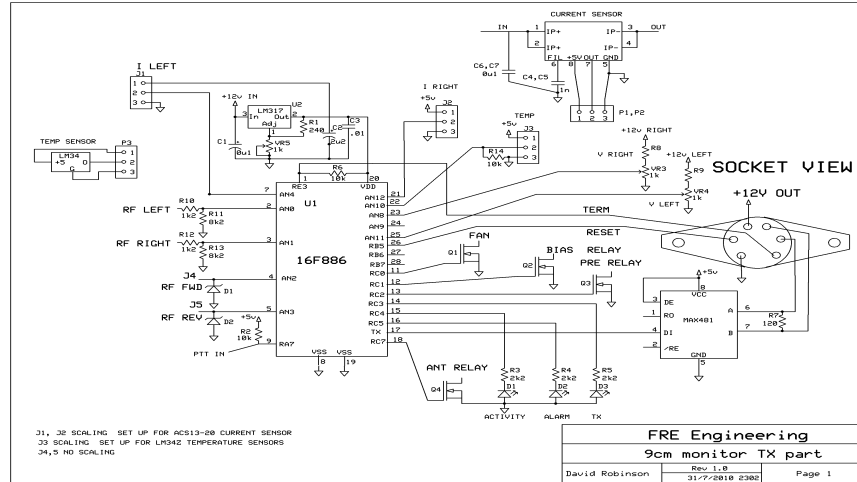


Note communication over RS422 link, RS232 doesn't work at 70'

# 9cm Amp local display

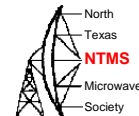

Microwave  
Society

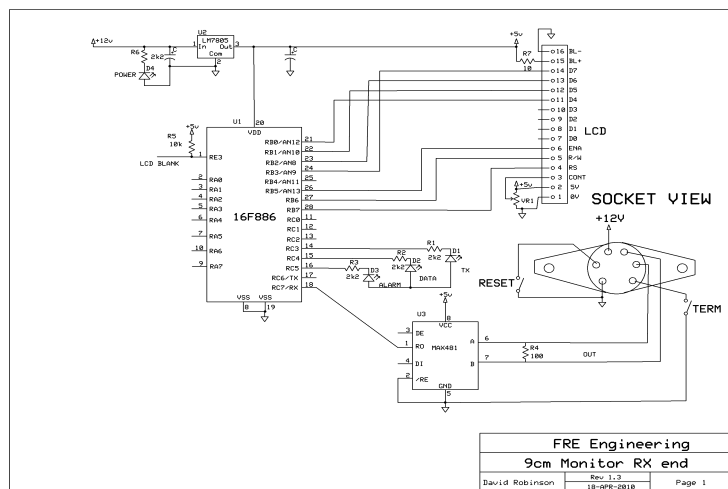

## Display in Shack



### LEDS

Power

Data from remote

Alarm

Transmit





### SWITCHES (On Back)

Preamp Term

Reset



## SPECTRIAN 13cm Amp

# Spectrian 13cm PA

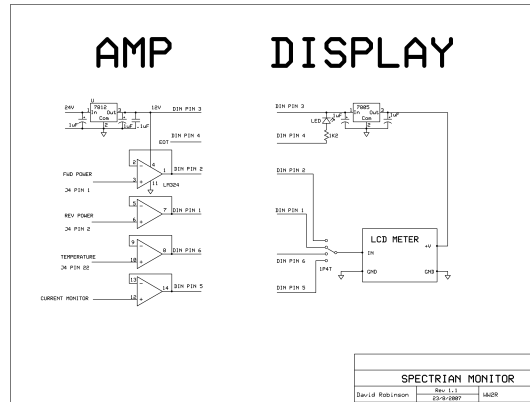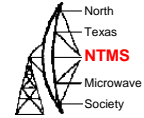

Like the Toshiba amp it lives out at the dish. Originally I fed 4 analog voltages back to shack to monitor status on LCD Voltmeter. Hard to see monitor all at once.



# Spectrian 13cm PA

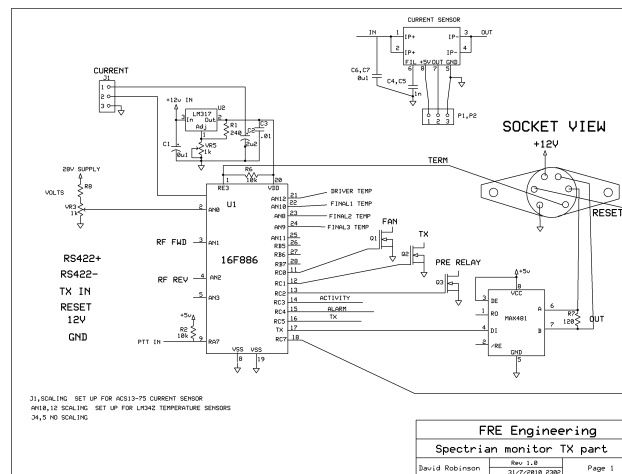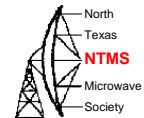


I Sensor: Allegro ACS750SCA-100 100A max



## Spectrian 13cm PA

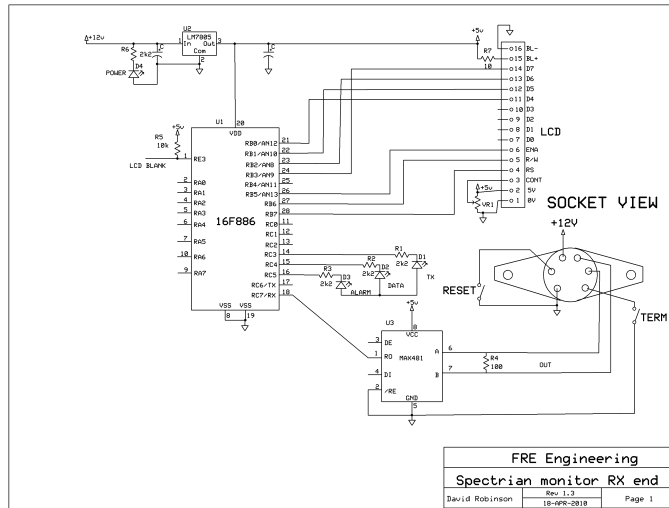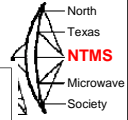



## Dual Spectrian 13cm PA

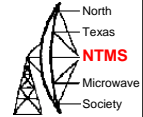


Having now got some protection for amps  
time to try a pair

Got some 500W rated hybrids that were CNC cut.

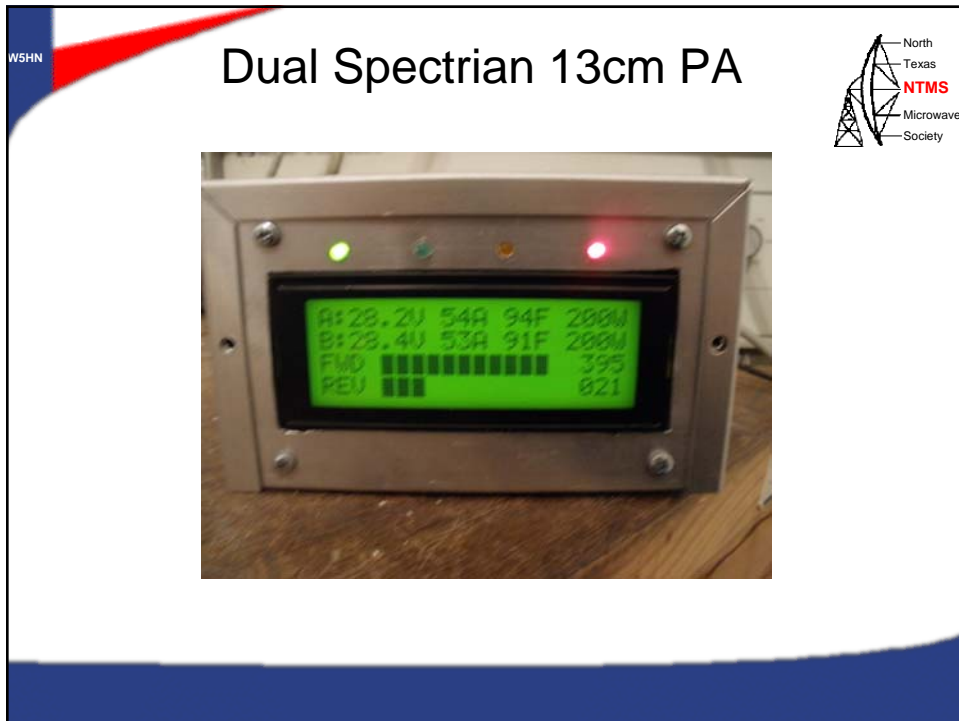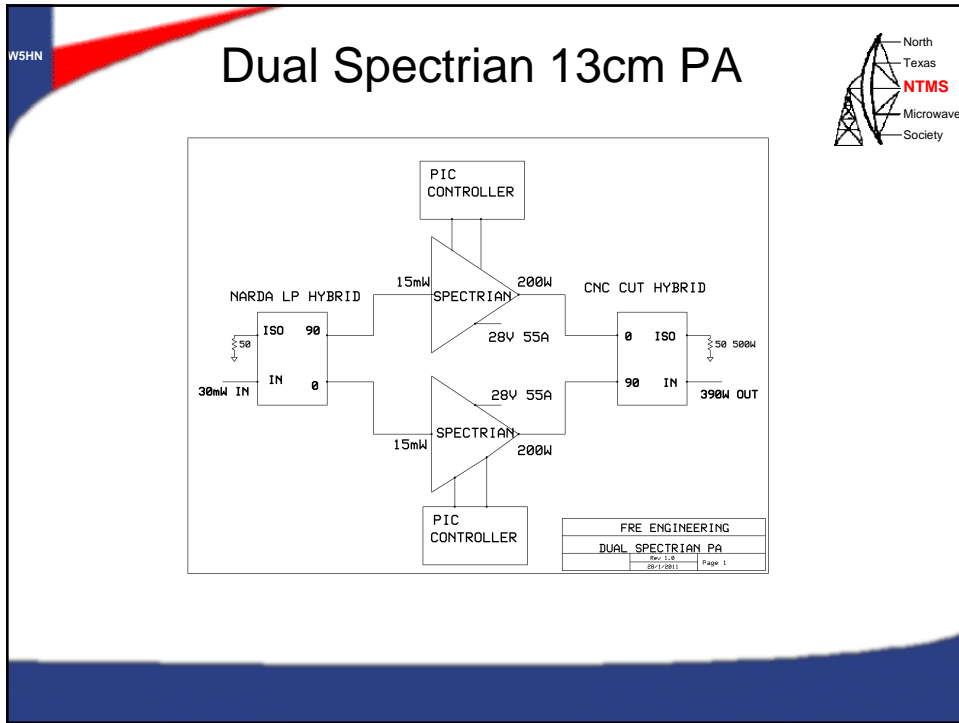Isolation and phase balance were impressive



## Dual Spectrian 13cm PA

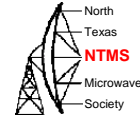


**30mW input 390W output**

**28V 110A total**


**Each amp has ~40dB gain. As W5LUA predicted this made equalising gain and phase a challenge**

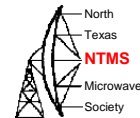**Tweaking driver stage bias helped get the expected output**



**I0JXX 144MHz Amp**

# I0JXX Amp

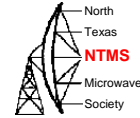


**Single MRF6VP2600 Device**


**2.5W In 500W output...IC202 Overdrives it**

**48V 16A peak**

## I0JXX AMP Finished

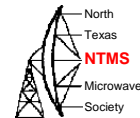

# I0JXX AMP Components


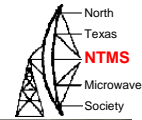


**Low Pass Filter**




**Surplus Directional Coupler**

# I0JXX AMP Controller

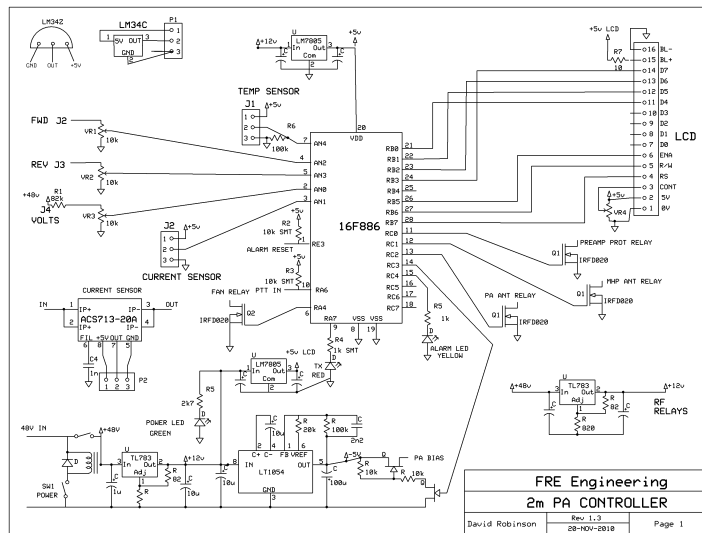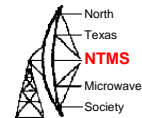

## More Information

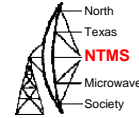

- 1296 Amp: [http://w6pql.com/xrf-286\\_amplifiers\\_for\\_23cm.htm](http://w6pql.com/xrf-286_amplifiers_for_23cm.htm)
- 1296 Amp Integration: <http://g4fre.com/400w1296pa.htm>
- Single Toshiba Amp: [http://g4fre.com/Toshiba\\_amp.htm](http://g4fre.com/Toshiba_amp.htm)
- Remote Spectrian monitoring <http://g4fre.com/Spectrian.htm>
- IOJXX integration: <http://g4fre.com/500w144pa.htm>
- HB9BBD W6PQL mods. Proceedings of MUD 2010 P22-27

Note W6PQL no longer sells the kits but I have seen PCB on the surplus market