

Eastern VHF/UHF Conference
April 18, 2009

Digital Station Enhancements K3TUF

A conglomeration of small
software/hardware devices that
make automated contesting a
reality

Outline

- ◆ Architecture Fundamentals
- ◆ Transmitter Keying
- ◆ Digital Sequencers
- ◆ Logging Software Interface
- ◆ DC Switching Circuit
- ◆ Distant Relay Activation


Architecture Fundamentals

- ◆ Use Transverters
- ◆ External T/R Switching
- ◆ Separate Amplifiers
- ◆ Each Band Stands on it's own
- ◆ Logging Must Drive Band Selection
- ◆ Common IF: Freq, TX Level, Keying
- ◆ Distributed Placement of Equipment

Transmitter Keying

- ◆ Traditionally a Separate PTT has been used
- ◆ Put keying on the IF coax
- ◆ Benefits Galore
- ◆ Use a Bias Tee
- ◆ Examples
- ◆ Simplifies Distributed Band Placement

Bias Tee

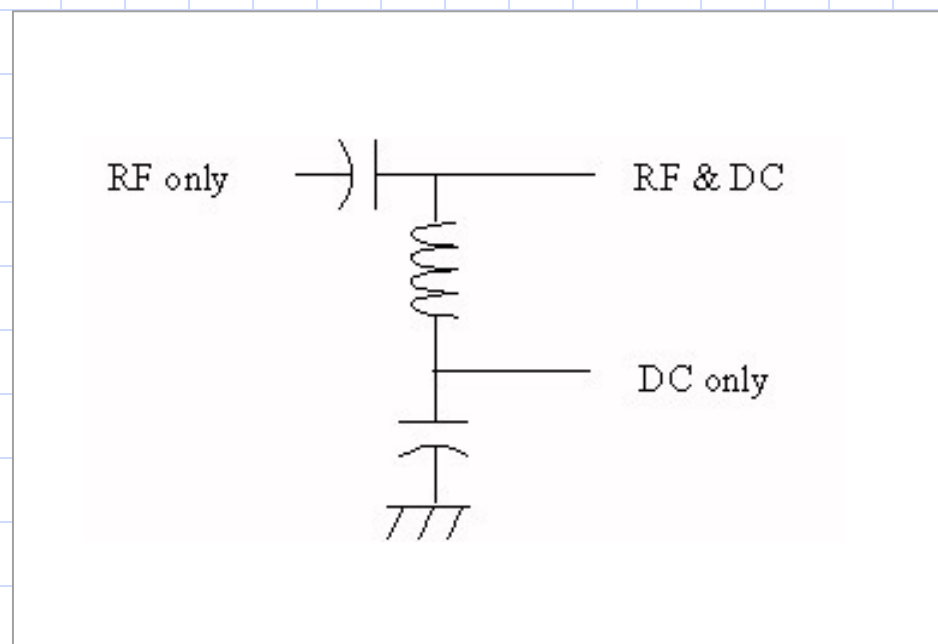





K3 XVTR Interface

DC INPUT
12 TO 24VDC

MFJ DEL


E
OU
EL


5000 XVTR Interface


TX


Digital Sequencers

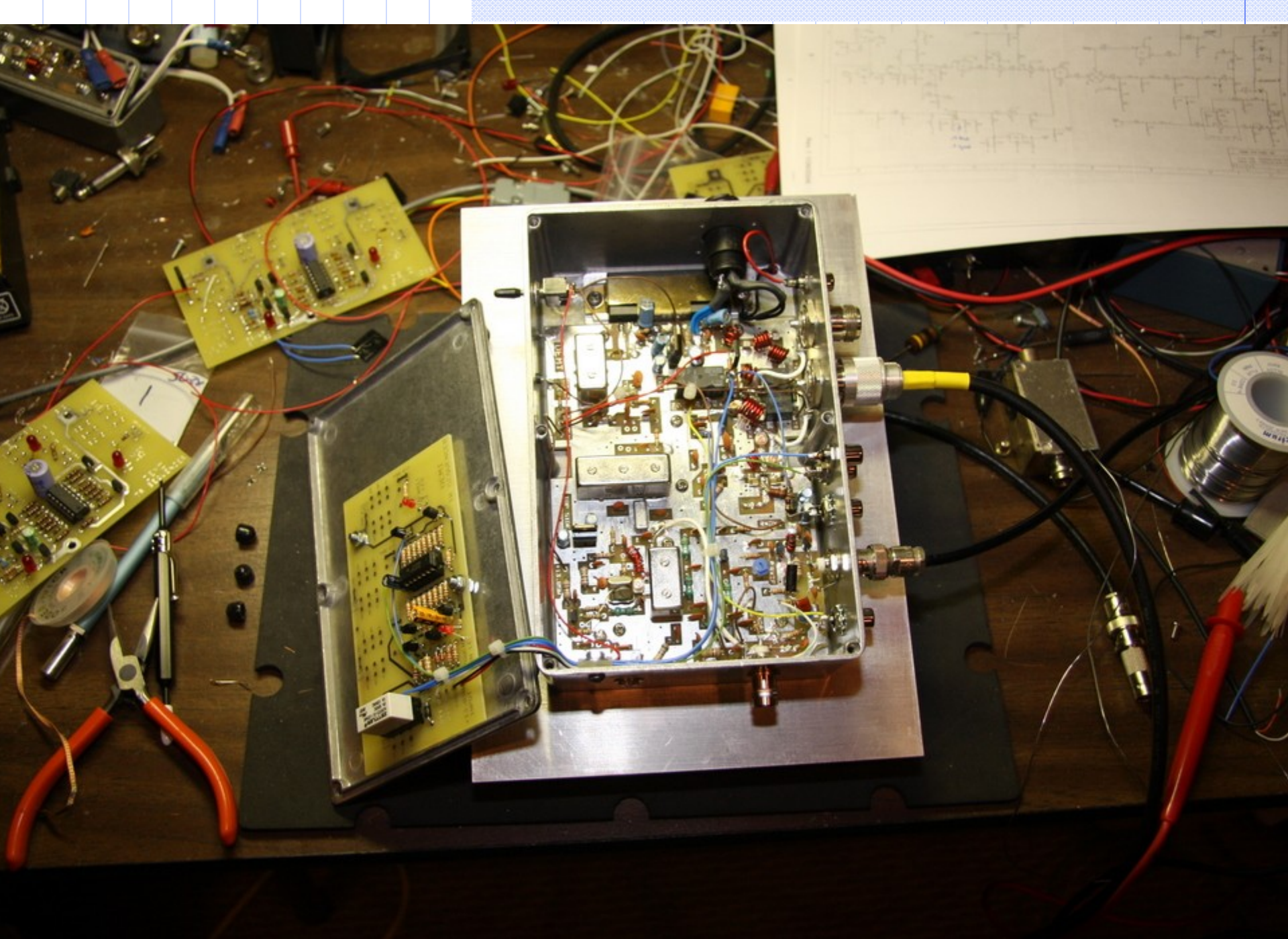- ◆ RF Protection for Front End
- ◆ Minimize the use of relays
- ◆ Integrate the Sequencer with the Transverter
- ◆ Make this an integral part of your System



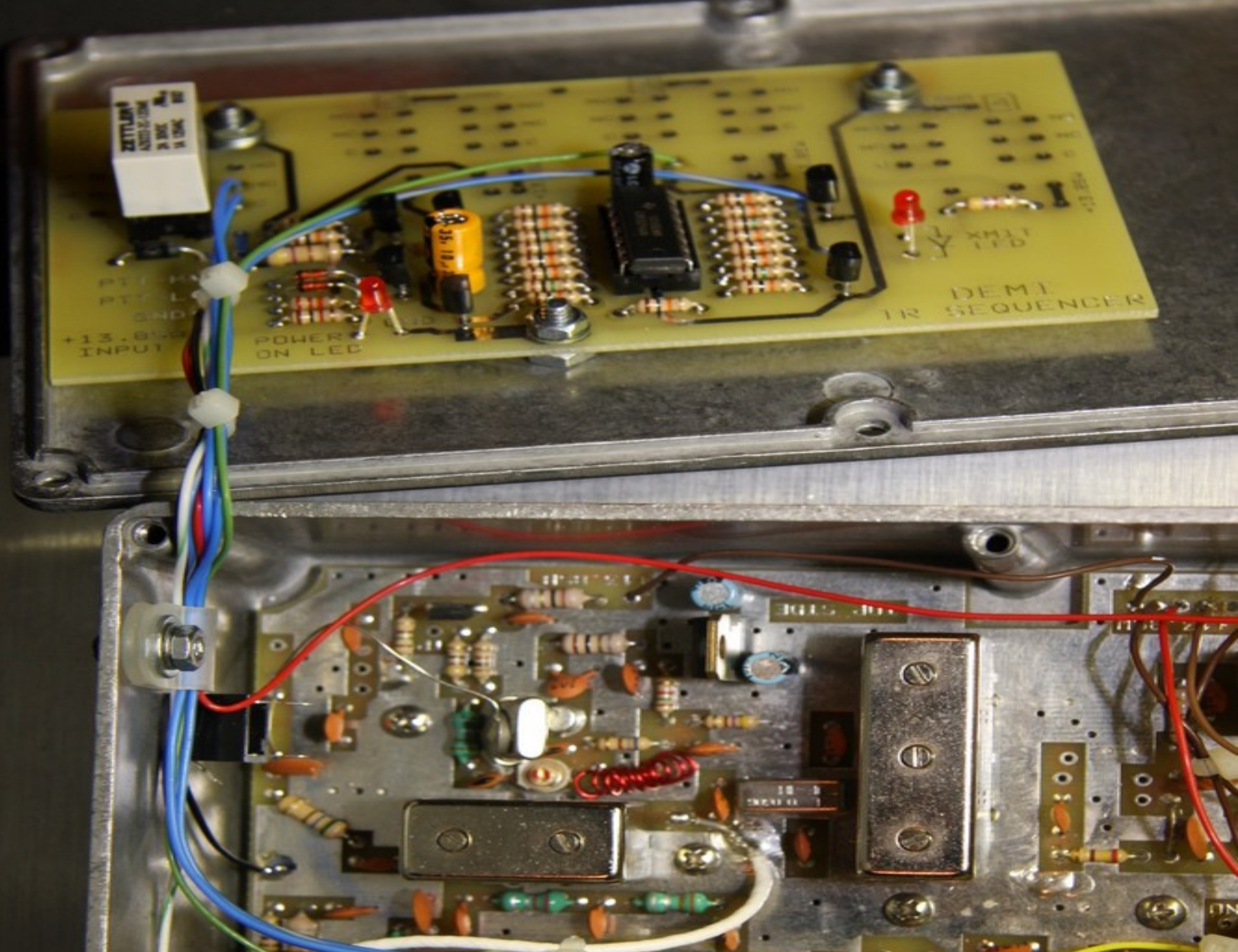


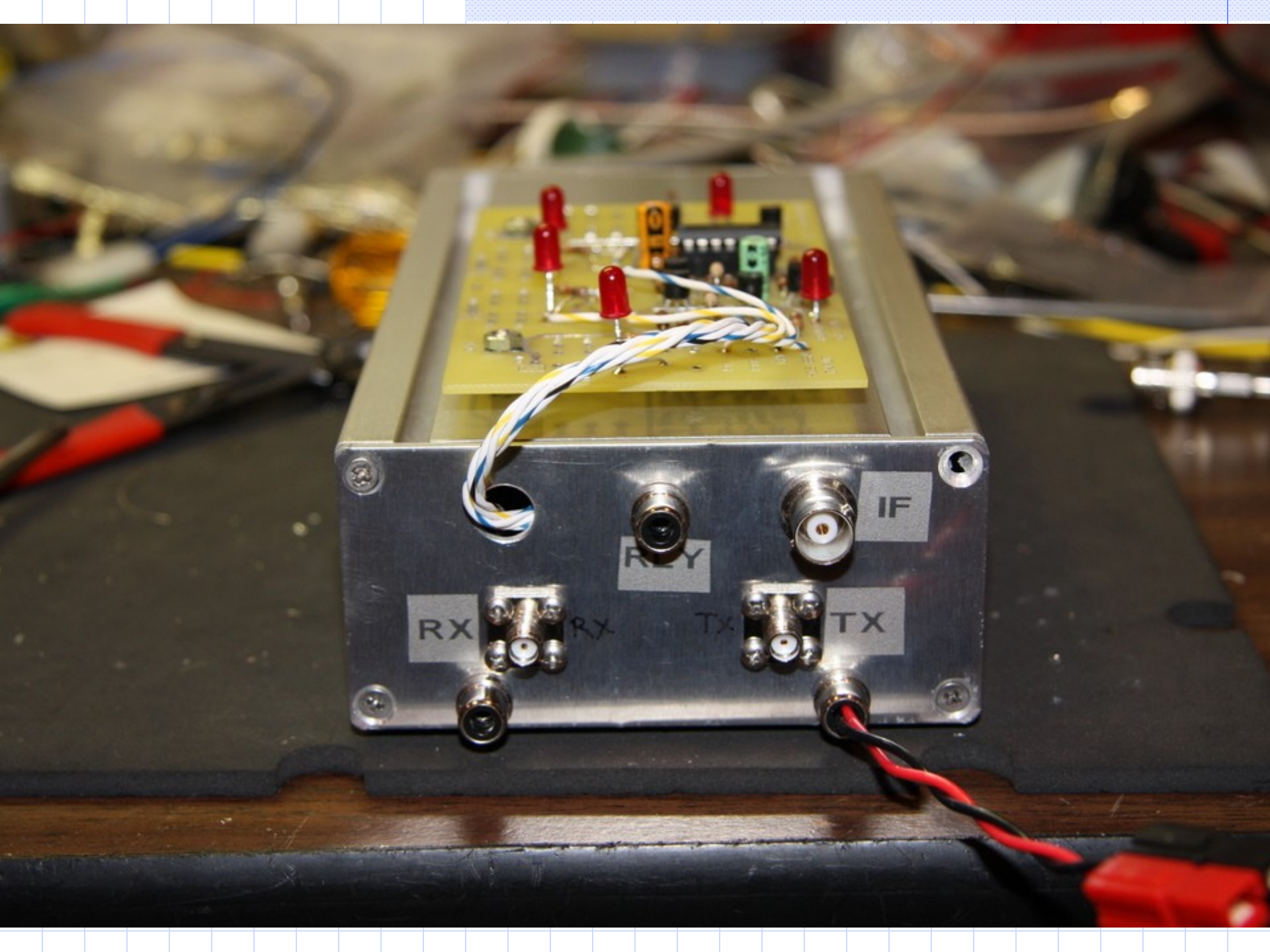


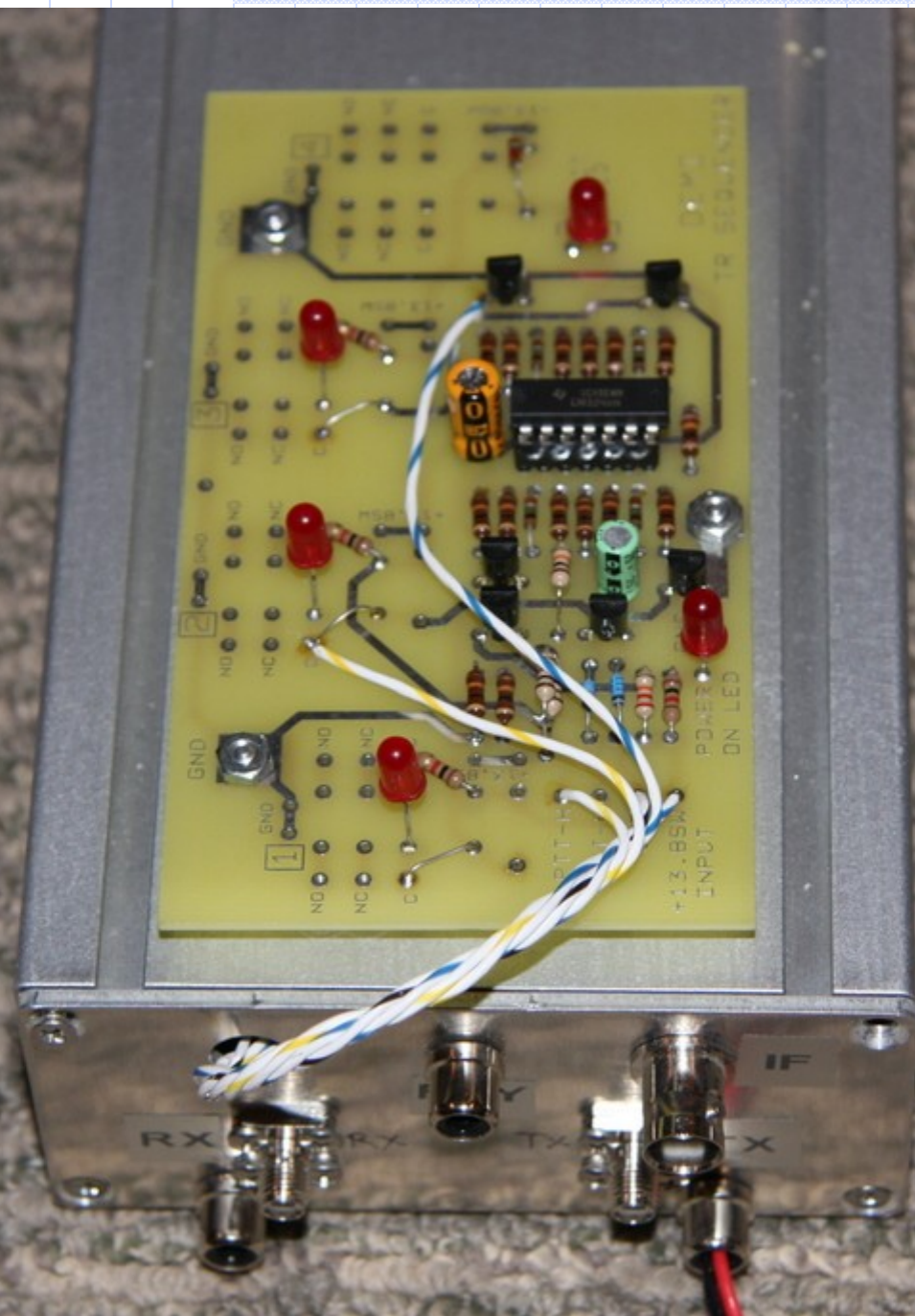





Logging Software Interface

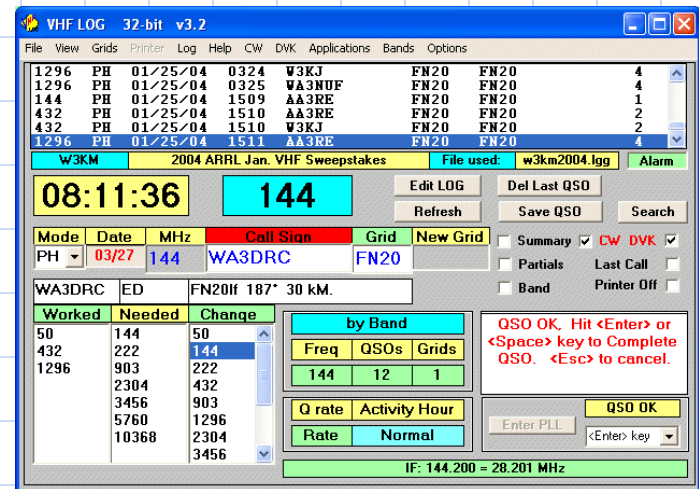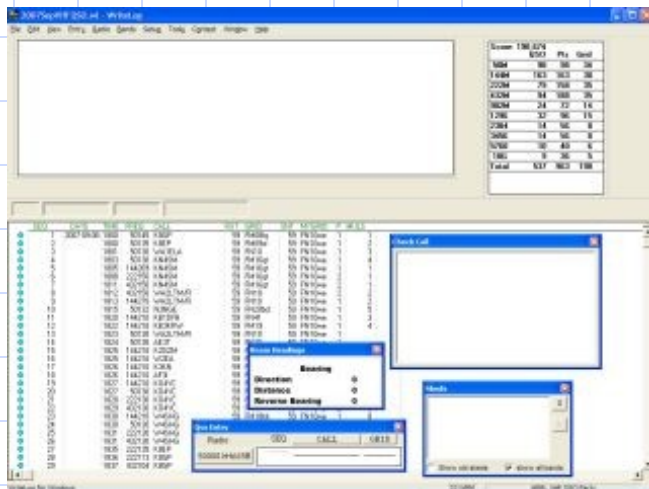
- ◆ Getting Band Data to the real world
- ◆ Keyer; MK-1100
- ◆ N3FTI
- ◆ UCB; Universal Controller Board



Heart of Interface: 4 to 16 Line Decoder

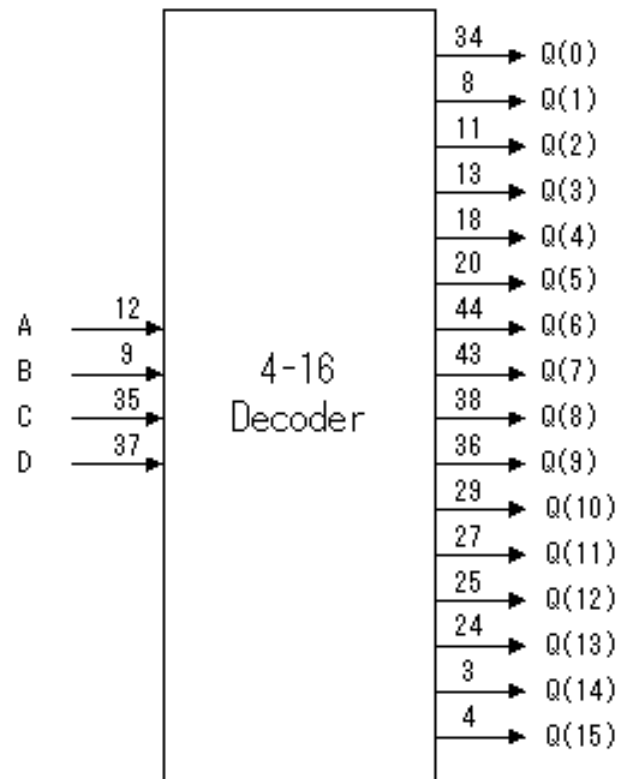

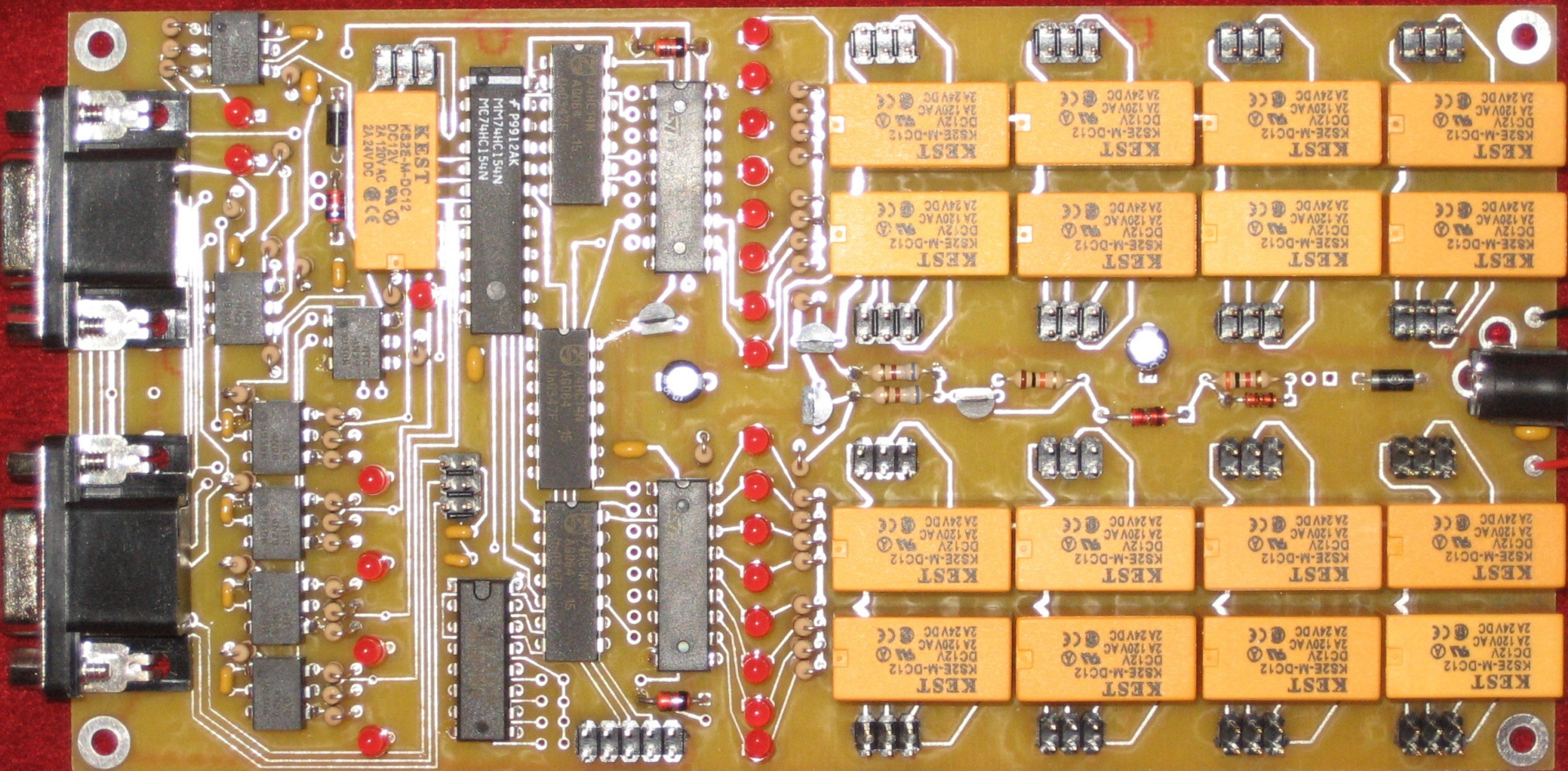

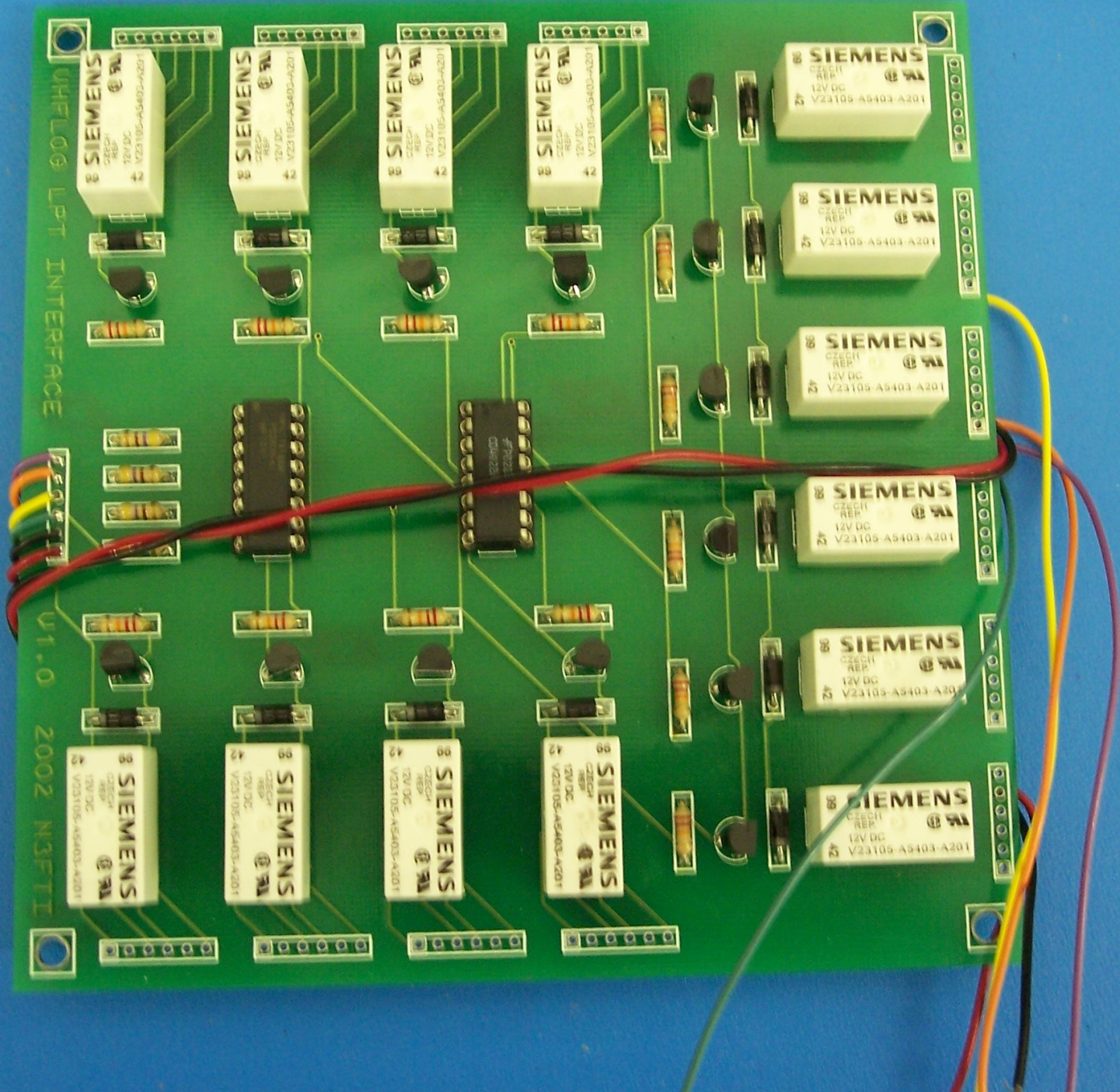

UHF/LPT INTERFACE

V1.0 2002 N3FTI

SIEMENS
CZECH REP.
12V DC
V23105-A5403-A201

SIEMENS
CZECH REP.
12V DC
V23105-A5403-A201

SIEMENS
CZECH REP.
12V DC
V23105-A5403-A201

SIEMENS
CZECH REP.
12V DC
V23105-A5403-A201


DC Switching Circuit

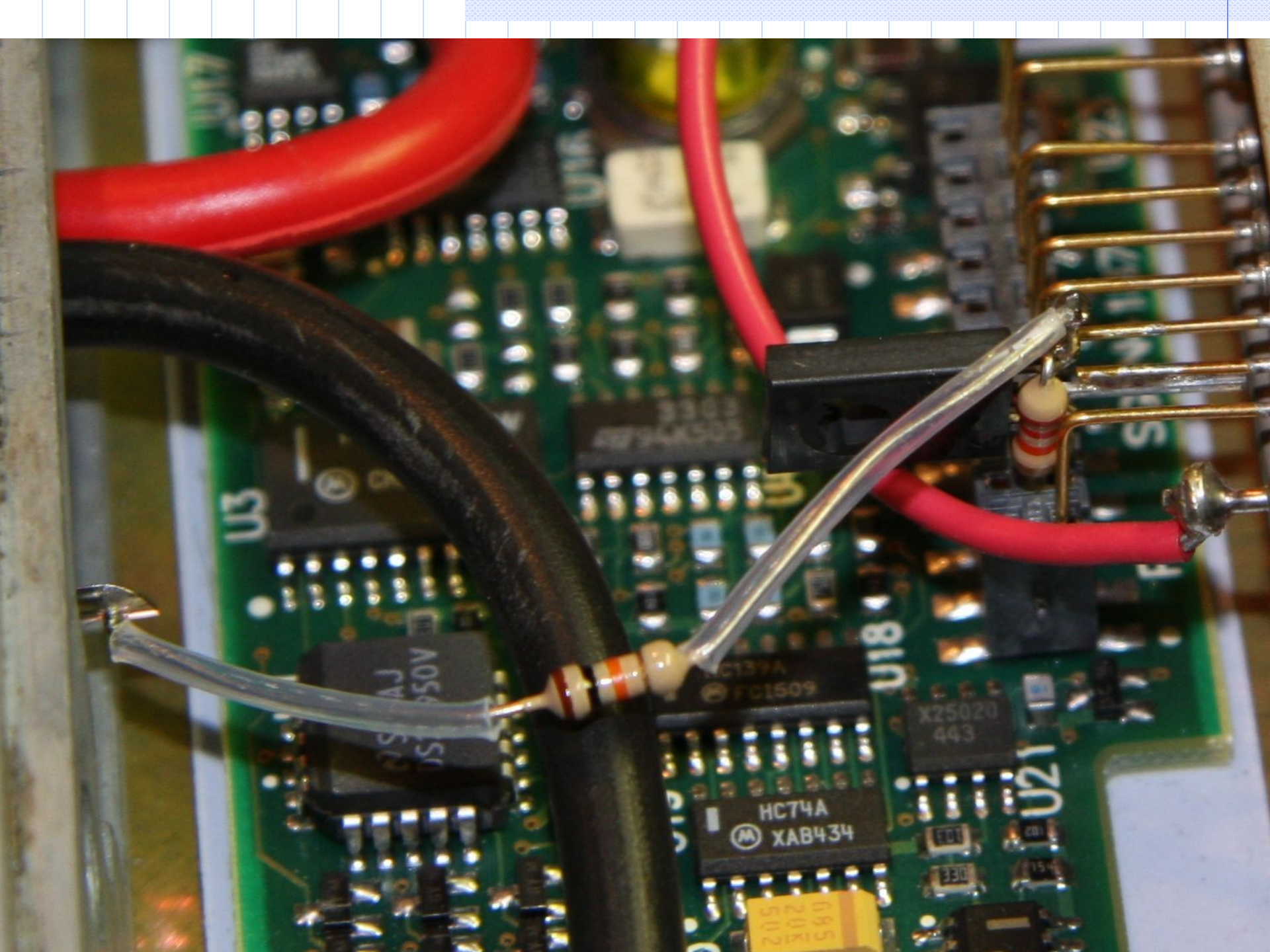- ◆ Use a single device to supply + VDC
- ◆ Inexpensive PNP Transistor
- ◆ Avoids Surplus or Failure-prone Relays
- ◆ Easy to implement
- ◆ Driven by open collector



Distant Relay Activation

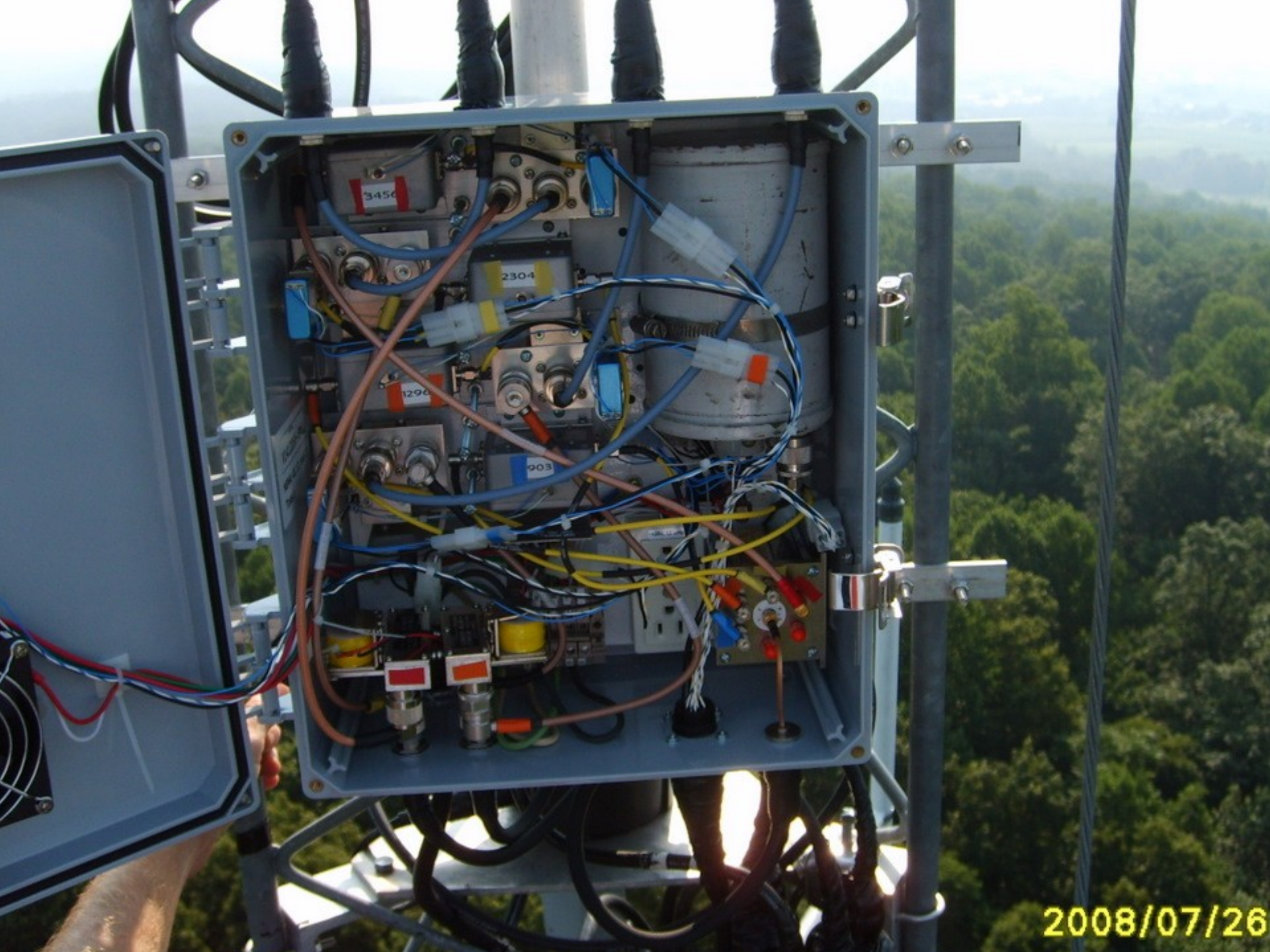- ◆ Dilemma: Relay at the top of the Tower
- ◆ Potential Solutions
 - Ignore; Indicator; Sensing; Current Sensing
- ◆ Indicators Increasingly Scarce and 26vdc
- ◆ Sensing is Exotic and Future
- ◆ Constant Current Regulation





2008/07/26

Constant Current Regulation

- ◆ Relay Coil is a Current Device
- ◆ LM-317 as a Current Regulator
- ◆ Takes slightly Higher Voltage
- ◆ Enforces Constant Current
- ◆ Permits Positive Indication with an LED


Constant Current Regulator

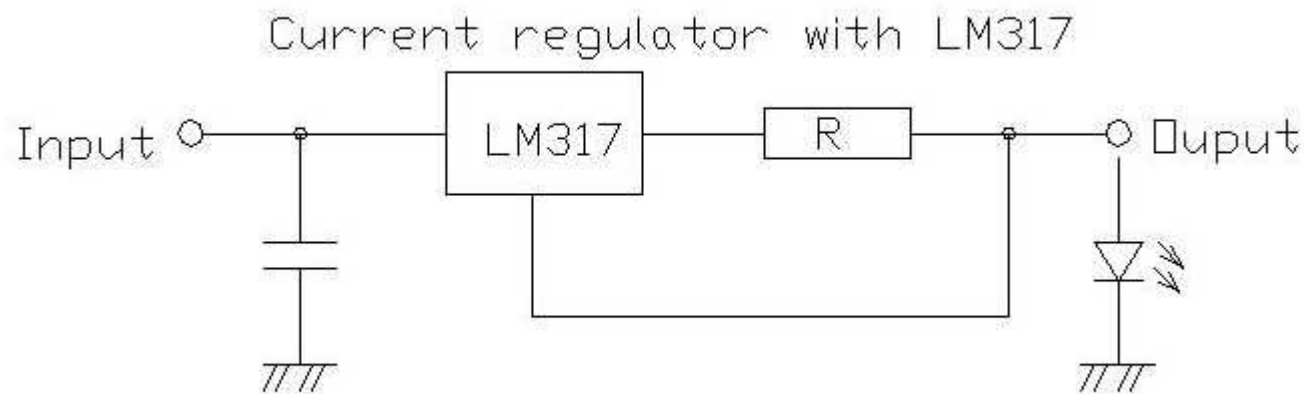

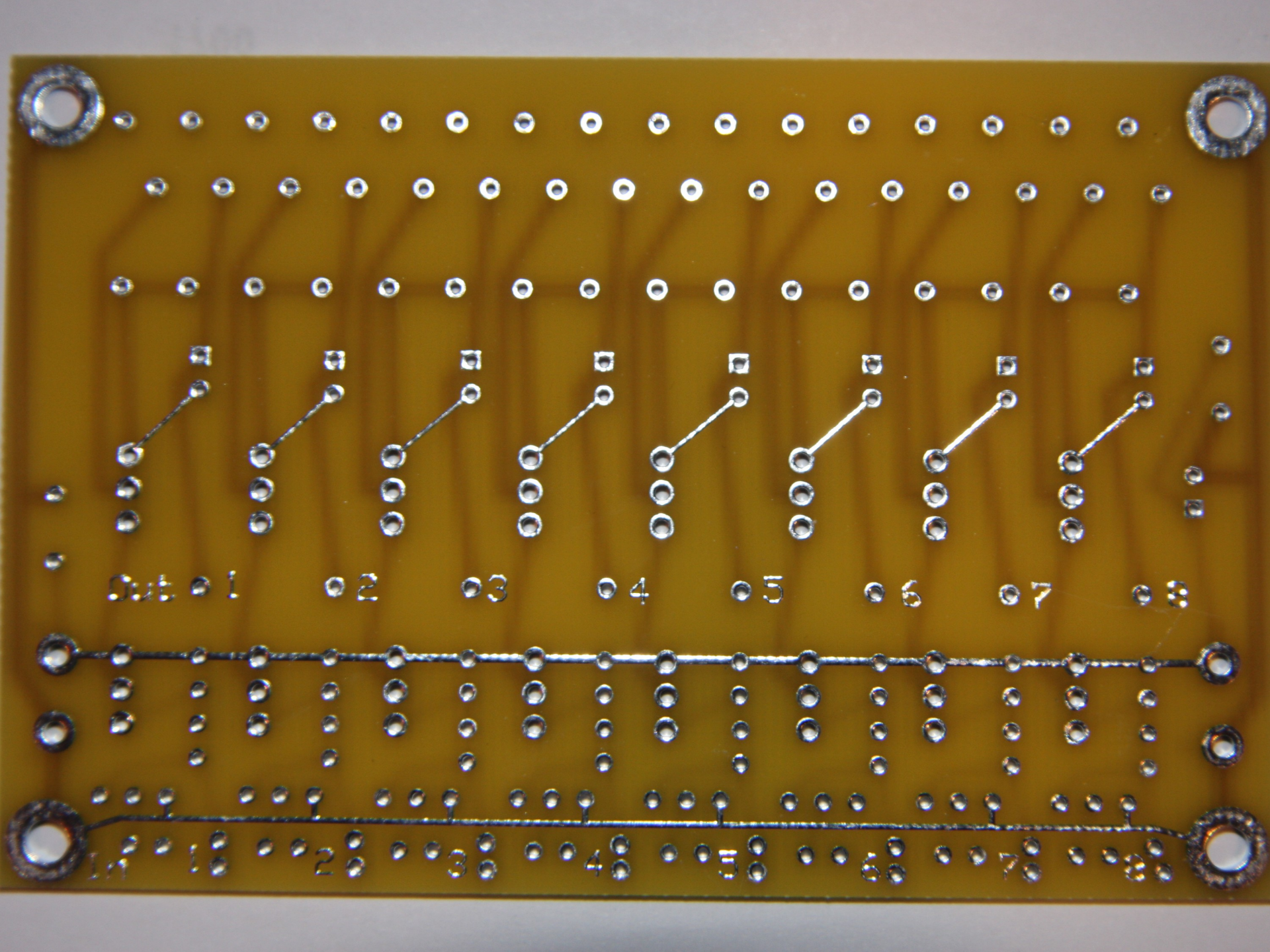

Out 1 2 3 4 5 6 7 8

1 2 3 4 5 6 7 8

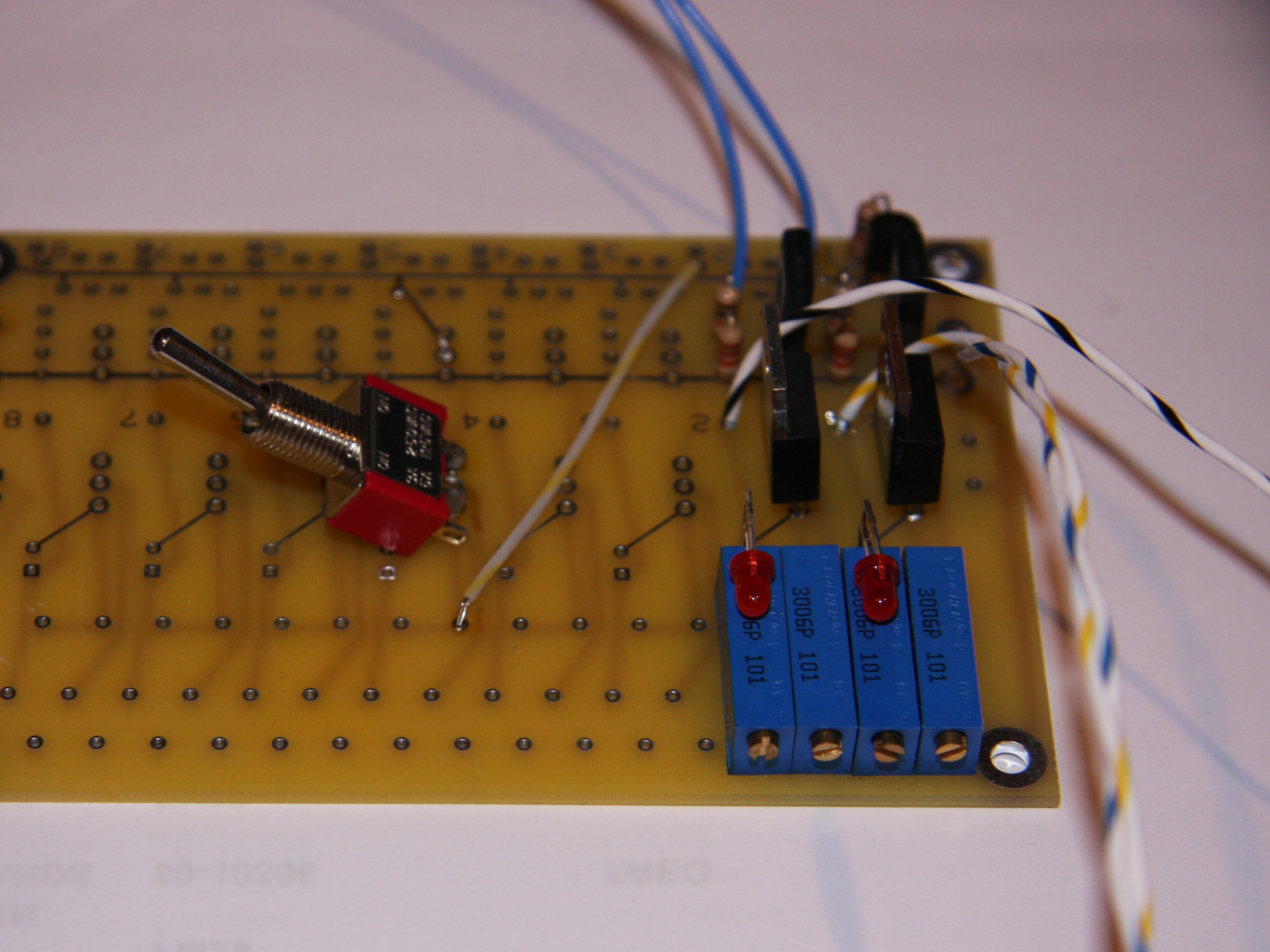

CHANNEL SELECTOR



Putting it all Together

- ◆ TTL Circuits
- ◆ Distributed Control
- ◆ Logic over Relay where possible

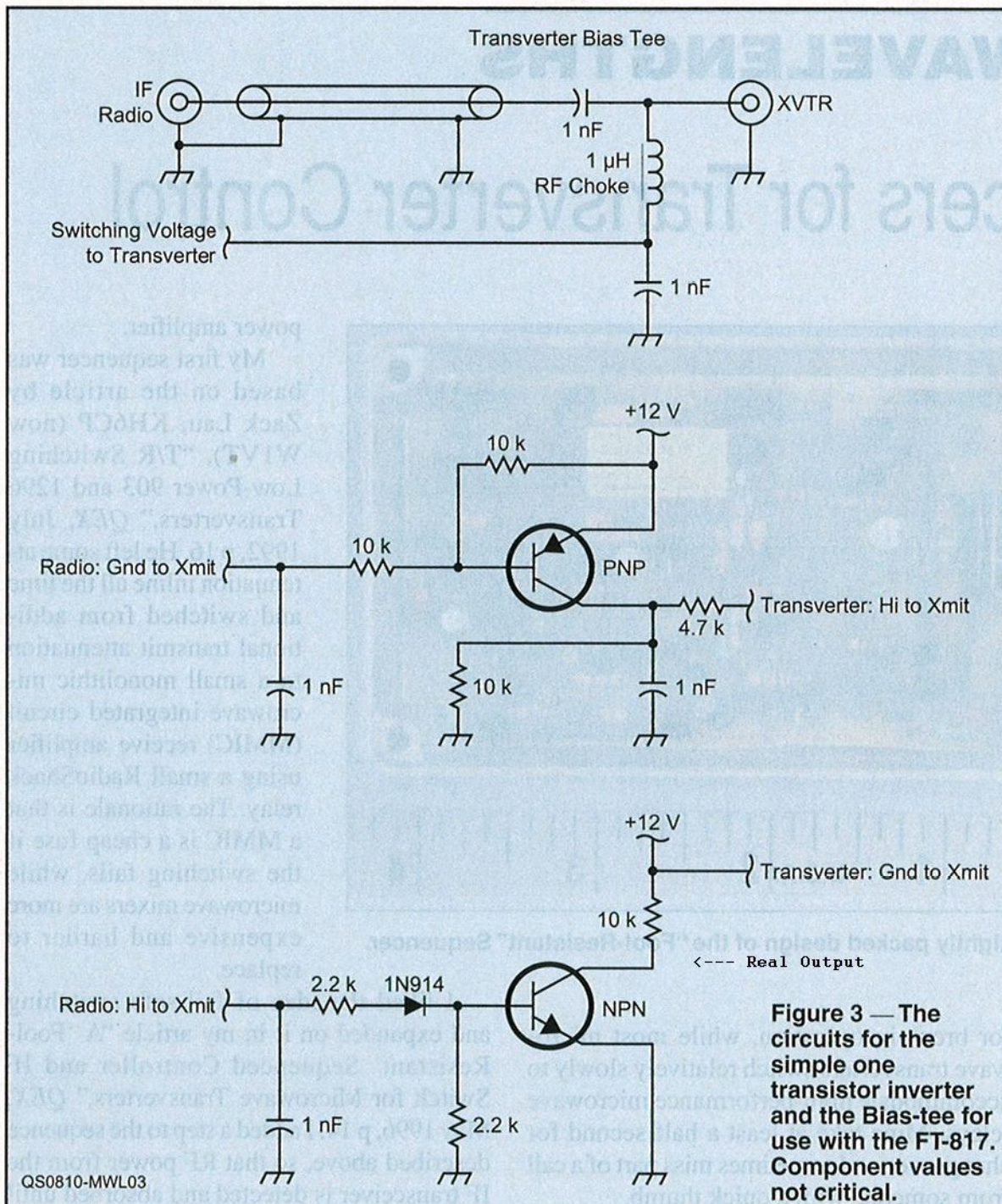



Figure 4 —
mounted on



Figure 5 —
constructio
Bias-tee.

Figure 3 — The circuits for the simple one transistor inverter and the Bias-tee for use with the FT-817. Component values not critical.

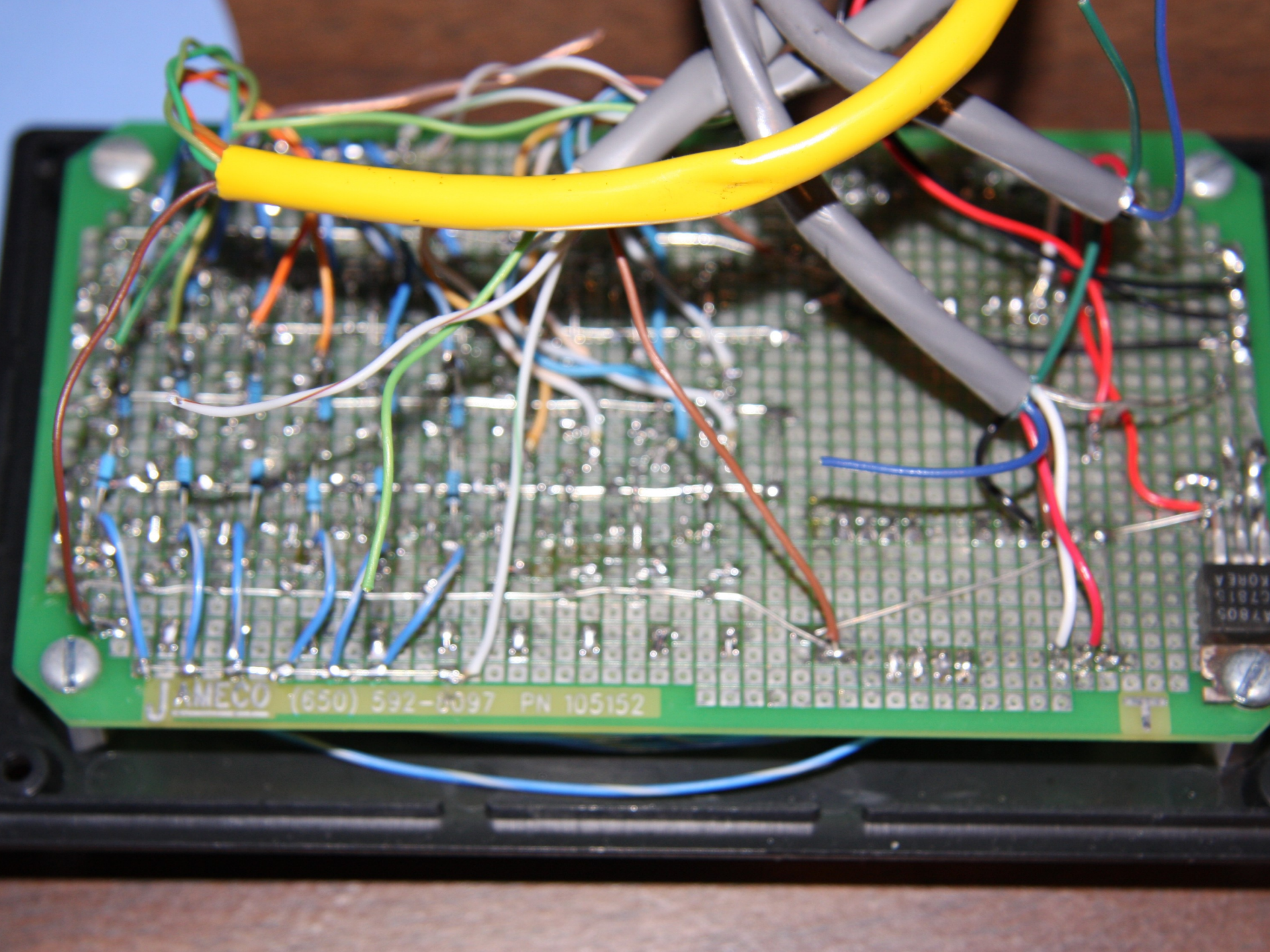
I looked ov
didn't find
fication. Ins
onto the co
to as a Bias
with three c



JAMECO (650) 592-6097 PN 105152


A7805
C7815
KOREA

276-1683

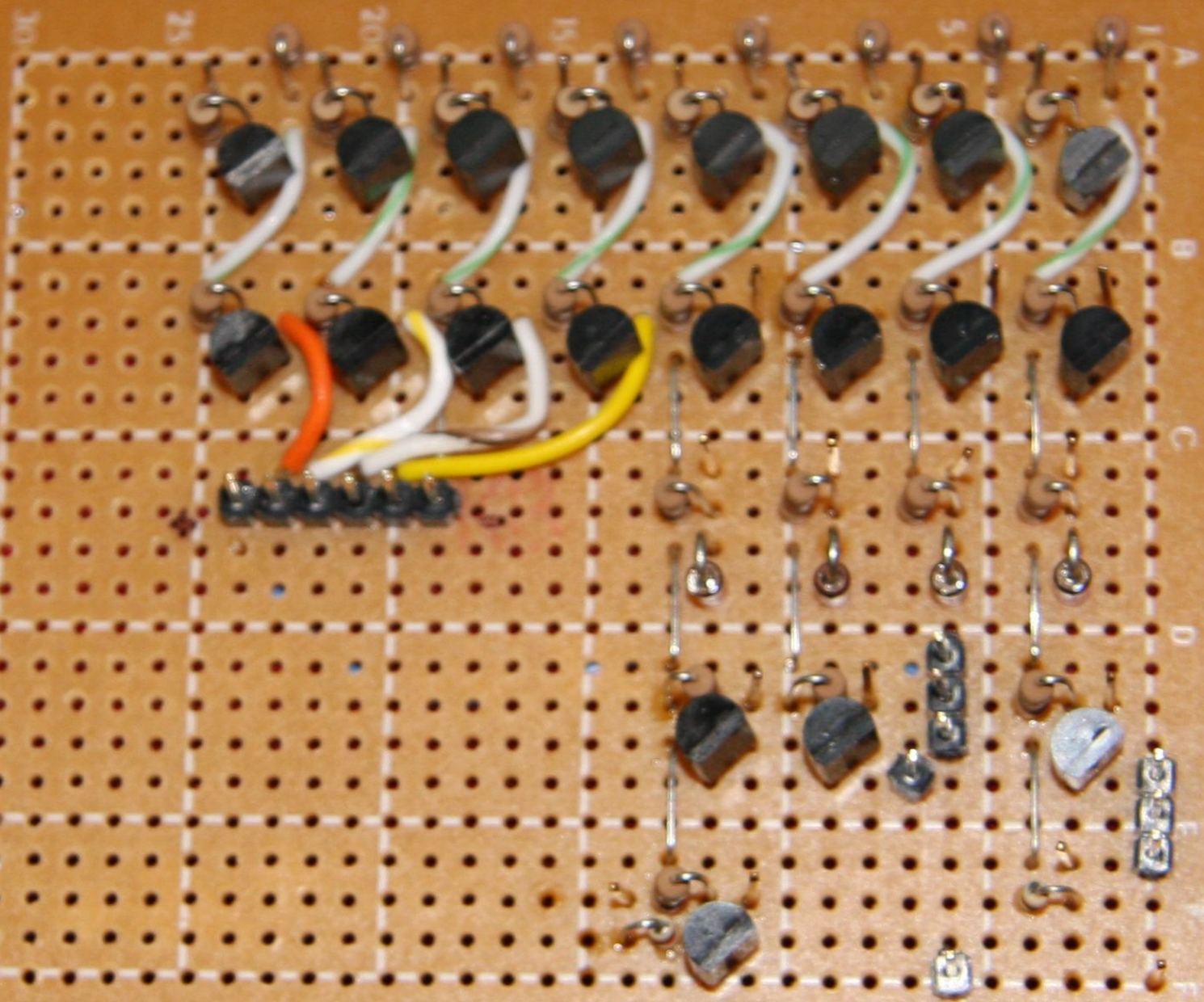

Summary

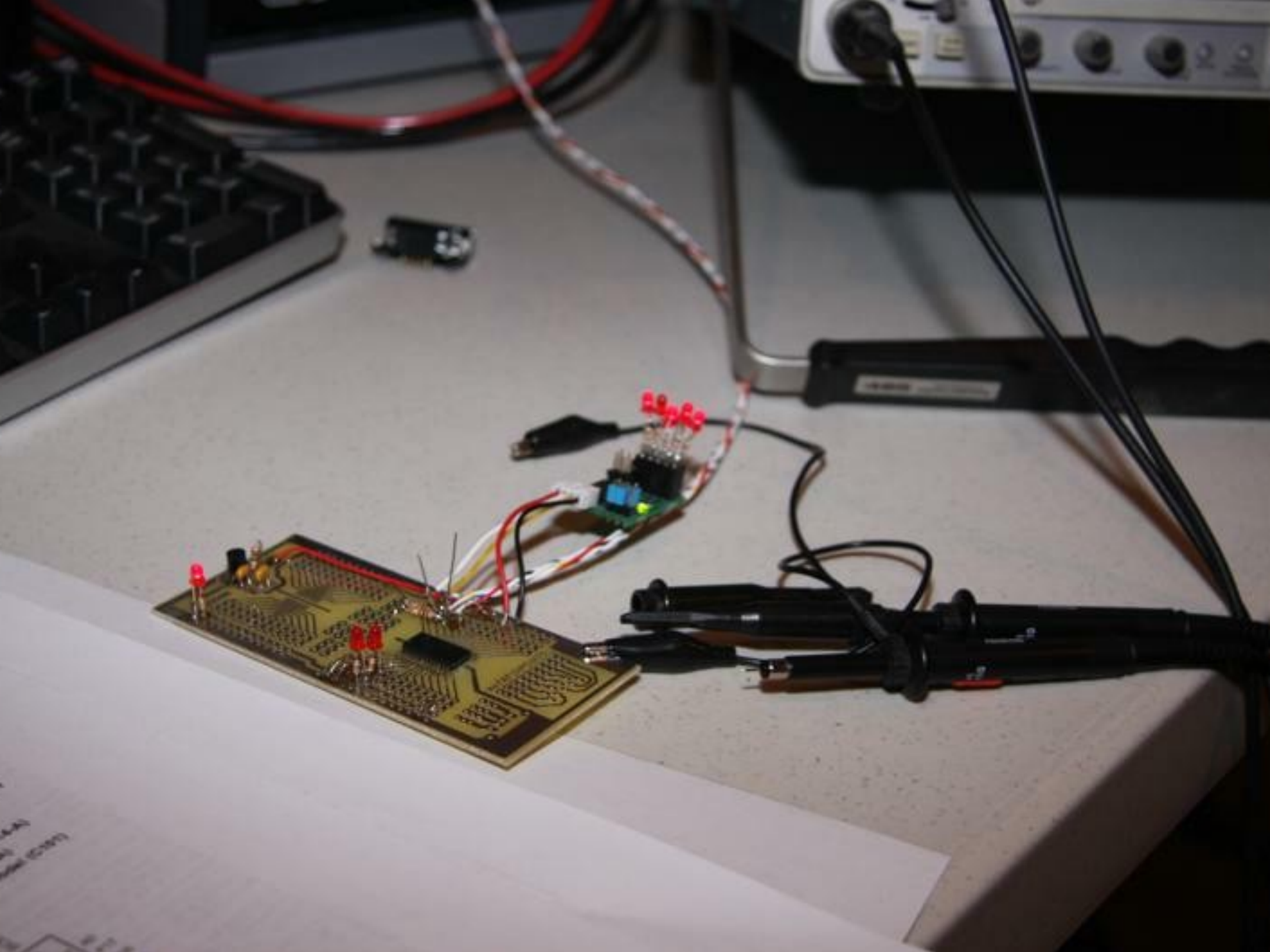- ◆ Benefits of RF Architecture
- ◆ Small circuits provide incremental improvements
- ◆ Reliability of proven technology
- ◆ Proof over time
- ◆ Illustration @ K3TUF and W1GHZ







2008/08/16



