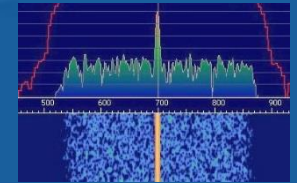


# *A Low Cost Panadapter Interface to a SDR dongle for radios with a 50 to 70 MHz 1st IF*



# Topics Covered



## Design

- Find out what others have done & define design objectives
- Circuit design, component selection, PCB generation


## Prototype Construction & Testing

- Filters – simulation & verification
- Main board PCB
- Installing the PCB in a radio

## Application Software


- How do you use this thing?

# What others have done

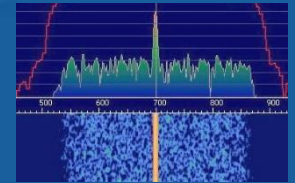
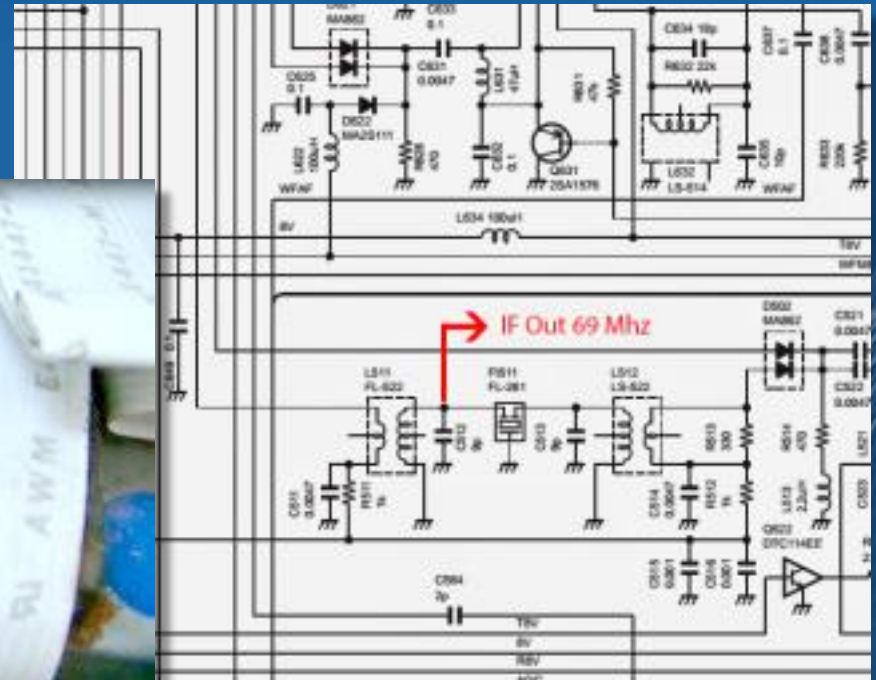
## Coax connection directly to the radio's 1<sup>st</sup> IF


- It works but radio performance can be compromised



PU2VLW taps the IF on  
an ICOM 706




# What others have done...

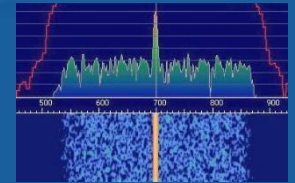

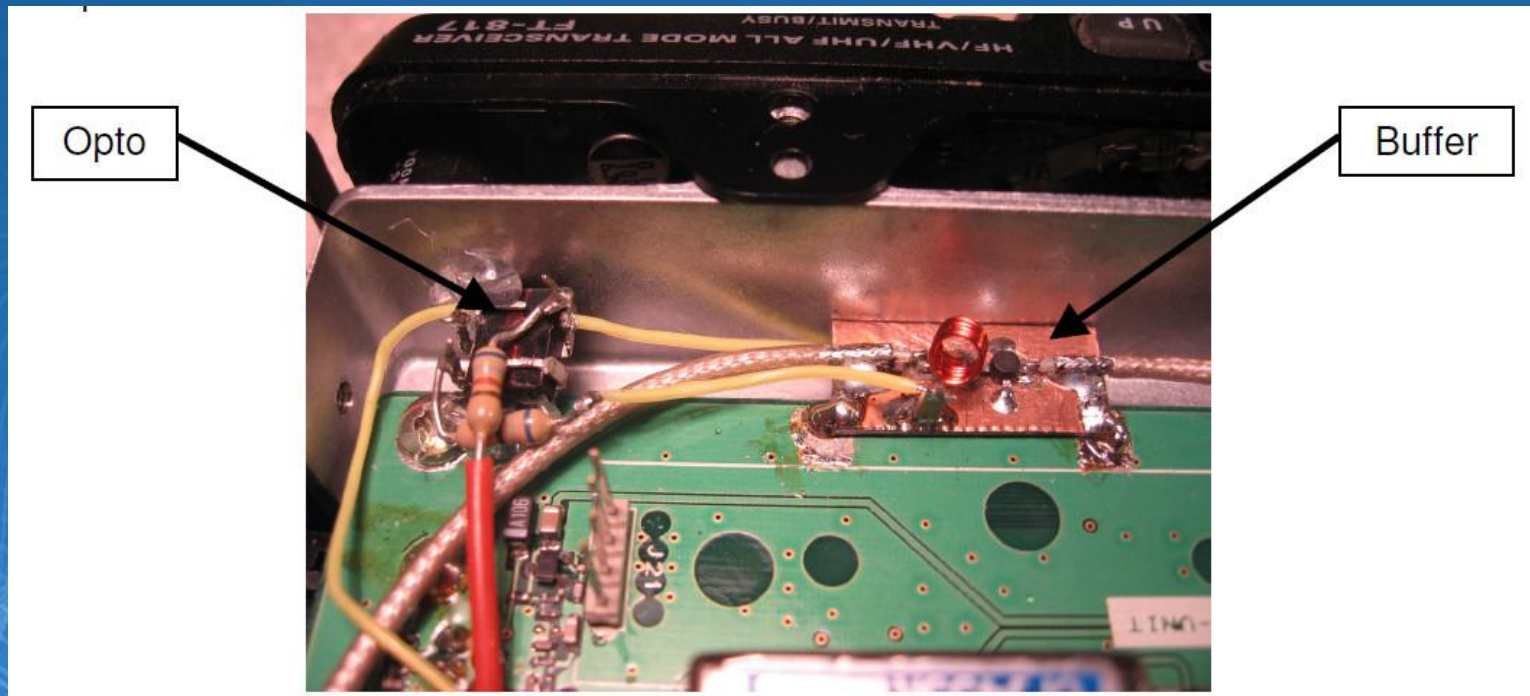
## Mike Seguin N1JEZ & Don W1KEF

- Cap coupled MAR6 MMIC buffer amplifier at the 1<sup>st</sup> IF
- Opto isolator switch frm PTT line turns amplifier off during Tx
- Interface to FUNcube dongle via Mini-Circuits SBP70+ filter







# ***What others have done...***

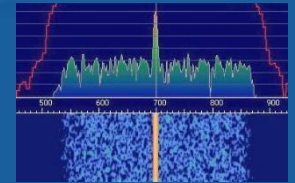

## ***N1JEZ installation in FT817***

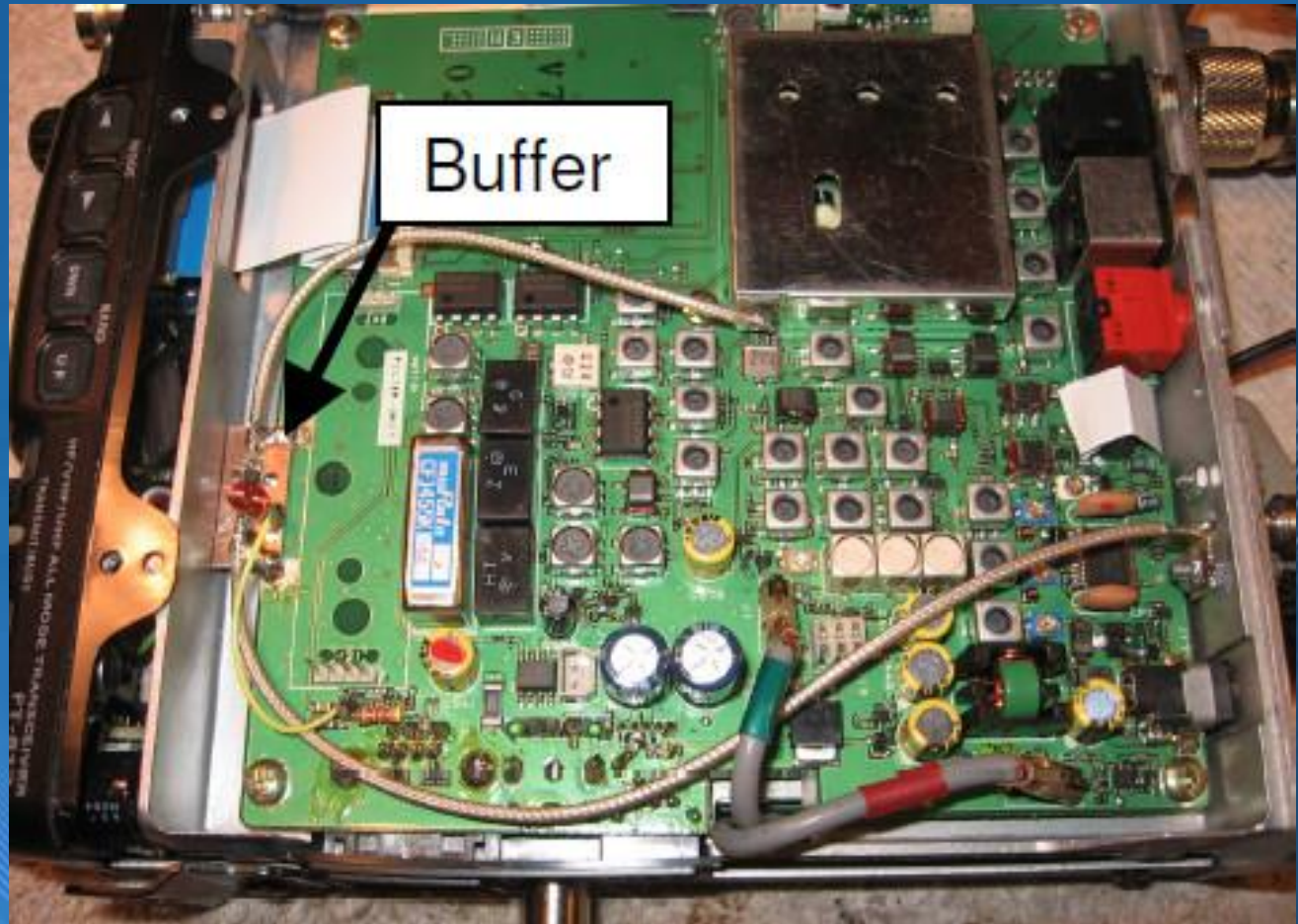


# What others have done...

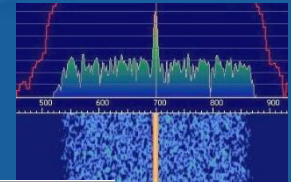

## SPB70 Filter

CENTER FREQ. (MHz)	PASSBAND (MHz)	3dB BANDWIDTH (MHz)	STOPBANDS	
			(I. loss > 20 dB) at MHz	(I. loss > 35 dB) at MHz
70	I.L. 1.5 dB Max. 63-77	Typ. 58-82	51 & 94	6.0 & 193-1000

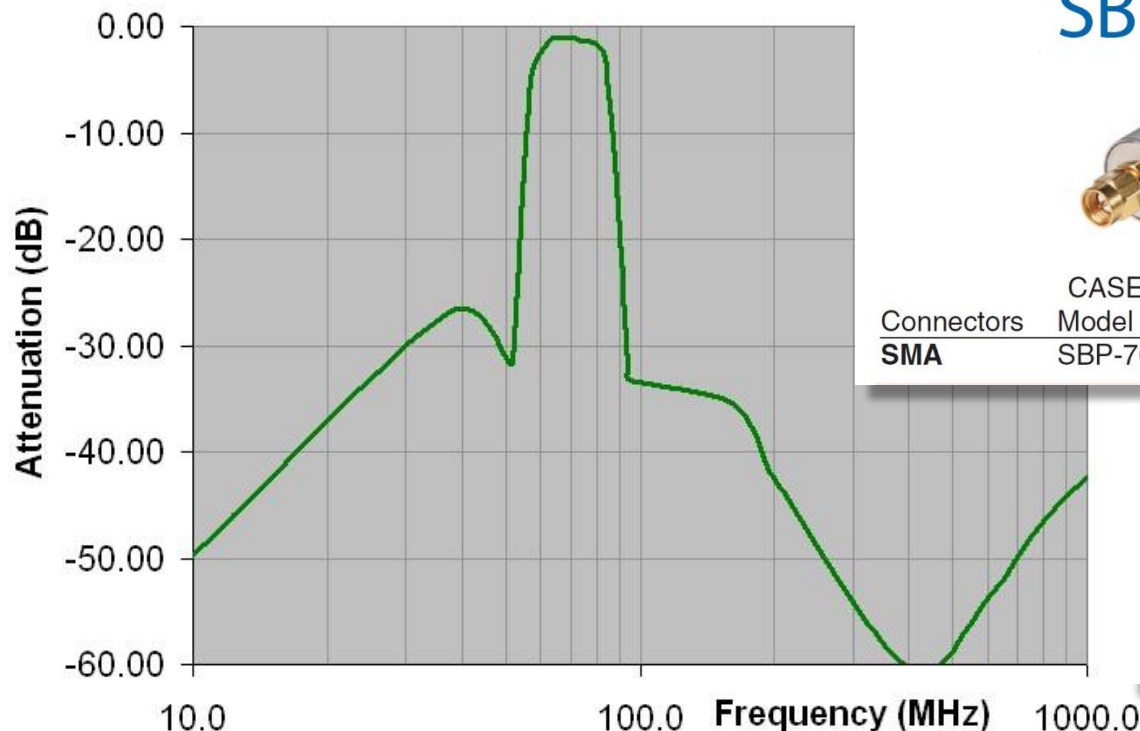


## SBP-70+



CASE STYLE: FF99

Connectors	Model	Price	Qty.
SMA	SBP-70+	\$42.95 ea.	(1-9)

### electrical schematic

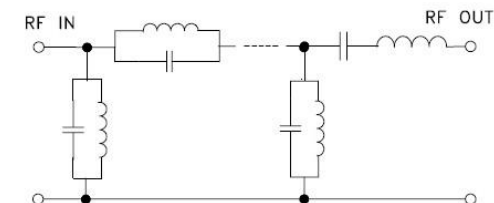





# ***What others have done...***

***Paul Wade W1GHZ***

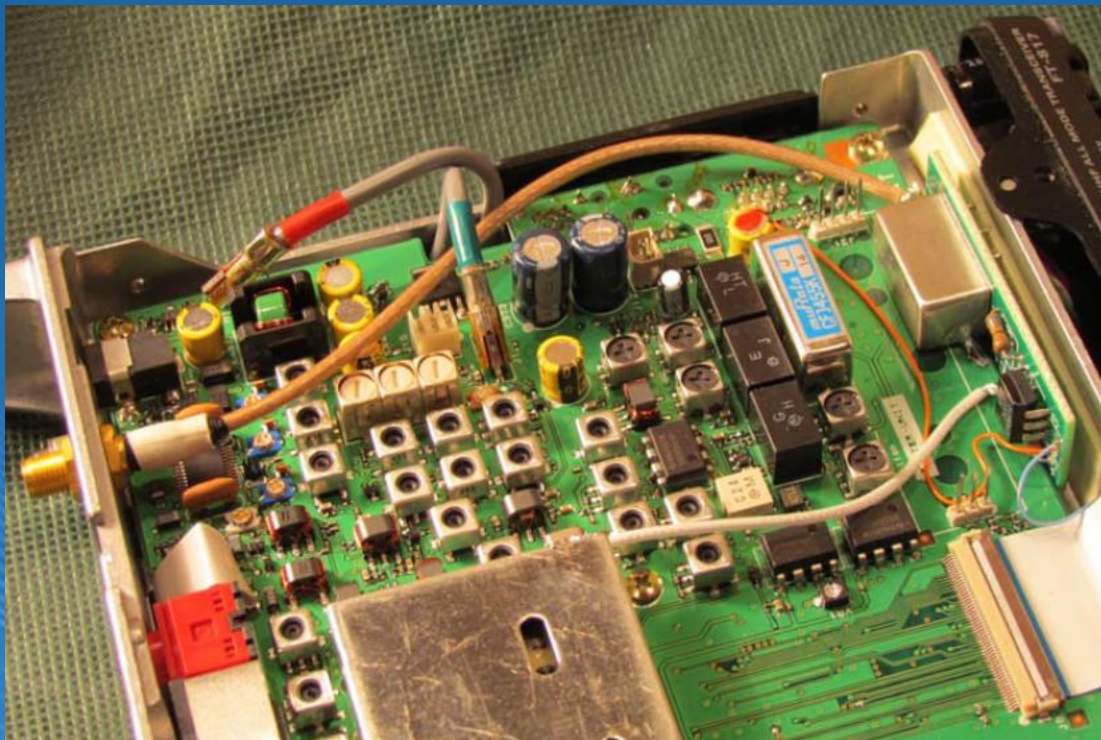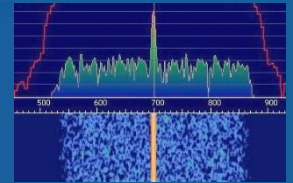
***PCB for the FT-817 Panadapter***

- Creates a PCB for Mike's design using less expensive PC mounted version of the Mini-Circuits MPL-PBP70 filter








# What others have done...

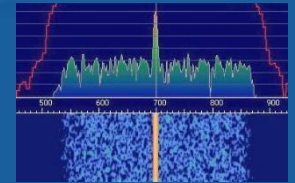


## W1GHZ cont'd

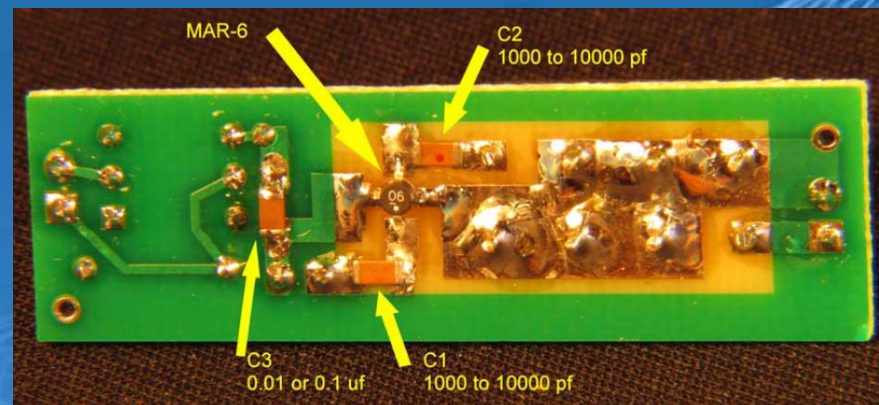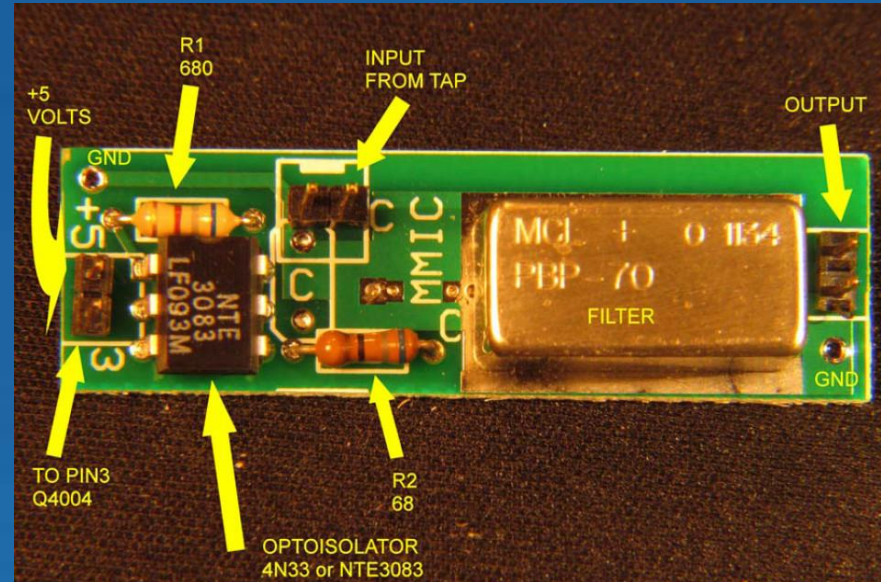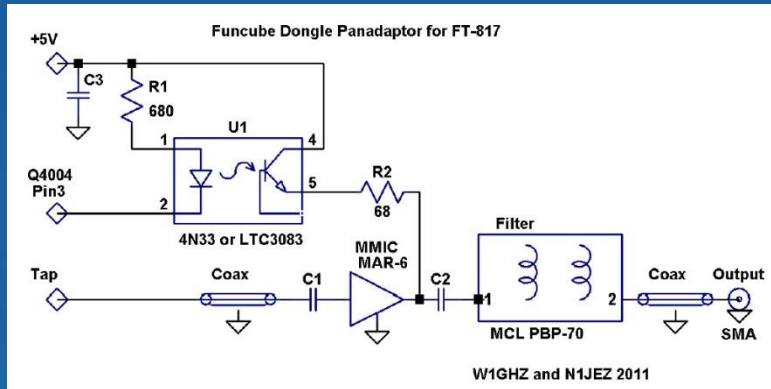




# ***What others have done...***

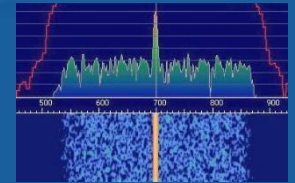

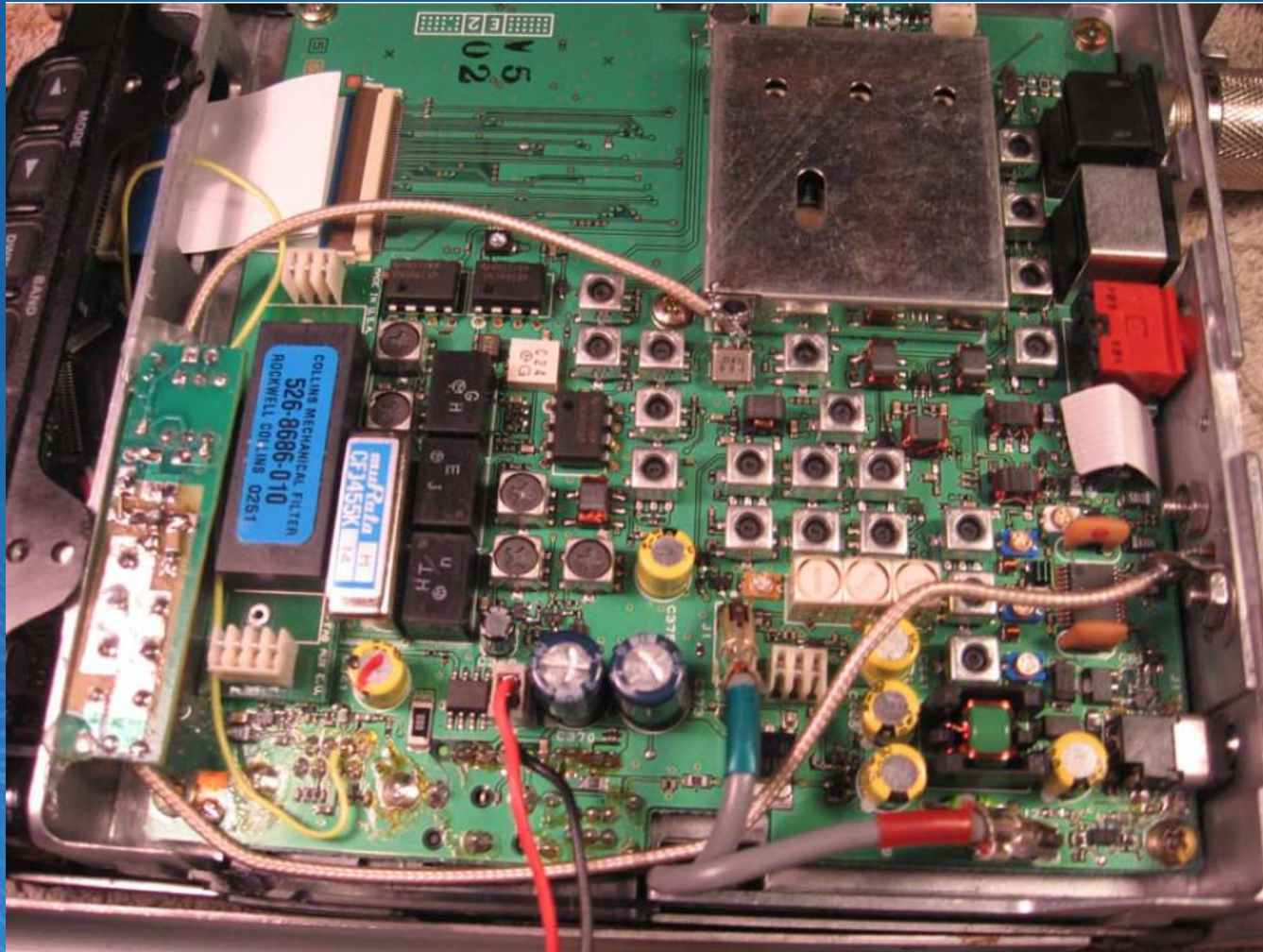
***Mike shoe horns PCB into a unit with CW filter***




Apr-15

Low Cost Panadapter

# What others have done...

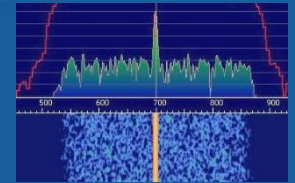


## G4HUP PAT (Panoramic Adapter Tap)

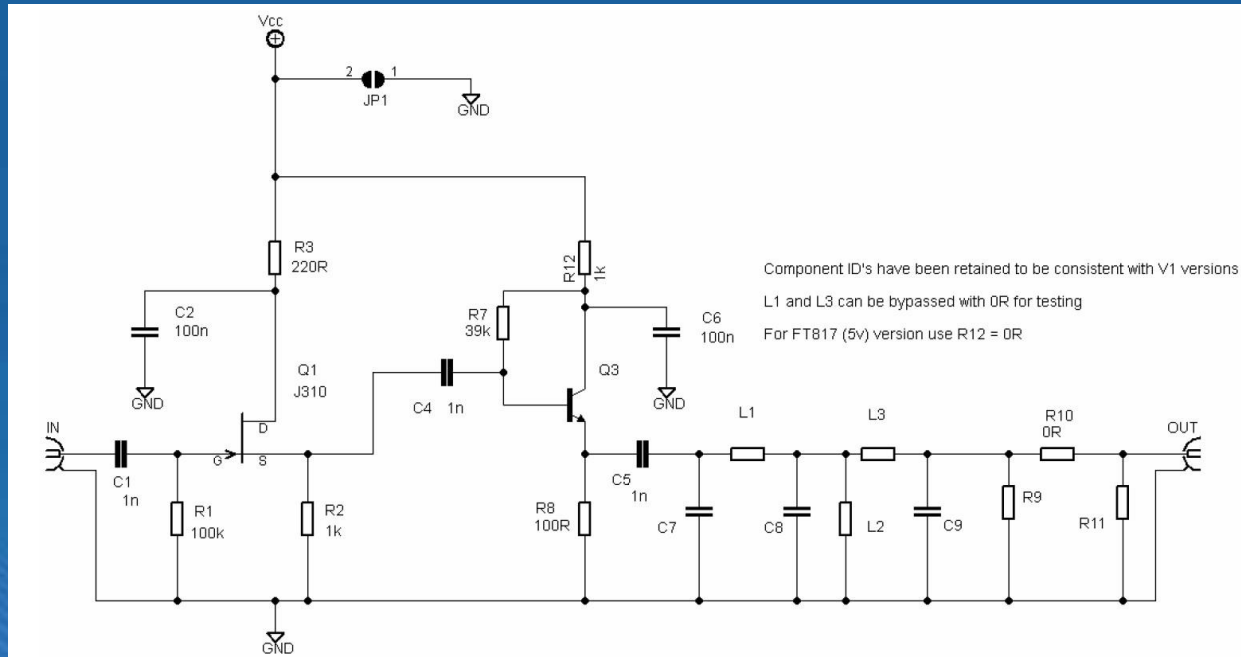


- Two voltage followers, low pass filter & attenuator
- Filter components can be chosen for IF's from 10-70MHz
- Power supply range is 5 to 13V.



# ***What others have done...***

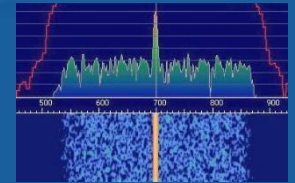


## ***G4HUP PAT in a Yaesu FT817***

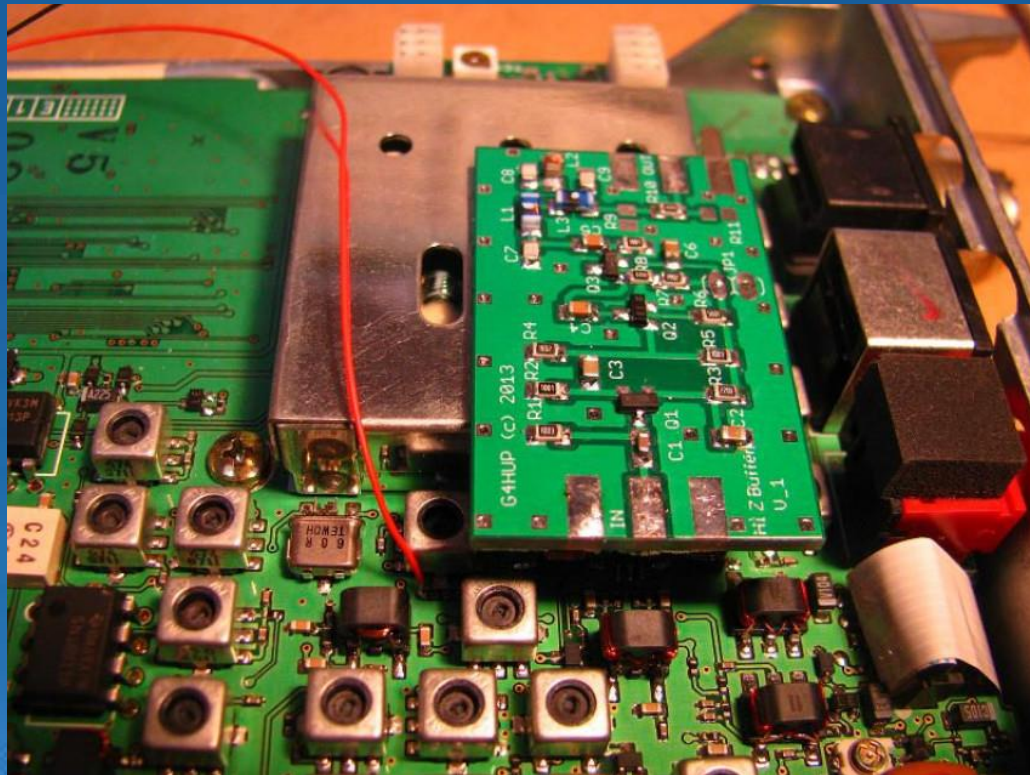

- PAT on the PLL shield held in place with double sided tape
- PCB layout – generous space for beginner SMT assembly

# ***Design Objectives***

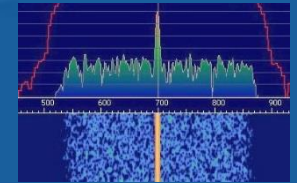


## ***1<sup>st</sup> IF interface design goals***


- Low current consumption. Target about 5mA
- No impact on receiver sensitivity
- Small size so that it could be installed into most radios
- Versatile
  - Can be used with a variety of supply voltages from 5 to 14V
  - Usable with any radio 1<sup>st</sup> IF's in the 50-70 MHz range
- IF output must remain stable with any dongle load or open circuit
- Low cost



# ***Interface Block diagram***

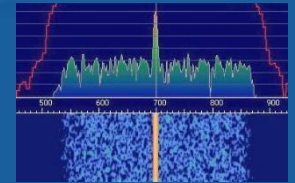




## ***Three Stage Solution***

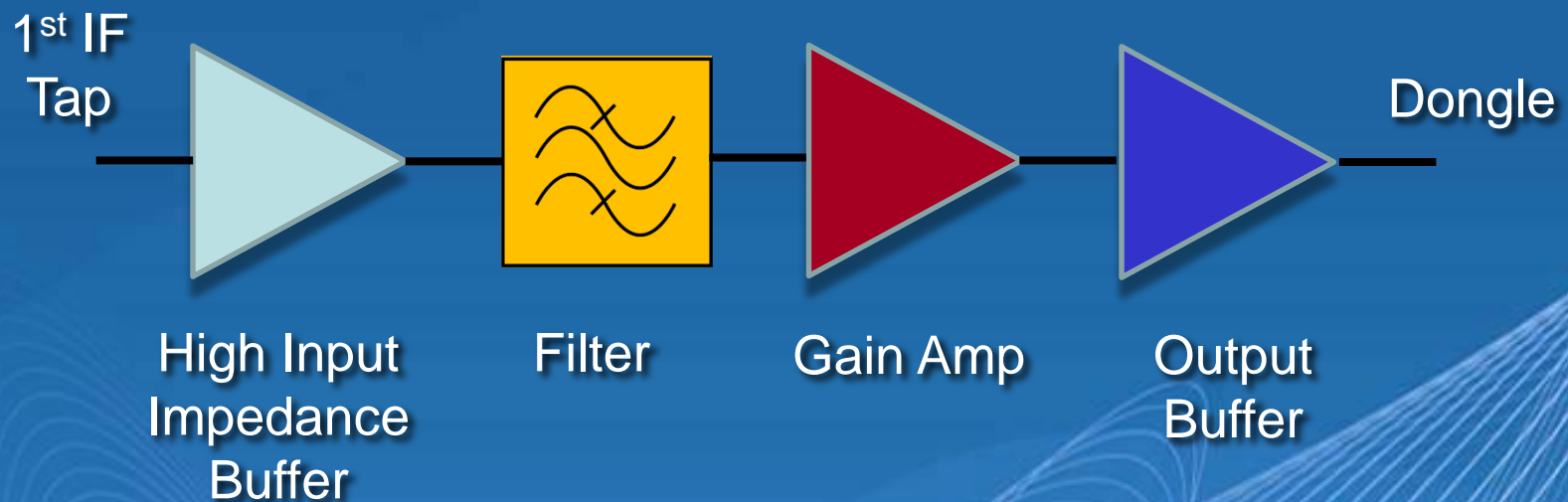


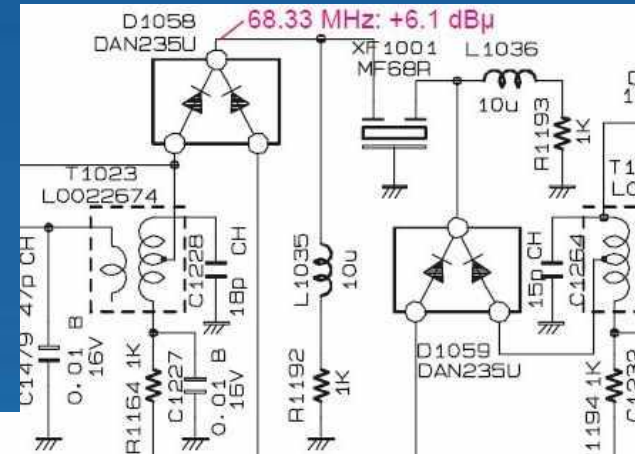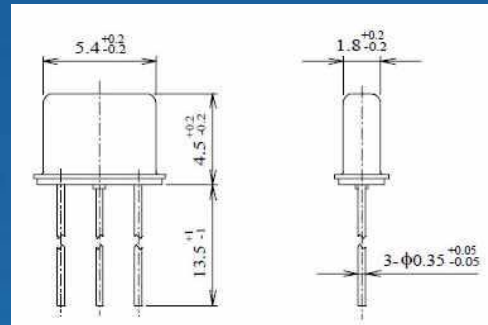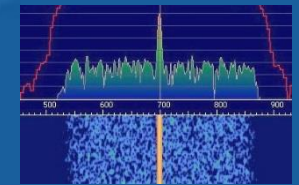
# High Z Input Buffer

Why?... The IF tap point is typically just ahead of a crystal filter that has a high Z<sub>in</sub>




## ■標準仕様 | Standard Shi yoshikidai

名称	Name	MF40M2(2pole)	MF45U9(2pole)	MF68Q(2pole)
公称周波数	Nominal Frequency		45.000 (MHz)	68.330 (MHz)
通過帯域幅	Bands domain via the web		3.0 (dB): ±15.0kHz min.	3.0 (dB): ±6.00kHz min.
減衰帯域幅	Bands domain via amplidude damping		15.0 (dB): ±60.0kHz max.	15.0 (dB): ±25.0kHz max.
リップル	Ripple	1.0 max. (dB)	1.0 max. (dB)	0.5 max. (dB)
挿入損失	Insertion Loss	2.5 max. (dB)	3.0 max. (dB)	2.5 max. (dB)
保証減衰量	Ensure that the amount of damping		65min. (dB) @ f <sub>0</sub> -910kHz	65min. (dB) @ f <sub>0</sub> -910kHz
入出力インピーダンス	Input & Output Impedance		1.2k(Ω)// 0.0(pF)	480(Ω)// 4.0(pF)

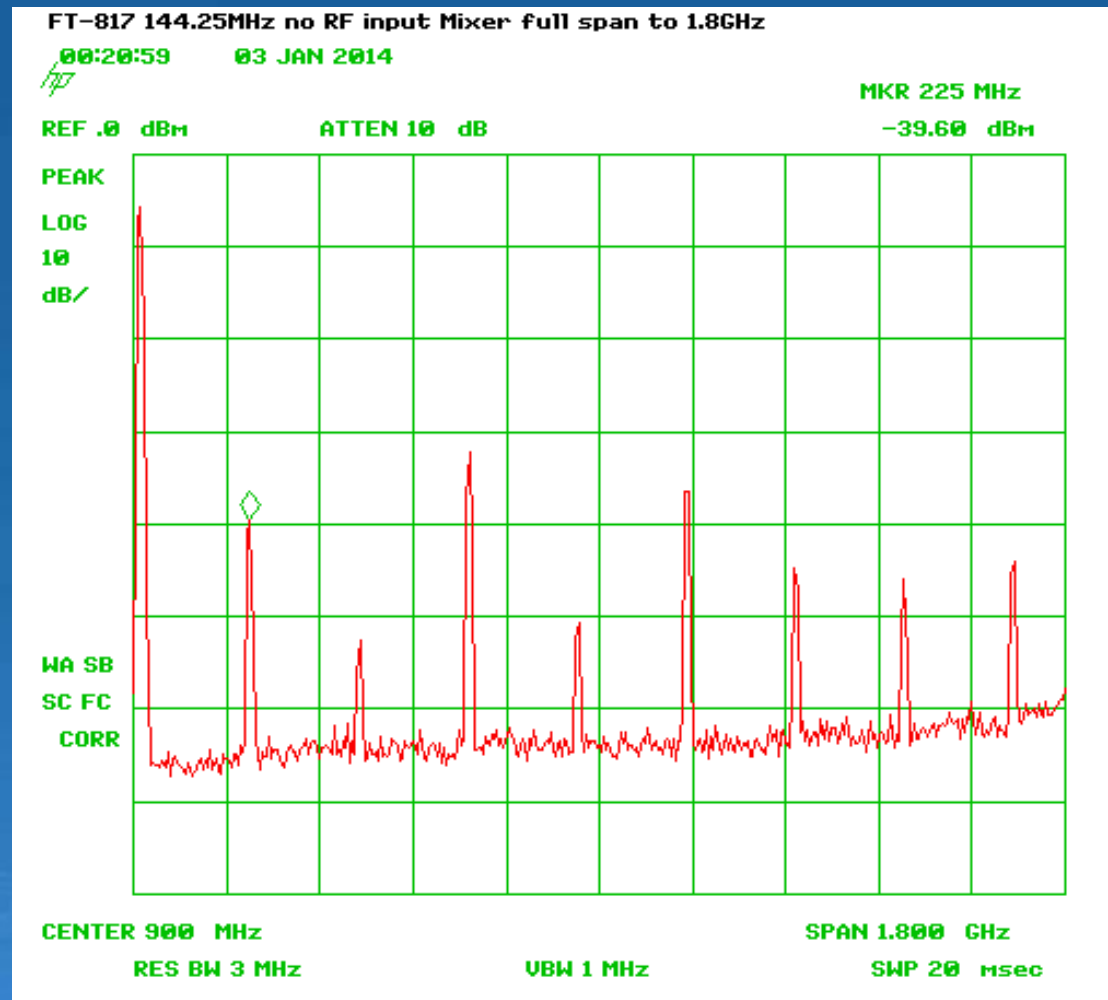
# Filter

Why?...The 1<sup>st</sup> IF is not quiet !

This spectrum analyzer snapshot shows the FT817 IF when set to the 2 meter band with NO RF signal present.




# Filter (cont'd)

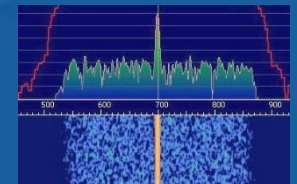


1<sup>st</sup> IF @ 2m with -50dBm CW signal at 144.25MHz

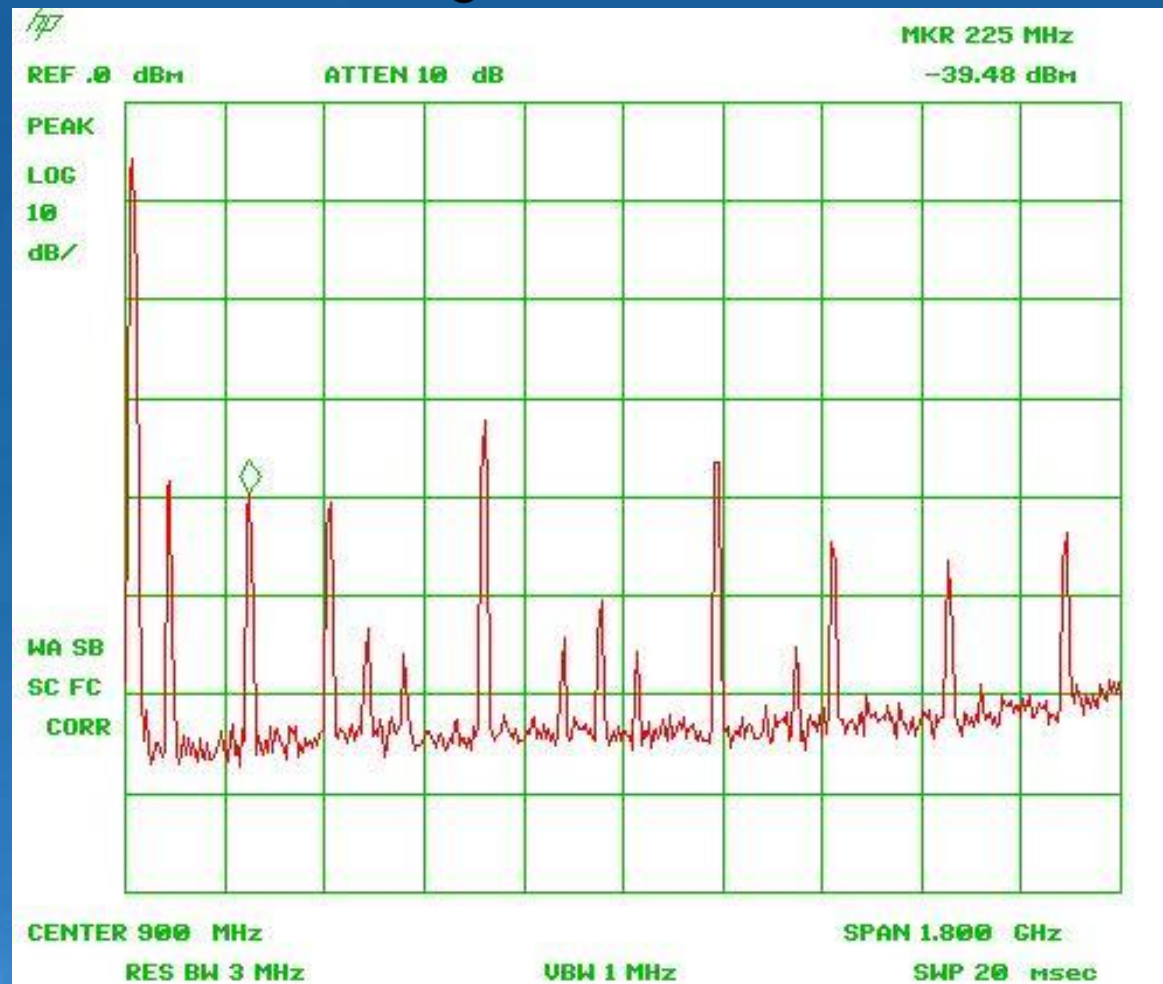With a moderately large input signal there are several carriers that have levels close to or higher than the intended RF signal.







# Filter (cont'd)

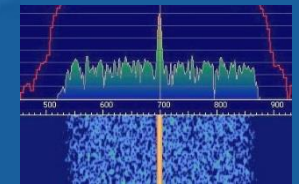

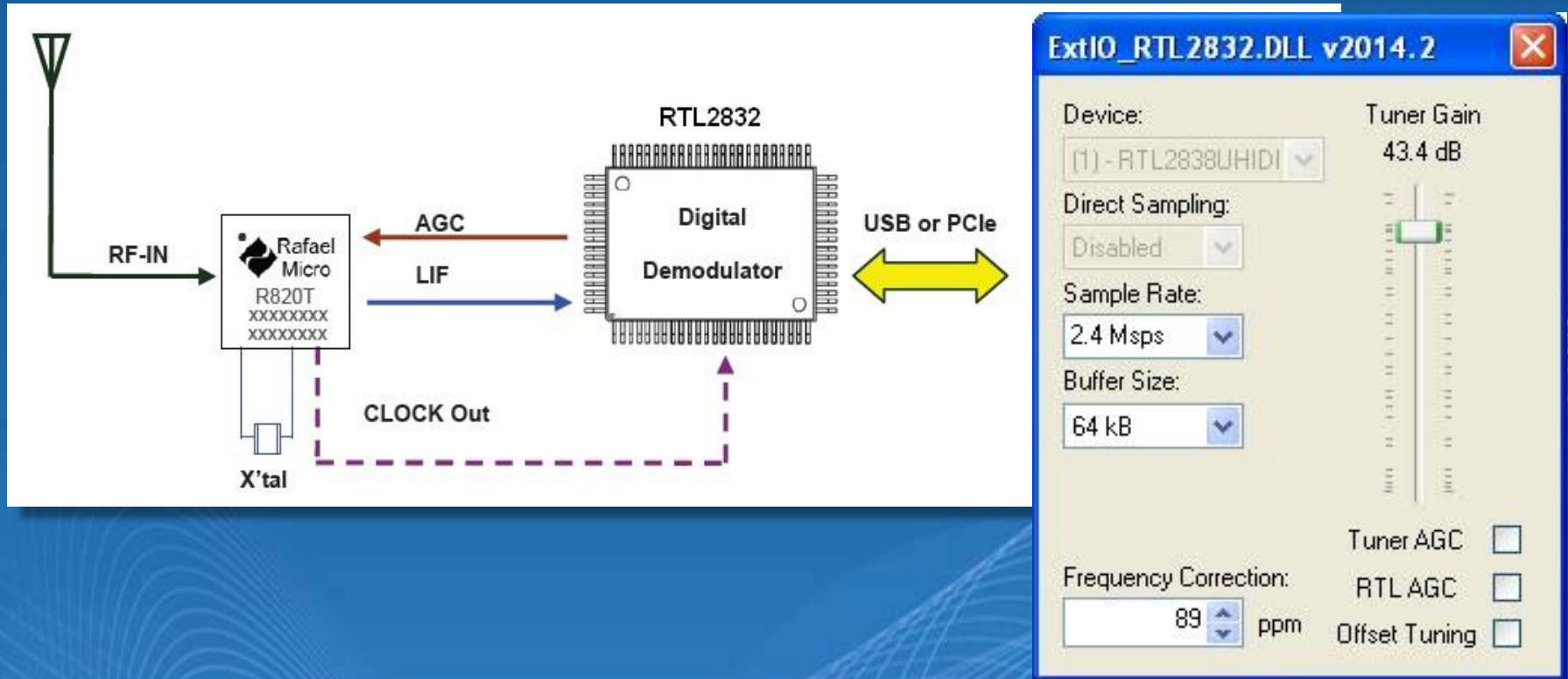Impact of large out of band signals on receive sensitivity




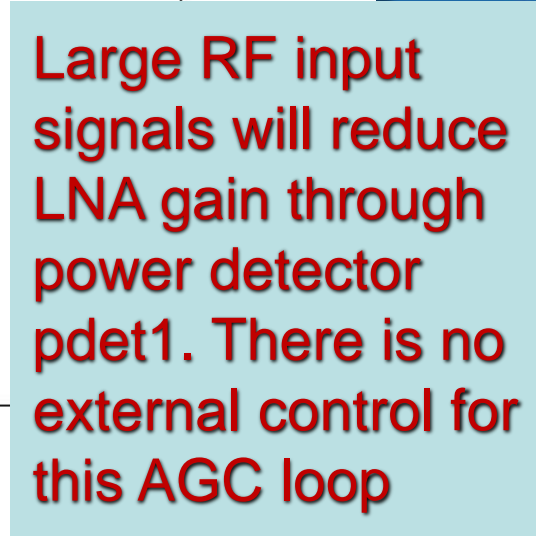There are typically three AGC loops in most SDR dongles  
Two can be selectively controlled by most applications






# Filter (cont'd)

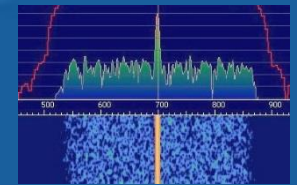


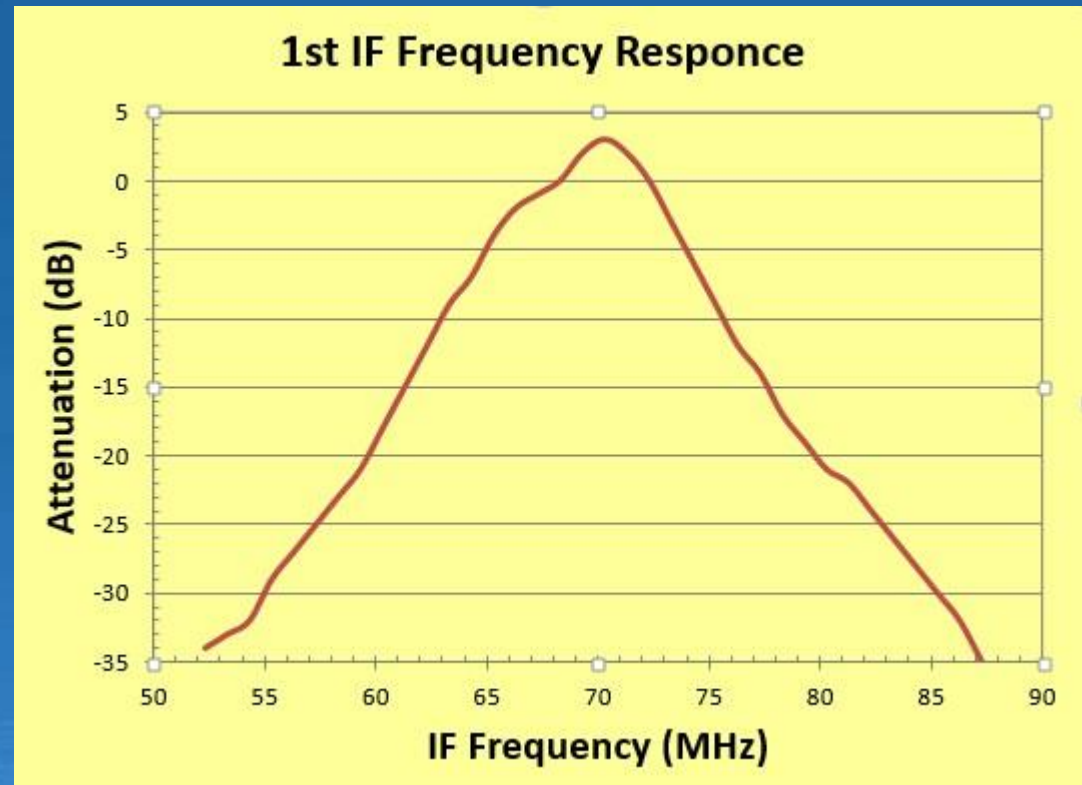***Large unwanted signals within the dongle's passband will reduce receiver sensitivity***

NooElec RT820  
passband is  
WIDE...about 25-  
1750MHz.  
Transceiver's first  
IF's usually have  
some a filtering to  
the RF input.  
The graph to the  
right shows FT817  
normalized IF gain



# ***Filter (cont'd)***

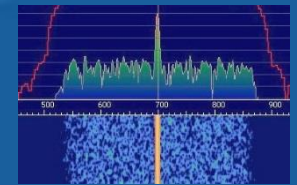


## ***Large signals within the dongle's passband will reduce overall sensitivity***

- While the transceiver offers some filtering of RF from the antenna to the 1<sup>st</sup> IF there are still a lot of strong carriers present on the radio's 1<sup>st</sup> IF.
- Large constant carriers present in the IF need to be attenuated to prevent the tuner chip LNA gain being reduced by the power detector
- Gain reductions caused by AGC power detector feedback can often be seen as a level shift in the displayed noise baseline




# ***Filter (cont'd)***

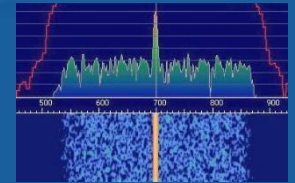

## ***Filter Criteria***

- Small footprint
- Moderate bandwidth – around 20 MHz keeps filter order manageable in small size
- Insertion loss less than conversion gain 3 - 4dB max.
- Center frequency IF 68.33 or a design that can be easily modified to suit IF's from 50 to 70 MHz.

# How much gain?

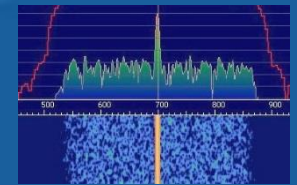

## How much gain is needed from the panadapter interface to optimize overall performance?

- Well not a lot really
- There is conversion gain from the RF input to the 1<sup>st</sup> IF


### FT817 Conversion Gain vs Frequency

Frequency (MHz)	1.8	3.6	14.1	28.3	50.3	144	430
Conversion Gain (dB)	5.1	3.2	4.9	4.6	12.5	10.9	11.4

- And the SDR dongles are decent receivers. Measurement for 12dB SINAD...
  - FT817 at 50MHz CWNarrow using the 500Hz CW filter was -131dB
  - NooElec RT820 using SDR# at 68.33MHz CW with 300Hz bandwidth was -133dBm




# ***How much gain?***

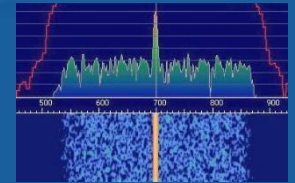

## ***Additional gain won't improve sensitivity***

- There is enough gain in the transceiver & dongle without additional gain in the panadapter interface
- Sensitivity is determined by the receiver's front end noise figure & gain. It should be noted that losses through the interface filter if greater than the conversion gain will degrade the sensitivity if the RF input signal is at the receiver's noise threshold.
- Significant interface gain will simply boost signal levels and could result in additional distortion unless the interface is extremely linear at higher signal levels.
- Enough gain to overcome filter losses (1 to 2dB) plus a small bit 6dB or so would be good objective.

# ***Output Driver***

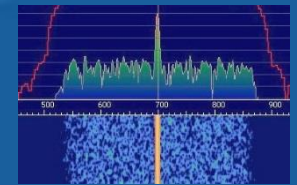



## ***What's needed at the panadapter interface output to a dongle?***

- Should be able to drive the dongle without impacting the interface's gain or filter frequency response.
- Must be stable driving an open circuit as the dongle may not always be attached
- Emitter follower buffer isolates the amplifier stage from the interface's output
- NooElec dongle impedance at the IF frequency looks quite reasonable as the next slide shows.




# NooElec RT820 Dongle

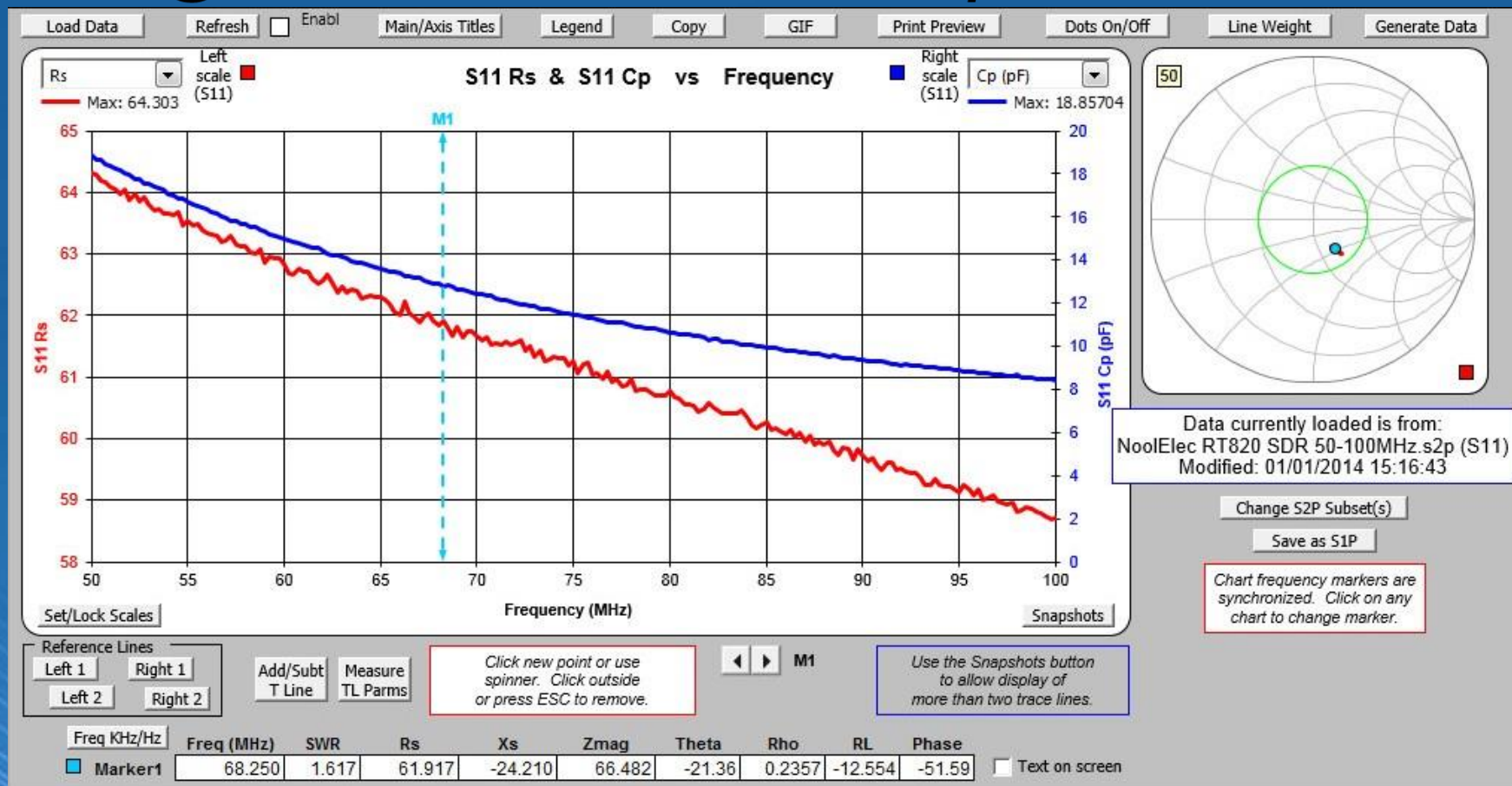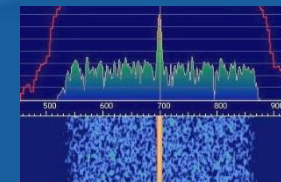**S11 @ 68.3MHz Rs=68ohms CP=13pF VSWR=1.6**




# Solution Summary

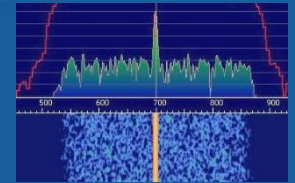
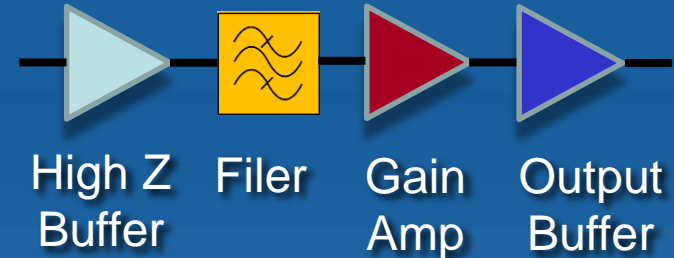
## Input Buffer

- $Z_{in} > 1k \text{ Ohm}$  so it won't load the IF crystal filter
- Output drives 50 ohm  $Z_{in}$  of filter



## Filter


- Compact & fairly simple - 20 MHz or so bandwidth 3<sup>rd</sup> or 4<sup>th</sup> order
- Insertion loss less than conversion gain target < 3 dB
- Center frequency design alterable for between 50 & 70 MHz

## Gain Block

- 6-10 dB gain (4 to 8 dB overall after filter loss)
- $Z_{in}$  matched to filter - 50 Ohms




# ***Solution Summary (cont'd)***

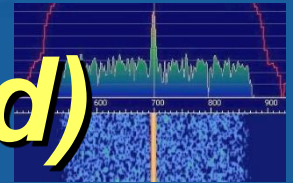
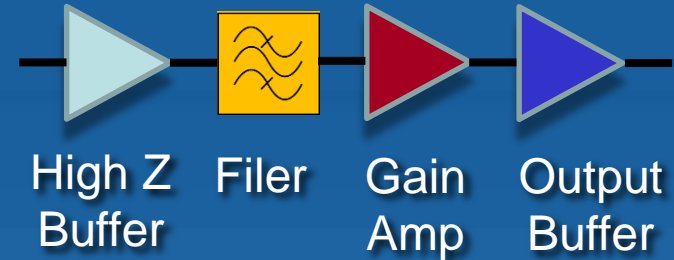
## ***Output Buffer***


- Unconditionally stable working into an open circuit
- Able to drive most (all) dongles



## ***Other Criteria***


- Small PCB size to fit into most rigs
- Low current consumption – 5 mA target

# Design...start with the filter

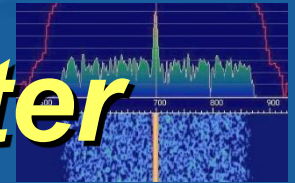
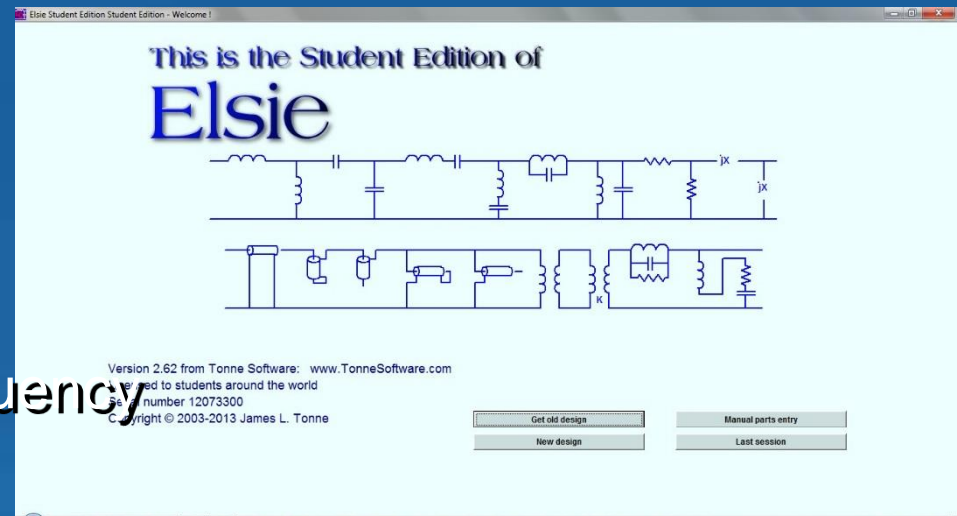
## Elsie Filter Design

- Explore Filter topology & family
- Explore filter properties
  - bandwidth - center frequency
  - filter order - Z in & out
- Access impact of other parameters
  - capacitor and inductor Q




## Filter Topology Chosen


- Nodal inductor coupled bandpass
  - A bit more complex but has steeper high frequency cut-off



# Filter Quest

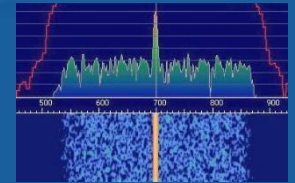

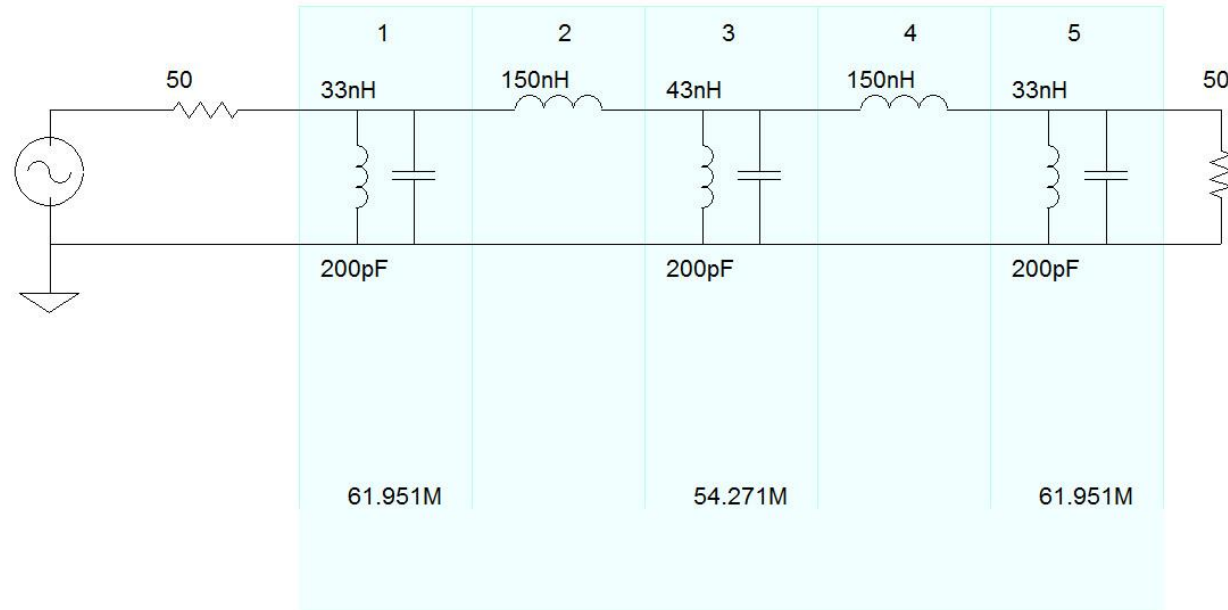**Choose the filter topology & key parameters**




Design data:  
Bandwidth: 10M  
Center: 67M  
Family: Manual entry


Q values:  
Inductors: 80  
Capacitors: 300

Maximum / minimum ratios:  
Capacitors: 1  
Inductors: 4.5455

# Filter Quest

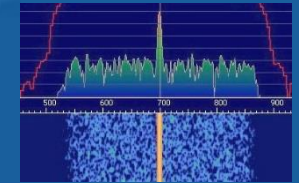


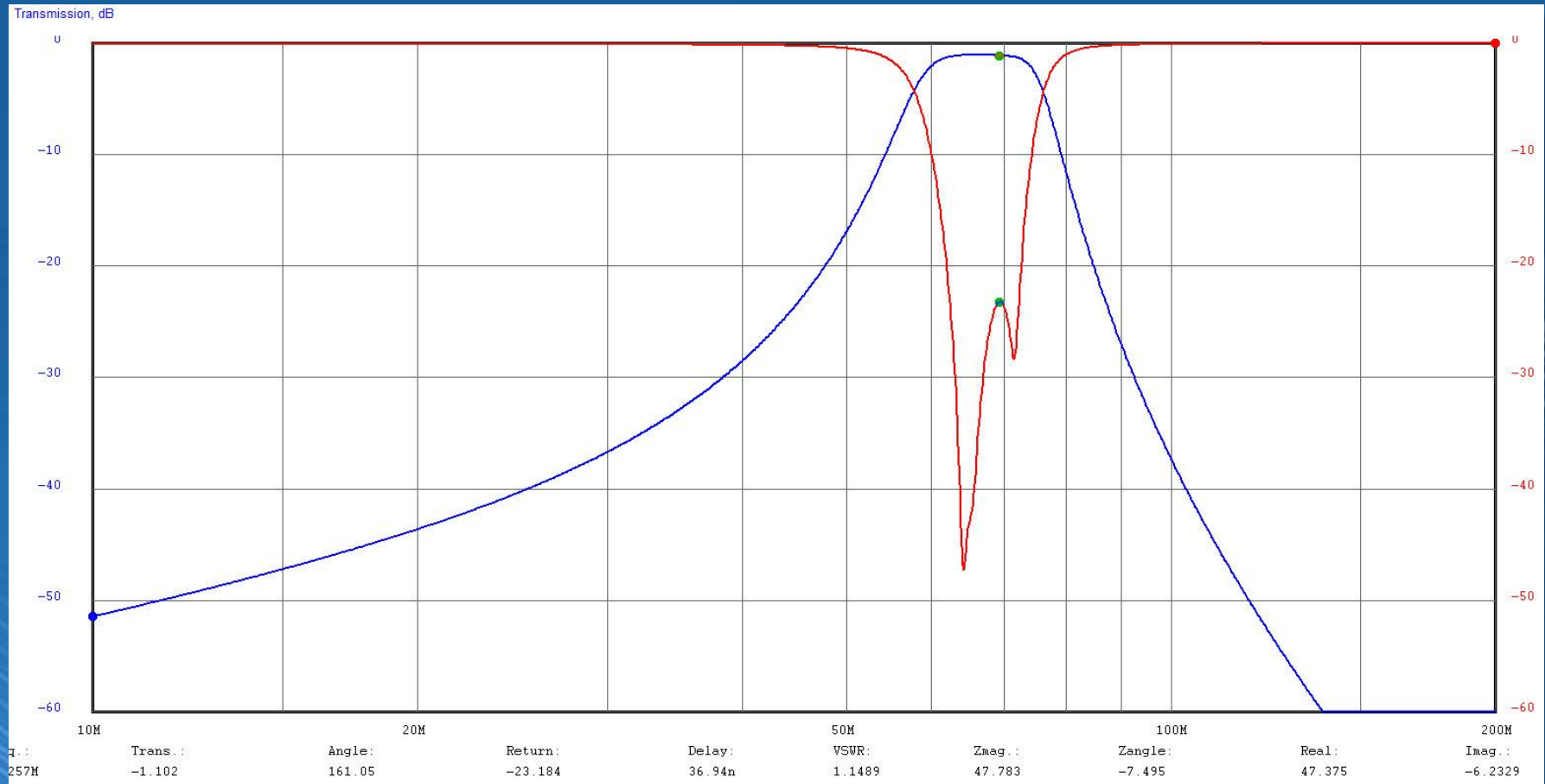- Filter S21 & return loss - plot marker at 68.33MHz







# Filter Quest

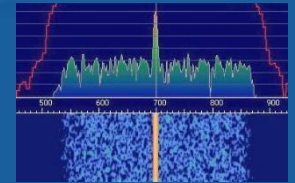


## Inductor Q

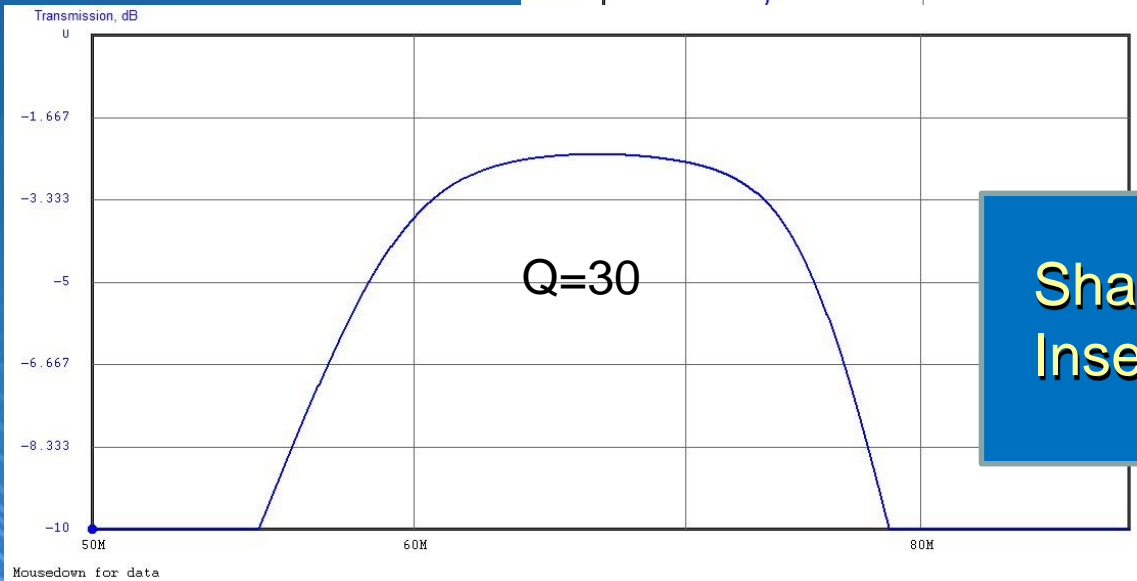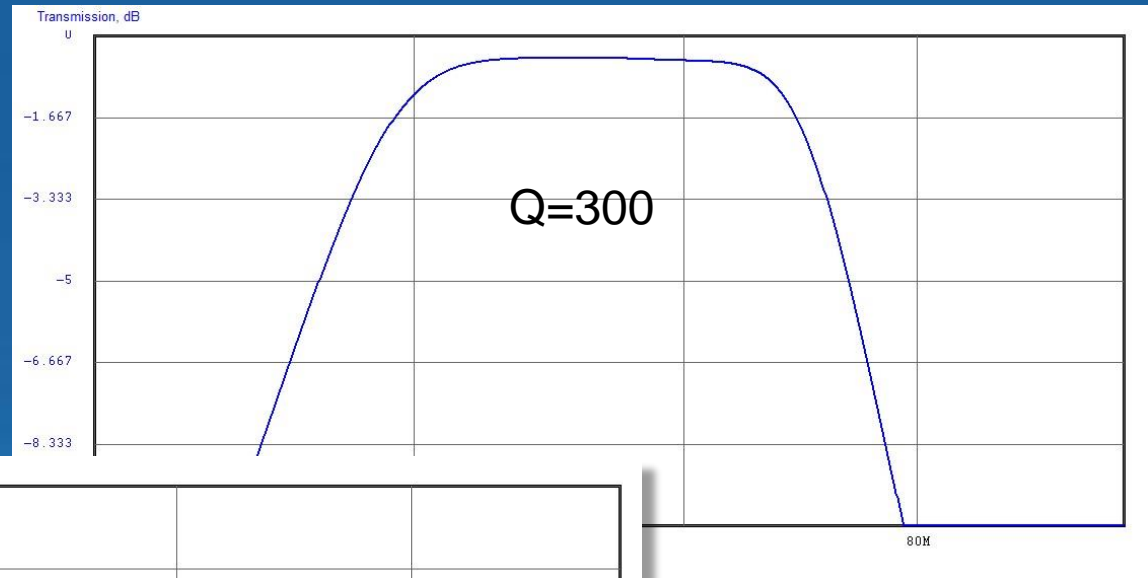


Shape factor degrades  
Insertion loss increases

# Filter Inductor Selection

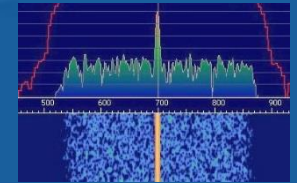

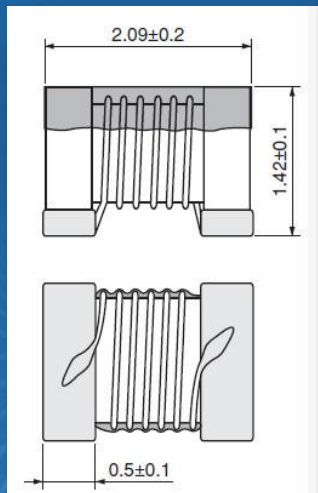
## Inductors – hard to find small parts with high Q

- Small Physical size < 3mm w & h x 6 -7 mm l
- $Q > 50$  preferably 70-100 at 70MHz.




Murata  
LQW2BA  
inductors

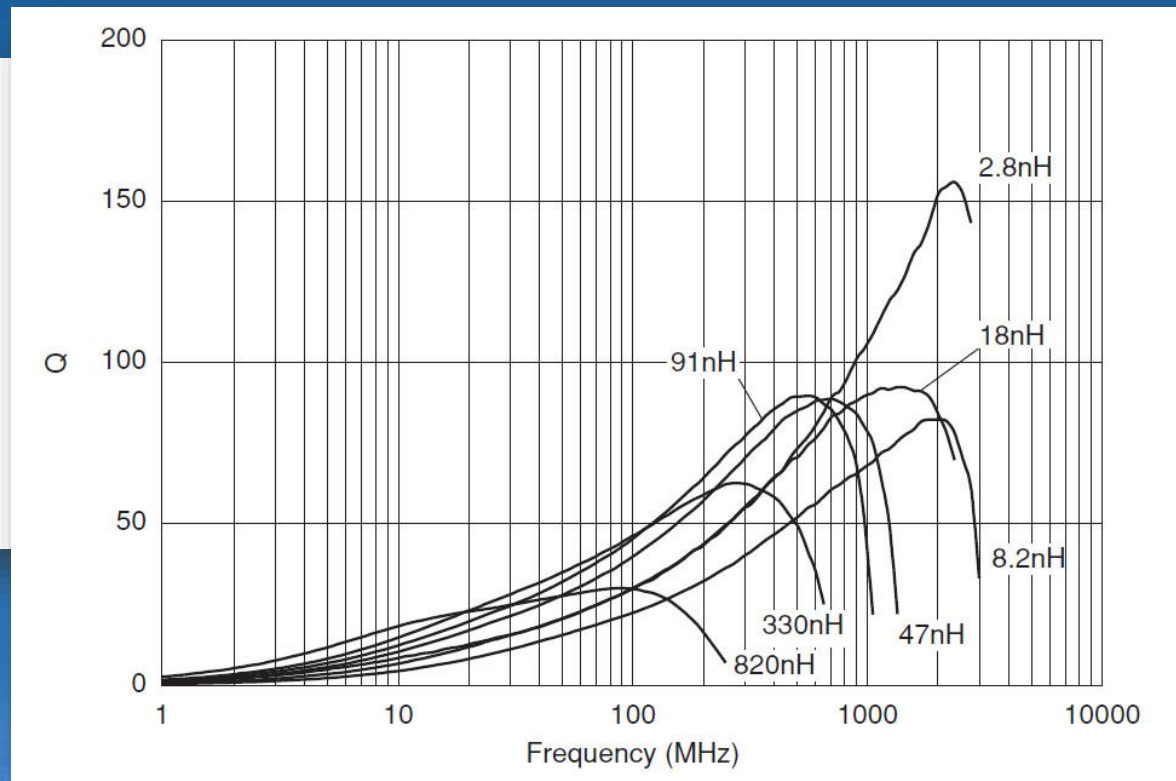




# Filter Considerations

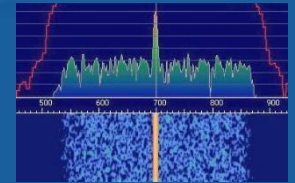



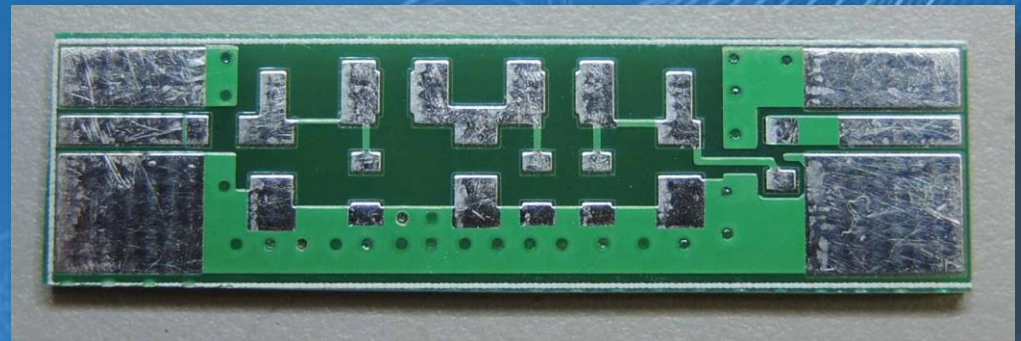
## *The criteria that simulation won't easily tell you*

- Multiple inductor placement on PC & mutual coupling
  - Space in-line inductors a minimum of 2 diameters apart
  - Place inductors orthogonal where possible
- PCB groundplane impact on filter
  - Standard practice removes the ground plane under the filter on all cu planes – how far away from filter does it need to be?
- Capacitor Q and size (0805 vs.. 0603)
- Impact of layout parasitics
- Test PCB created to evaluate performance of the filter alone




# First Filter Tests

*Didn't work out well*

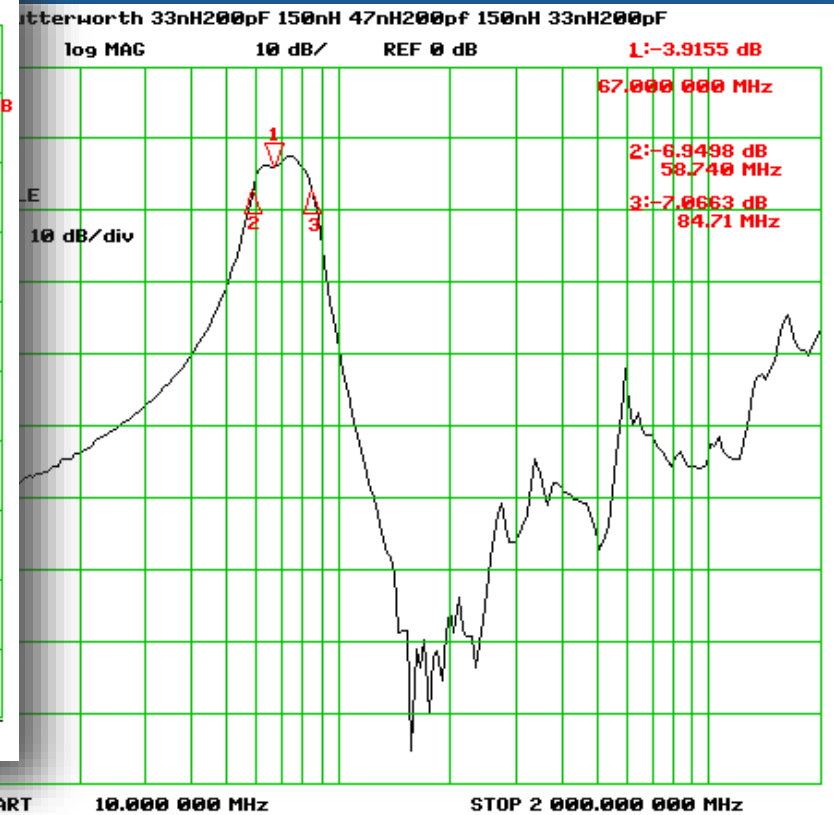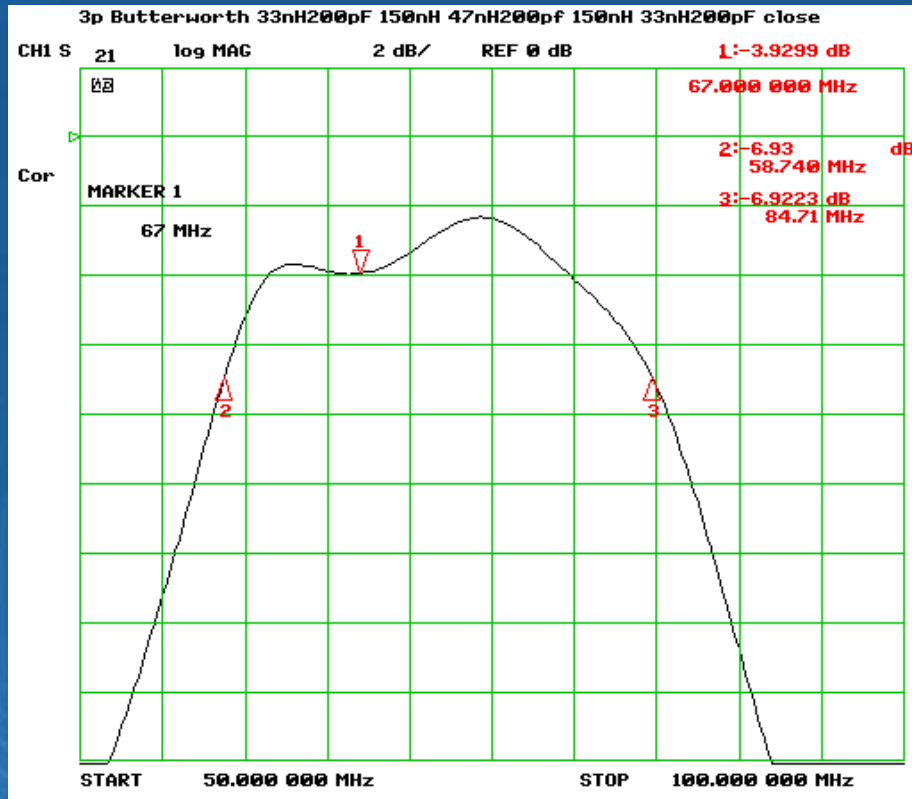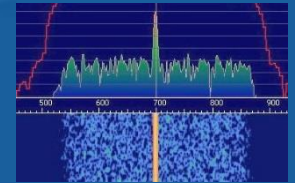





# ***First Filter Tests (cont'd)***

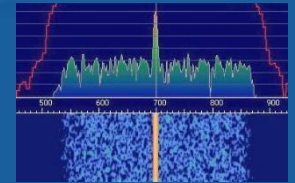

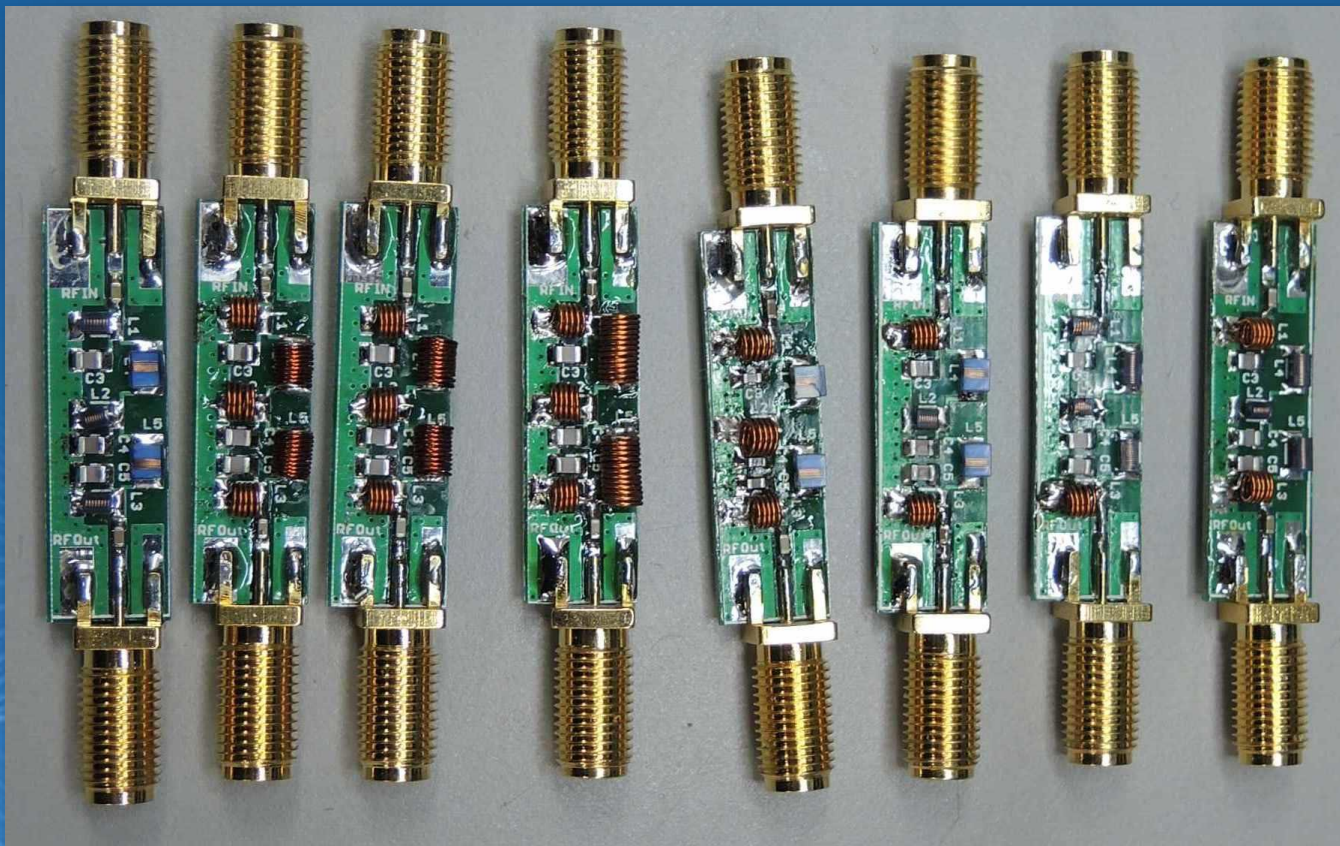***So I built more filters from different components some looked better but not all***



# Test Equipment Added

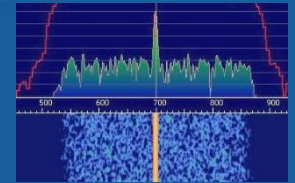


## HP 4274 /5

- Capable of measuring caps into the fF and inductors into the pH range.






# Found the Culprit

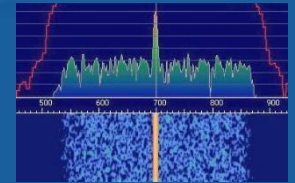



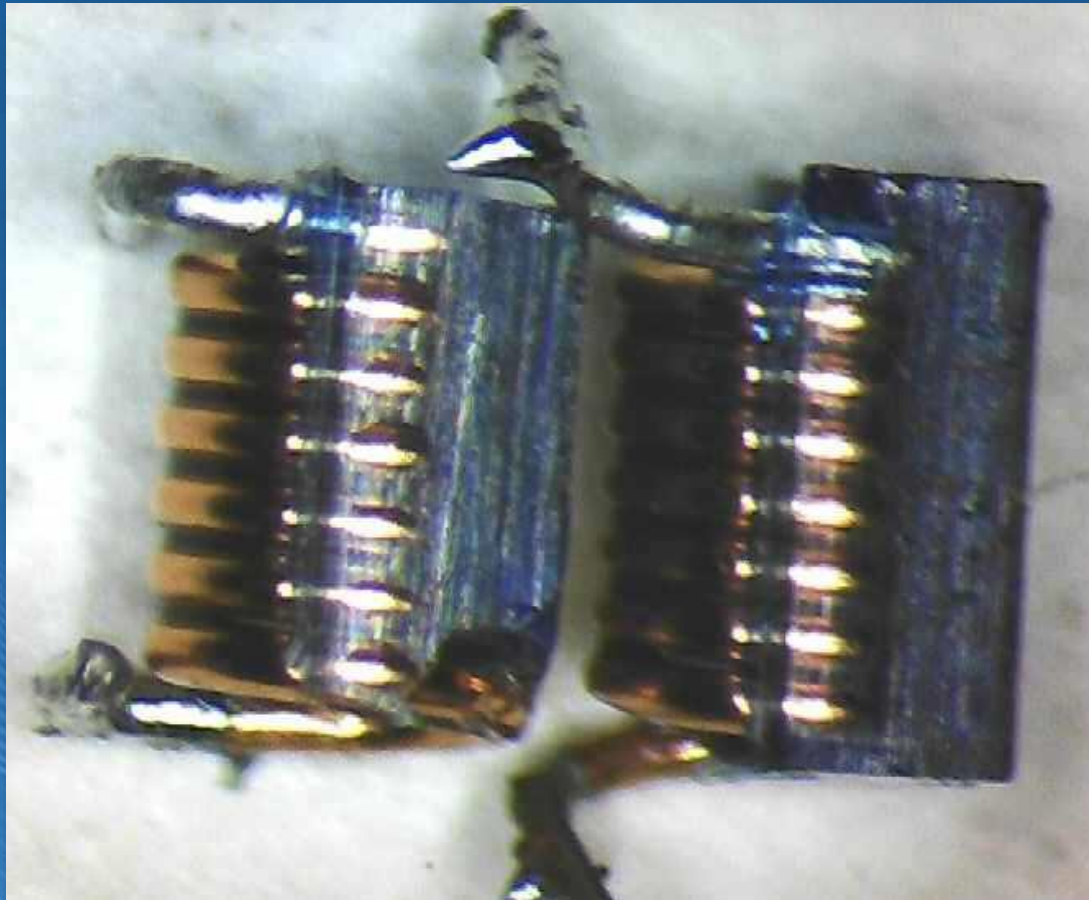
Abracon had mixed in some 22nH inductors along with 33nH parts. The inductors are the same diameter but one turn less





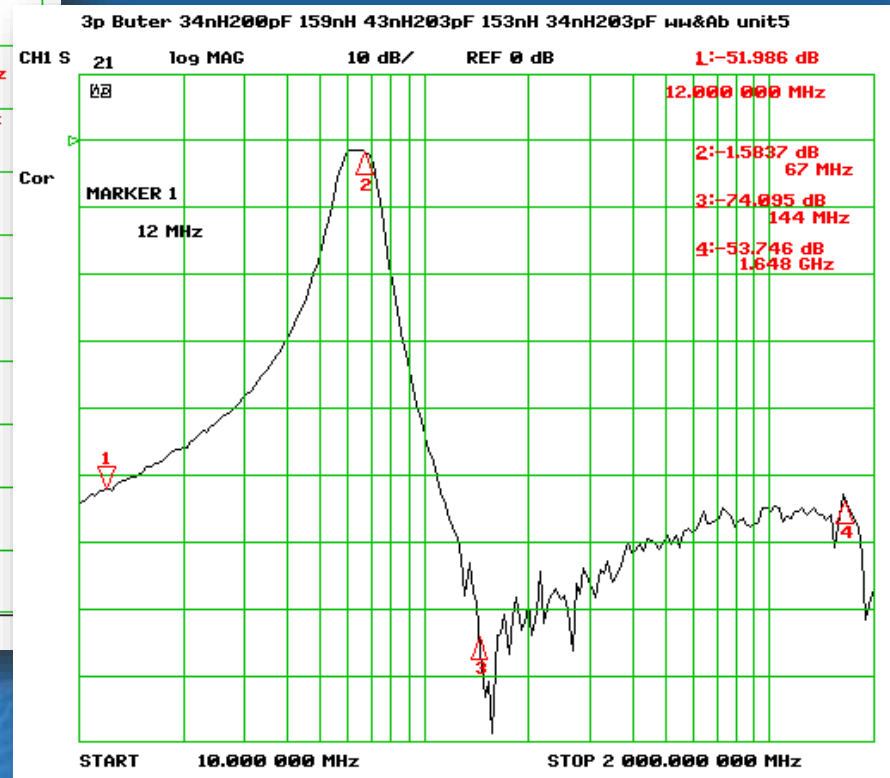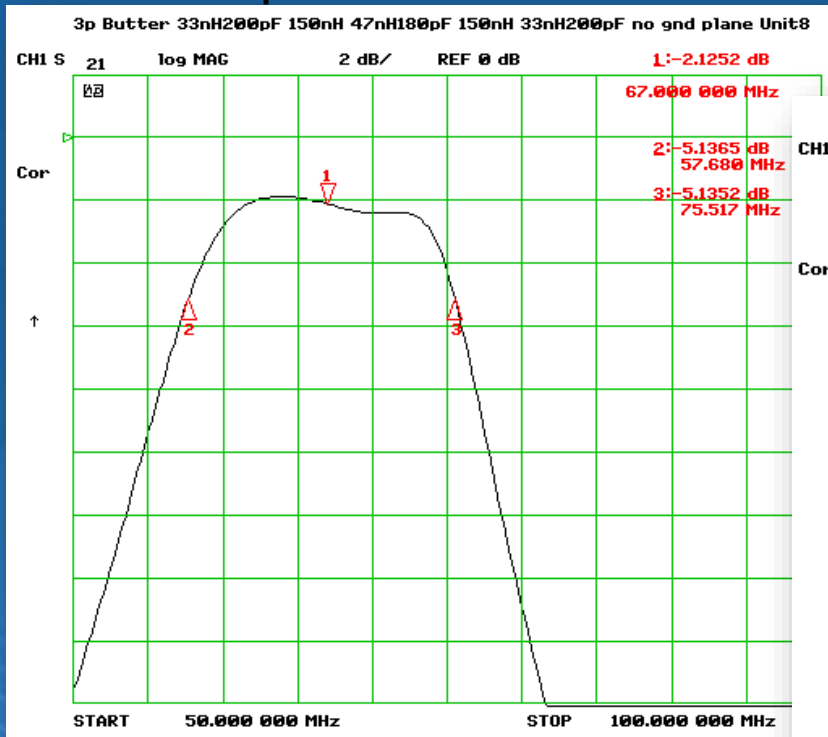
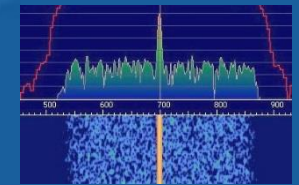
# Working filter

- Reasonable passband characteristics with standard parts
- Stop band attenuation best with full back ground plane



# Interface Schematic



V0.1a

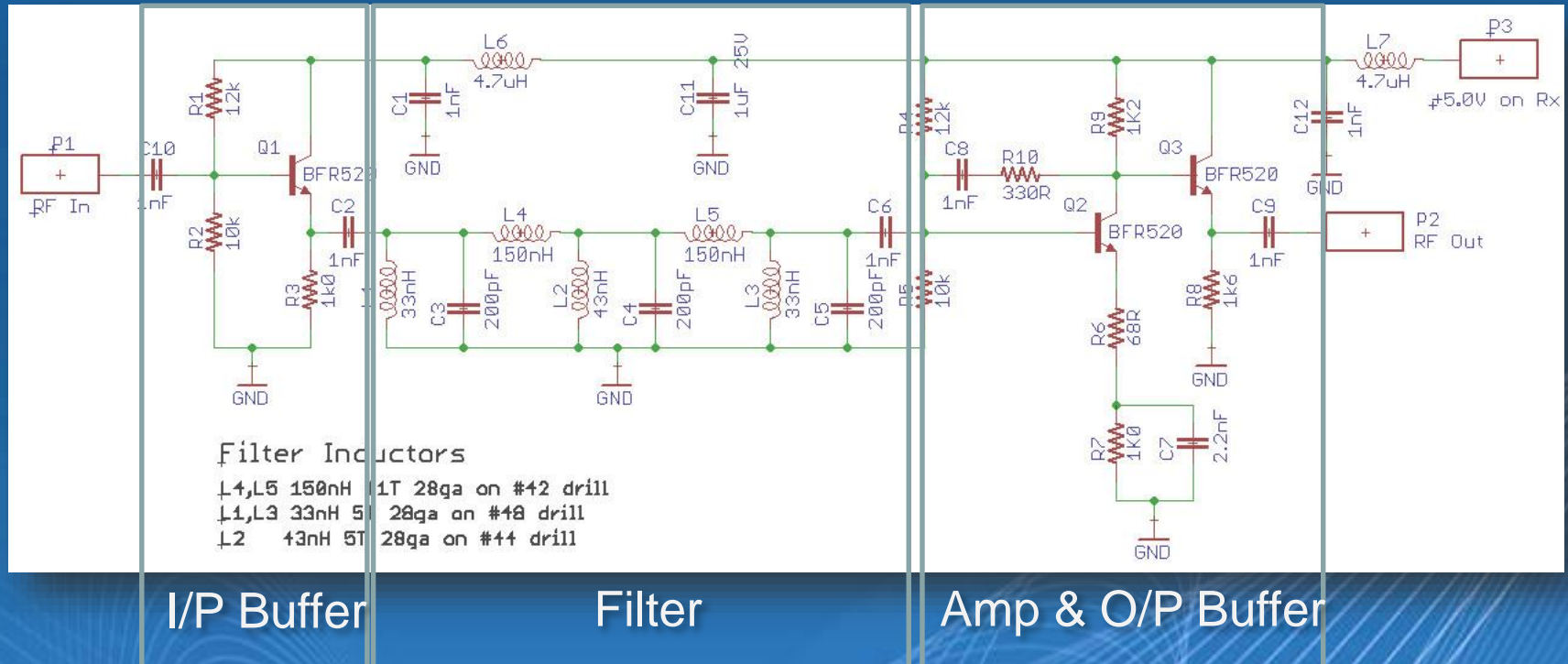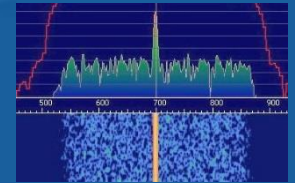

# Circuit Simulation
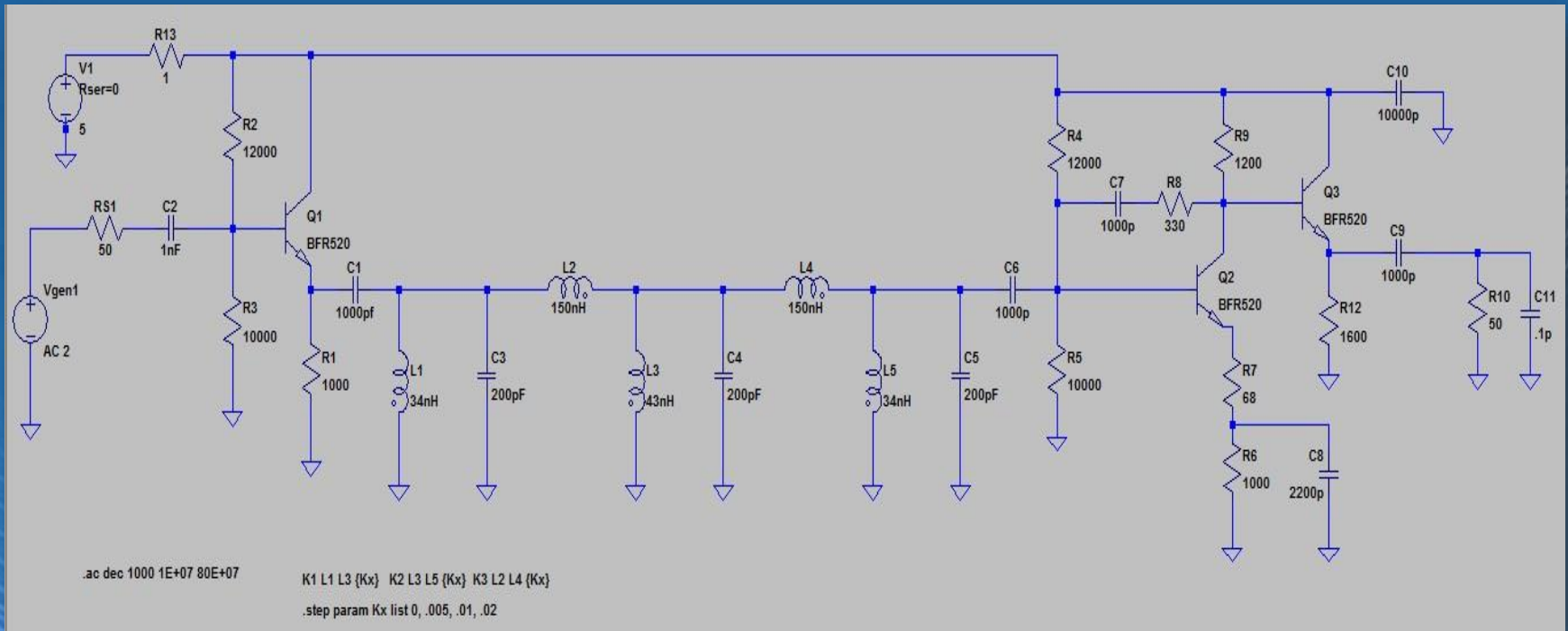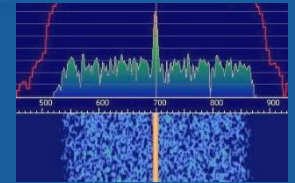
## LTSpice simulation files



- Complete circuit &
- Output amplifier + buffer






# Circuit Simulation

## LTSpice simulation results

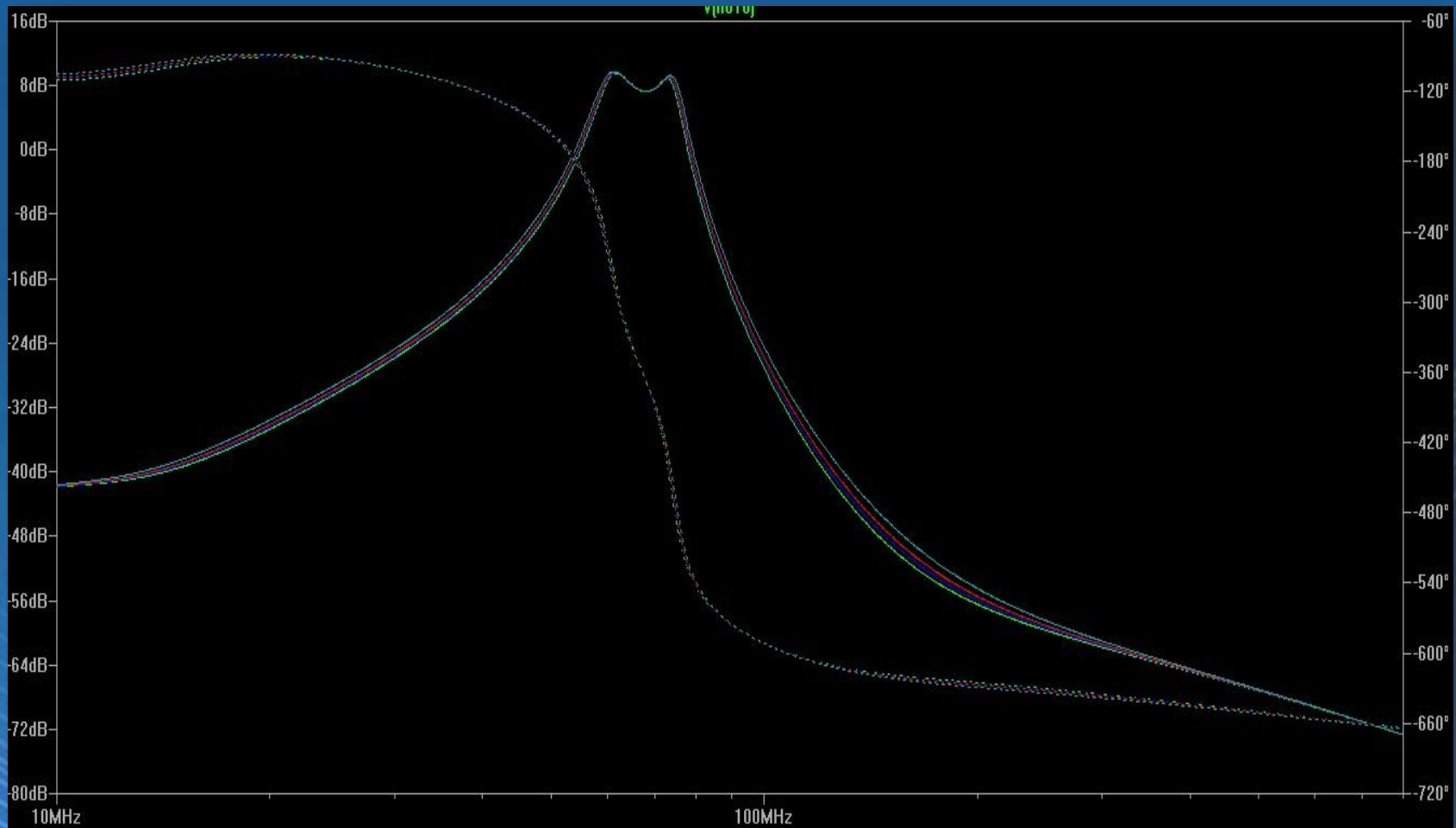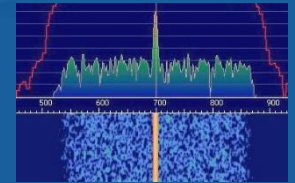

# ***PCB Layout***

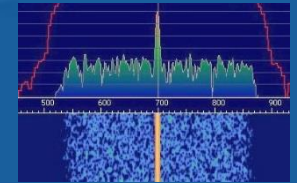

## ***Small size to fit most transceivers***

- 12mm x 40mm



## ***All components on the top side no tracks on bottom***

- Bottom is ground plane only, so PCB can be soldered to any grounded surface within the transceiver

## ***Keep-out areas allow PCB to be fitted against the PLL – Unit can in FT-817***

# PCB Layout

40 x 12mm

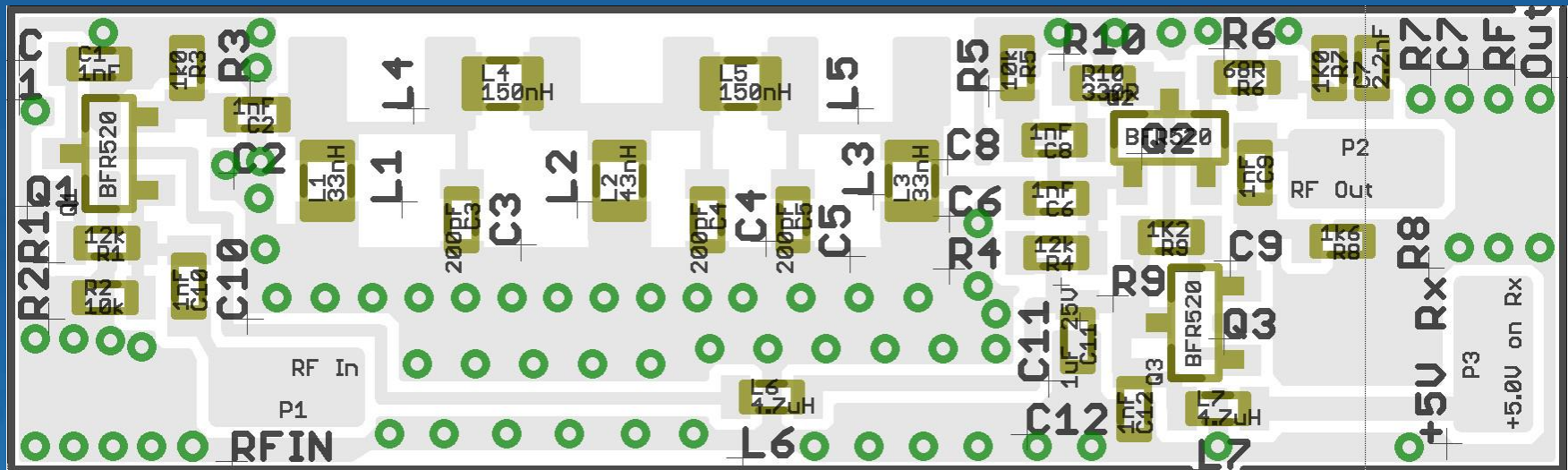
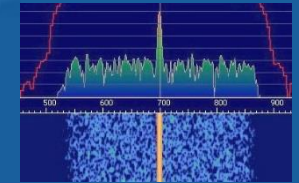


- Layout has keep-out areas that allow the board to easily fit against the side of the PLL - Unit shield in the FT-817
- All components are on the top side, bottom is ground plane




# *Assembled PCB*

*Using wire wound air core inductors*

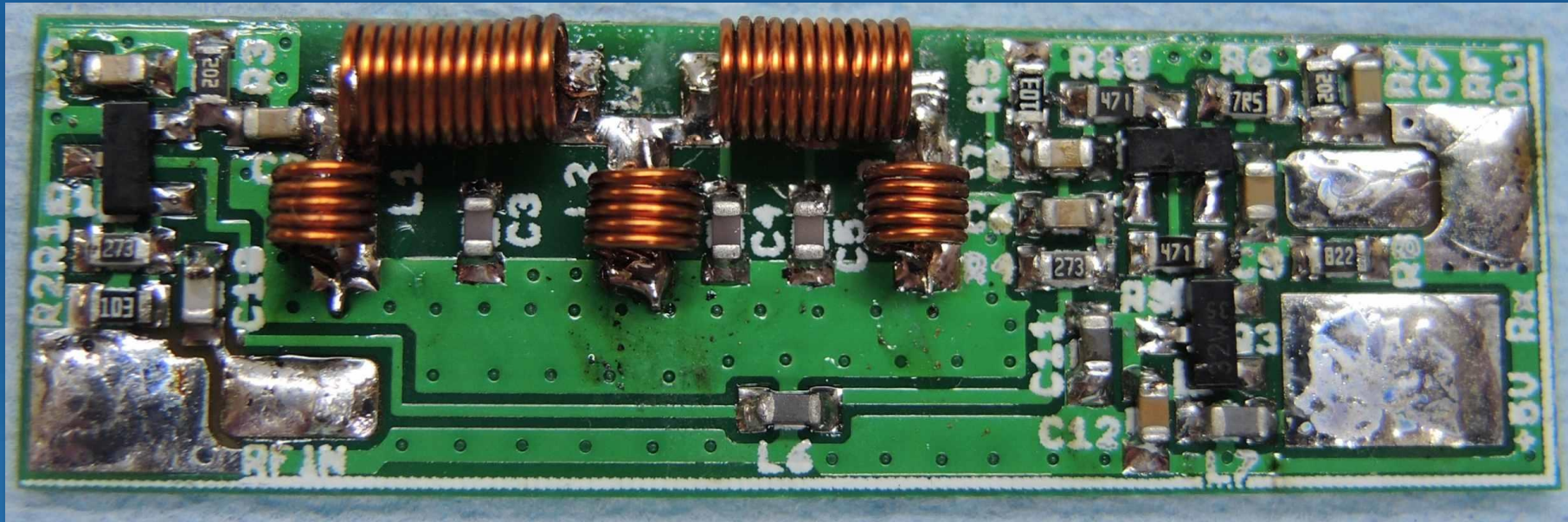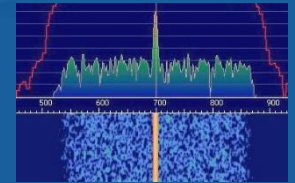




# Assembled PCB (cont'd)

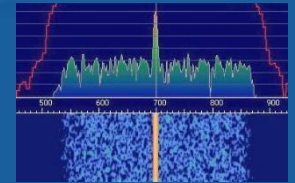

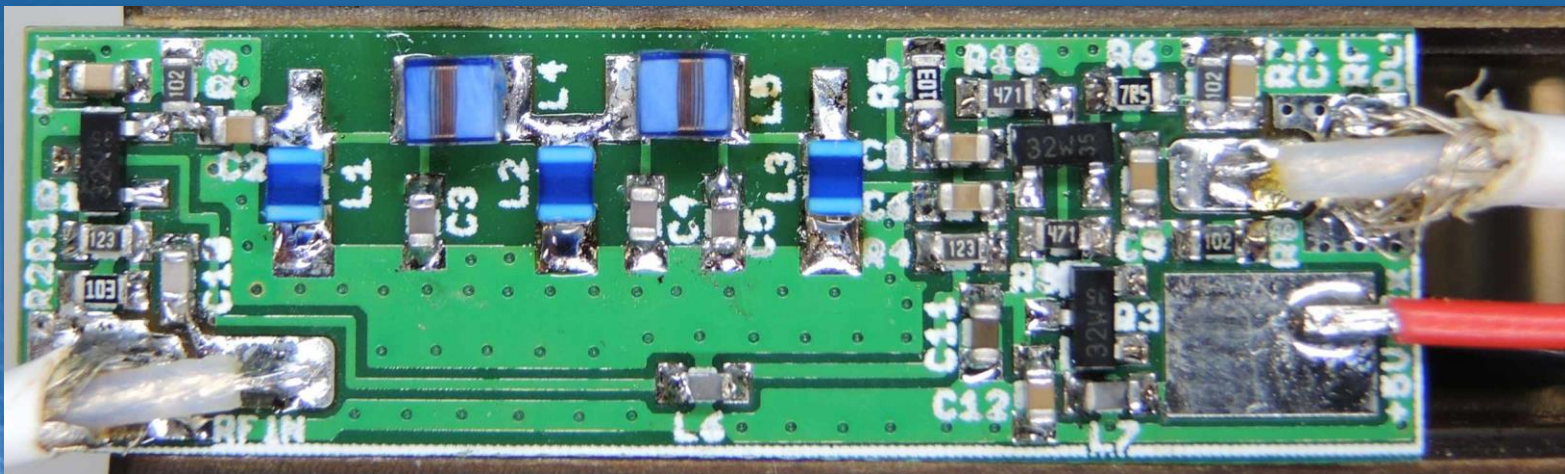
## PCB also has pads for commercial inductors



- L4 and L5 are 150nH - 1008
- L1 and L3 are 33nH - 0805
- L2 is 43nH - 0805
- These values shift the passband down slightly so that the 68.33 MHz center frequency is a bit closer to the upper edge



# Bench Performance tests

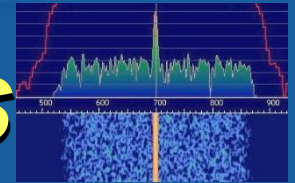

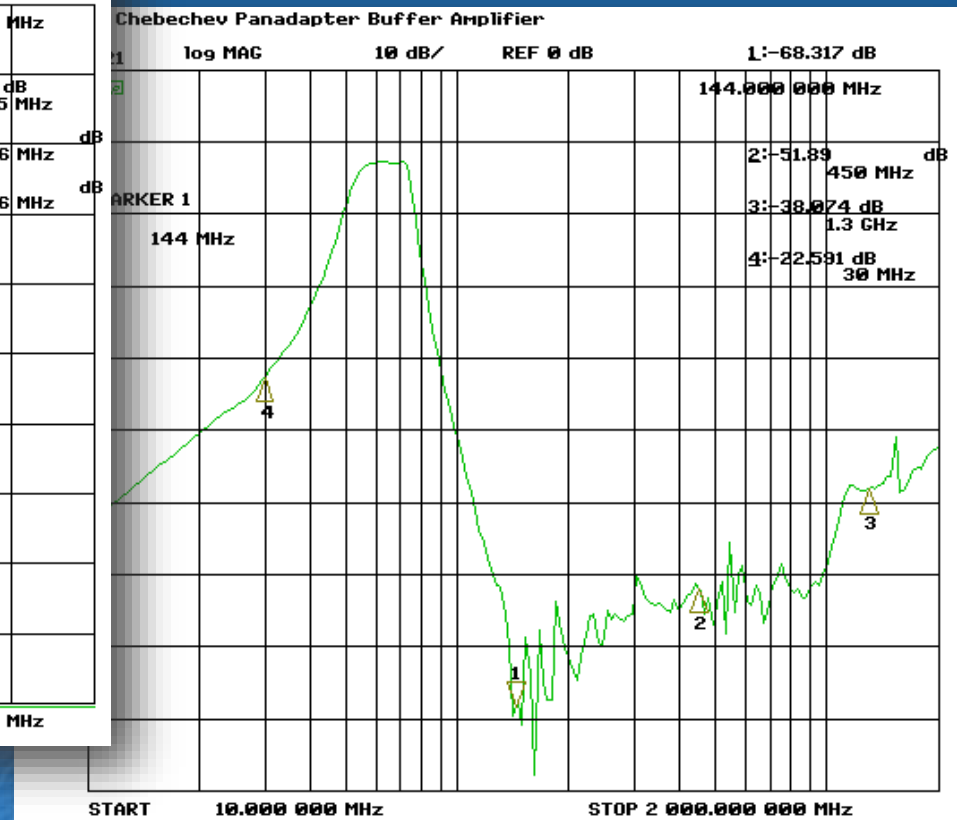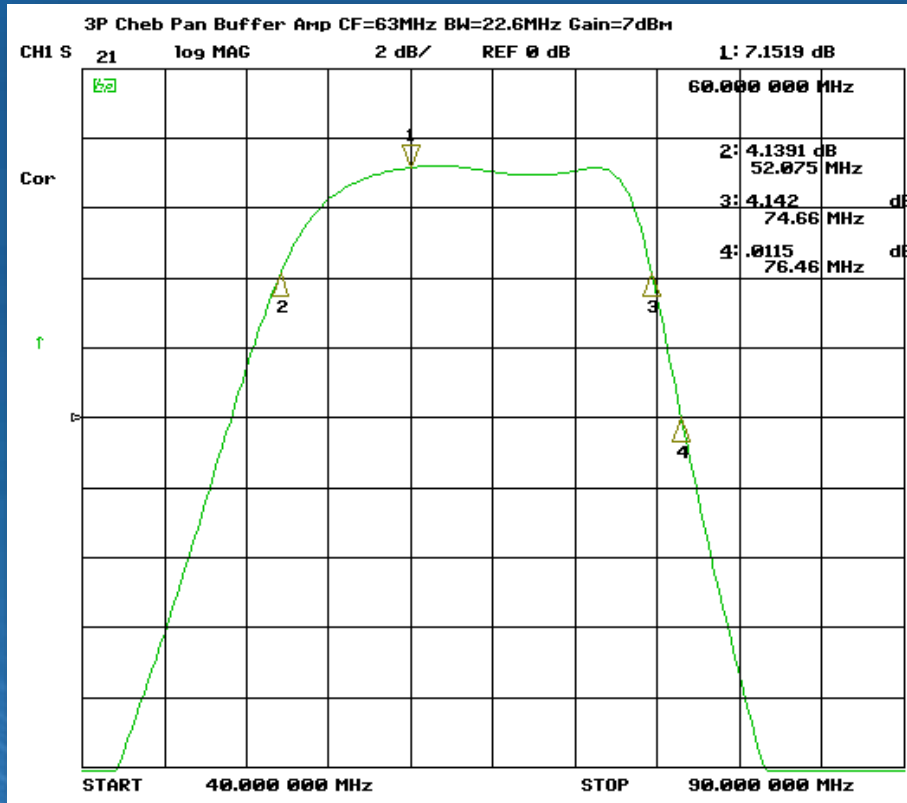
## PCB made with home brew air core inductors








# Bench Performance tests

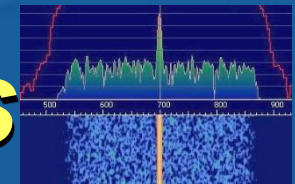

## PCB made with commercial inductors

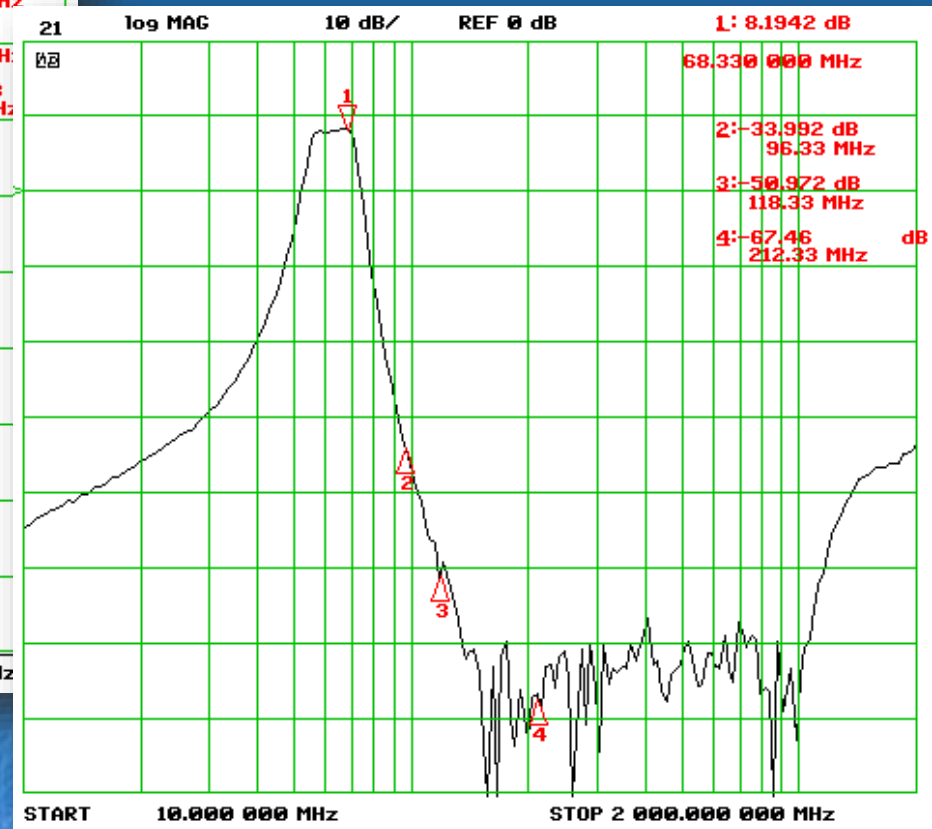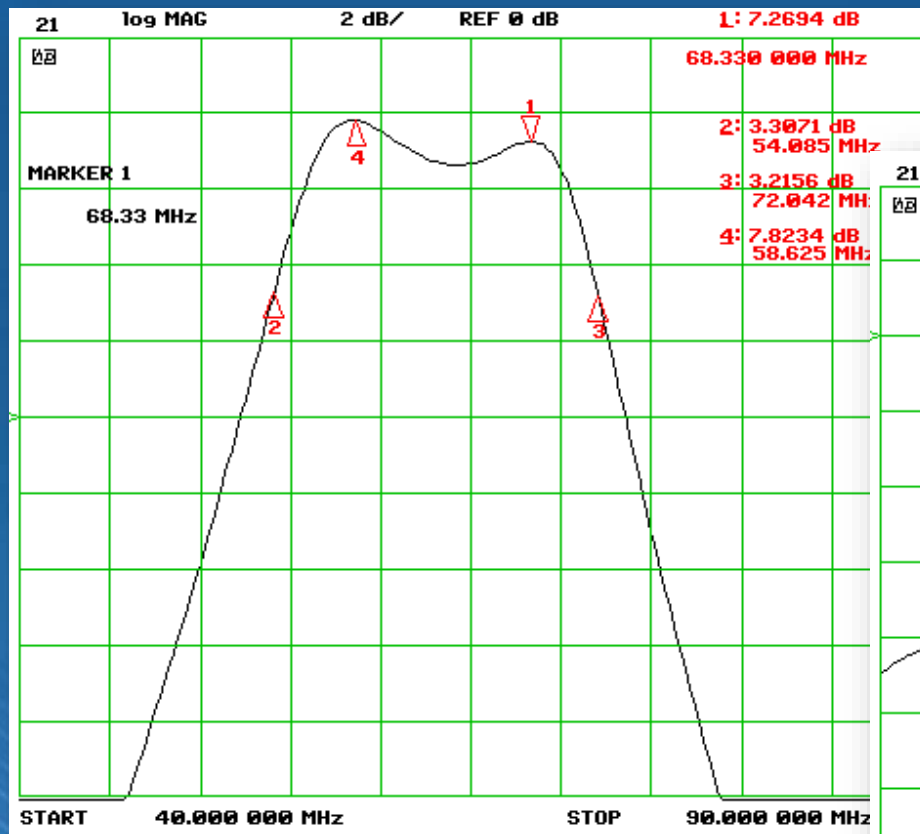


# ***Interface to a FT-817***

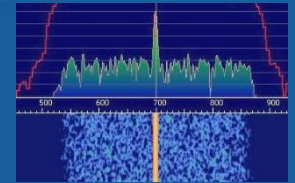



## ***Four connections are needed from the interface PCB to the transceiver***

- Switched +5V – on during Rx – off during Tx. A switched supply is very desirable as the IF is used for both Tx & Rx so the dongle display is quiet during Tx
- RF input – tapped into the radio's 1<sup>st</sup> IF before a crystal filter
- RF output – port connects the interface output to the dongle typically through a connector on the radio's rear panel
- Ground

# FT-817 Connection Points

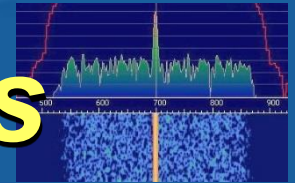

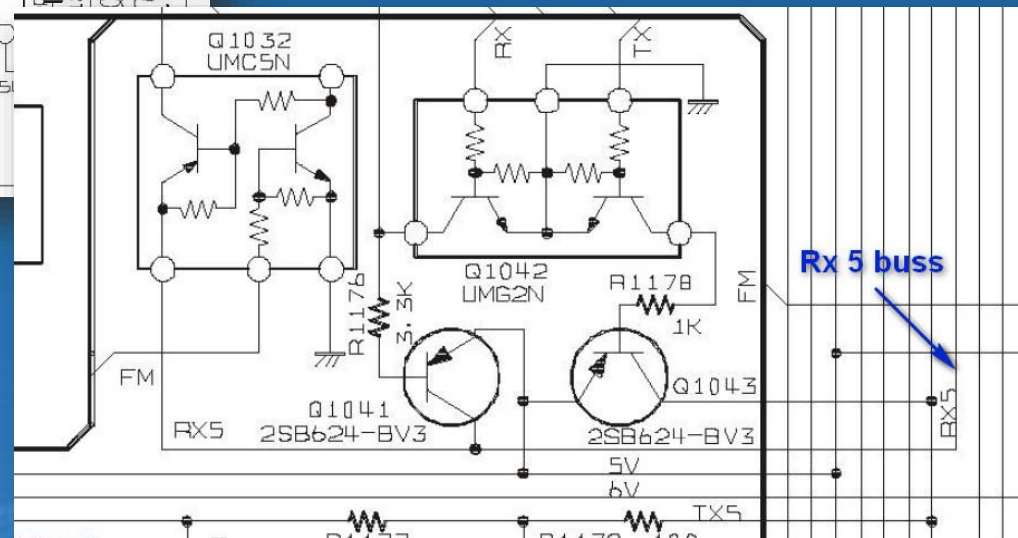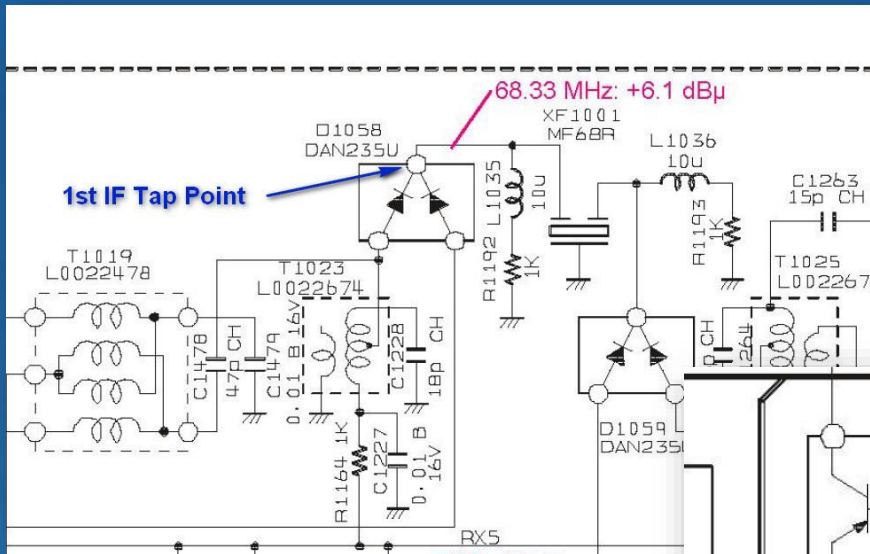
- 1<sup>st</sup> IF & switched supply on during Rx of during Tx






# FT-817 Connection Points

- Top PCB Connection Points

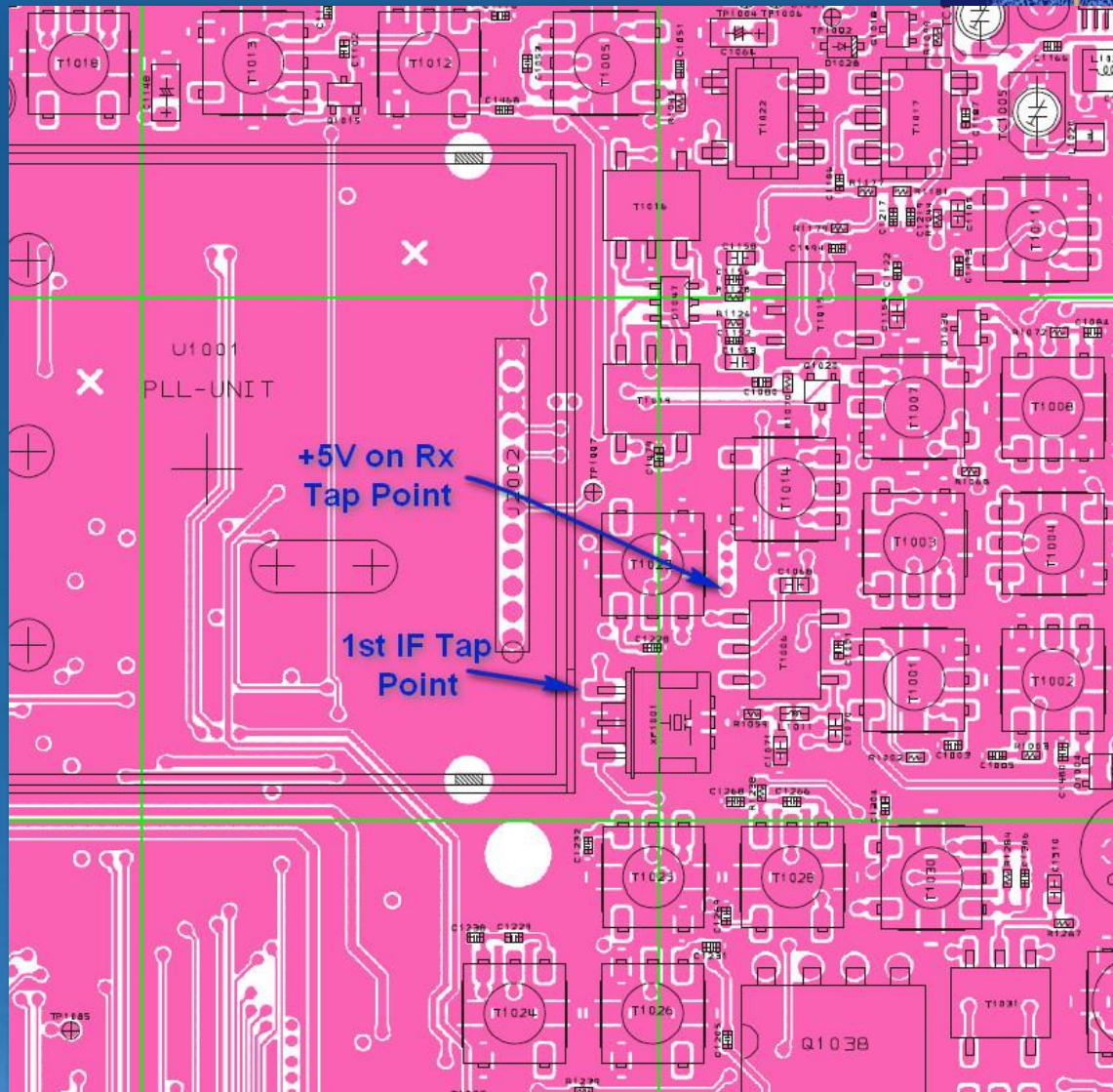




# FT-817 – I/F Connections

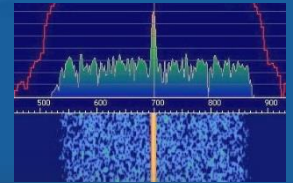

- Interface PCB bottom groundplane is soldered to the side of the PLL-Unit housing




# FT-817 – I/F Connections

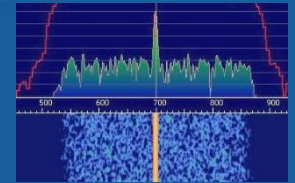

- 1<sup>st</sup> IF and 5V on Rx connections


1<sup>st</sup> IF  
connection

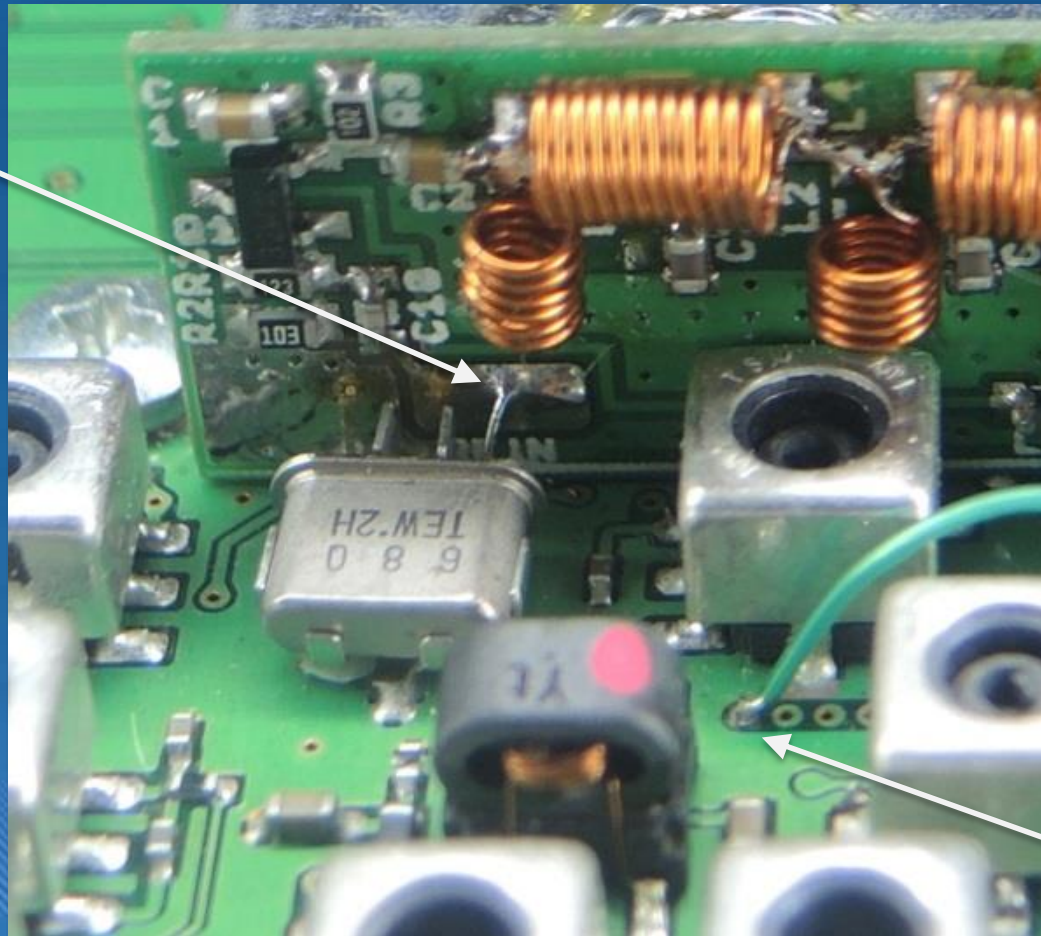


+5V on Rx  
connection



# FT-817 – I/F Connections

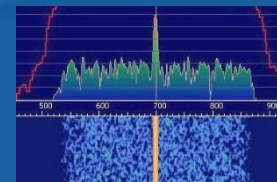


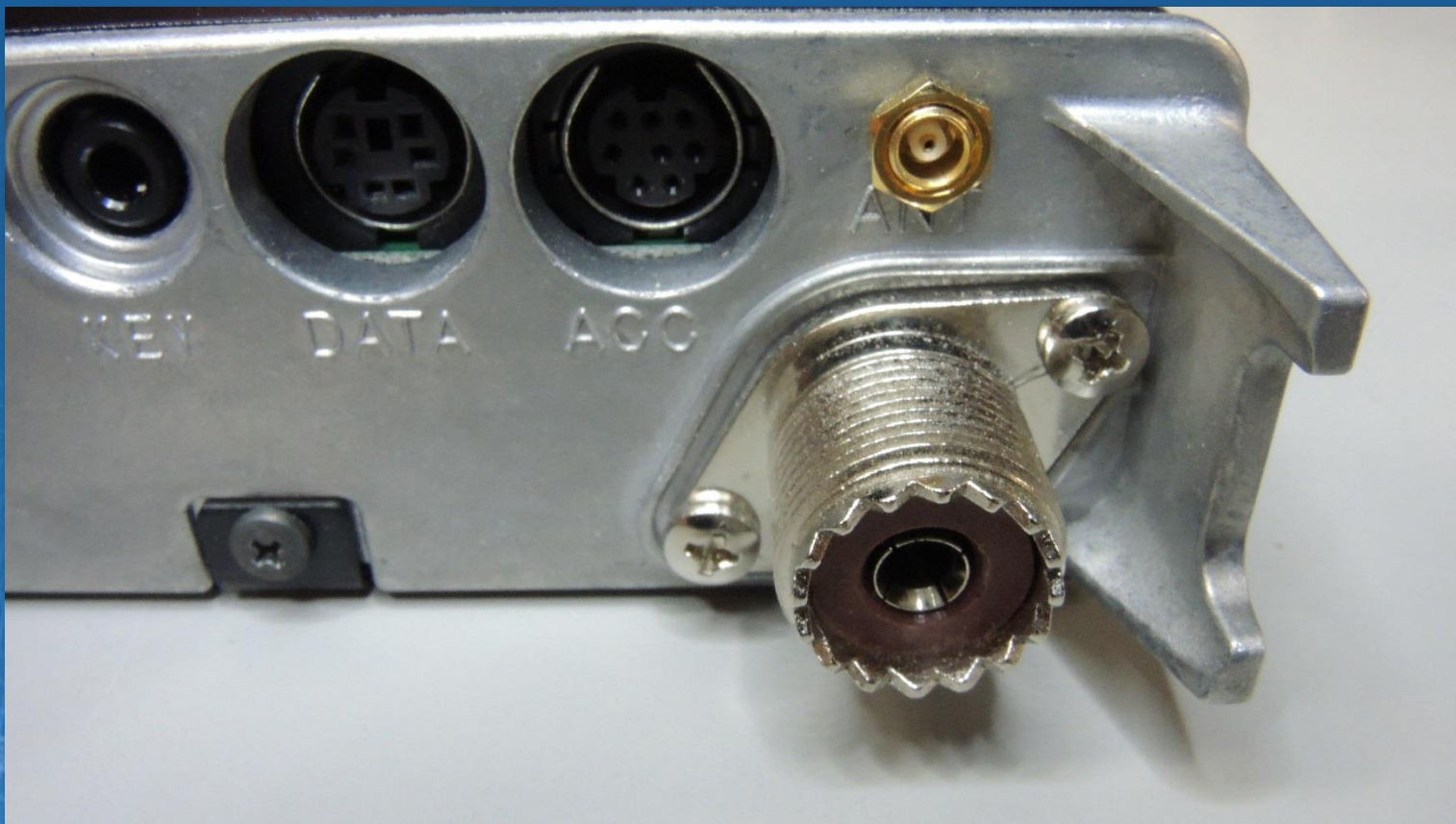- MCX push on connector jack is located above the SO239 antenna connector on the radio's rear panel



# Sensitivity Tests
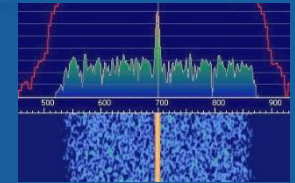
## Before & After Panadapter installation





			Baseline Measurement				FT817 wit Panadapter Installed					Difference			
Frequency	Mode	SINAD	S Units				SINAD	S Units				SINAD	S Units		
MHz		12dB	1	5	9		12dB	1	5	9		12dB	1	5	9
3.6	CWN	-123.7	-100	-96	-72		-123.9	-99	-94	-72		0.2	-1	-2	0
	CWW	-110.8	-96	-92	-71		-112.1	-95	-91	-70		1.3	-1	-1	-1
	FM 3KHz	-115.7	-103	-99	-92		-115.8	-103	-97	-91		0.1	0	-2	-1
14.1	CWN	-126.7	-104	-100	-76		-126.9	-103	-99	-80		0.2	-1	-1	4
	CWW	-113.4	-100	-96	-74		-114.4	-99.5	-95	-73		1	-0.5	-1	-1
	FM 3KHz	-118.8	-108	-101	-98		-118.3	-107	-100	-95		-0.5	-1	-1	-3
28.25	CWN	-127.8	-104	-101	-78		-127.4	-104	-100	-77		-0.4	0	-1	-1
	CWW	-115.2	-101	-97	-75		-115.5	-99	-95	-73		0.3	-2	-2	-2
	FM 3KHz	-119.4	-109	-101	-96		-119.1	-108	-100	-95		-0.3	-1	-1	-1
50.25	CWN	-131.0	-111	-107	-80		-131.1	-110	-106	-83		0.1	-1	-1	3
	CWW	-118.2	-108	-103	-78		-118.6	-105	-101	-79		0.4	-3	-2	1
	FM 3KHz	-123.3	-115	-107	-102		-123.4	-114	-106	-101		0.1	-1	-1	-1
144.25	CWN	-130.2	-112	-109	-82		-129.8	-111	-107	-83		-0.4	-1	-2	1
	CWW	-116.2	-109	-105	-79		-116.1	-106	-102	-79		-0.1	-3	-3	0
	FM 3KHz	-122.2	-116	-110	-104		-122.1	-115	-108	-103		-0.1	-1	-2	-1
430.25	CWN	-130.4	-110	-106	-79		-129.1	-109	-105	-81		-1.3	-1	-1	2
	CWW	-117.4	-107	-103	-78		-116.6	-104	-100	-78		-0.8	-3	-3	0
	FM 3KHz	-121.9	-114	-107	-102		-121.4	-113	-105	-101		-0.5	-1	-2	-1


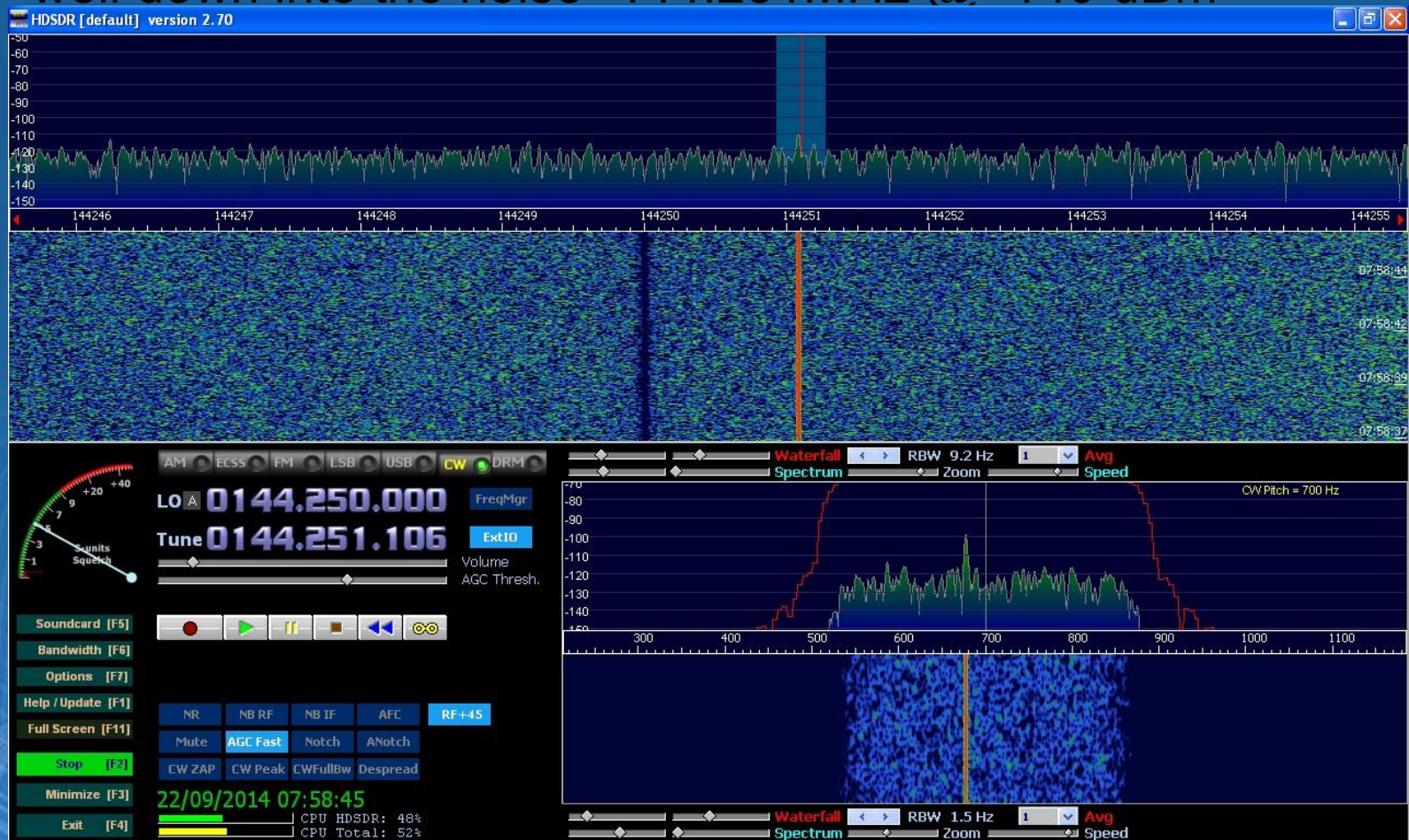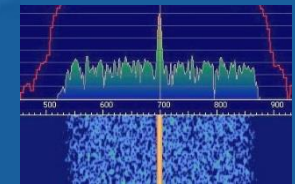
# Sensitivity



SDR display with narrow FFT bins enables signal detection well down into the noise -144.251MHz @ -140 dBm






# Sensitivity


144.251 MHz @ -150 dBm

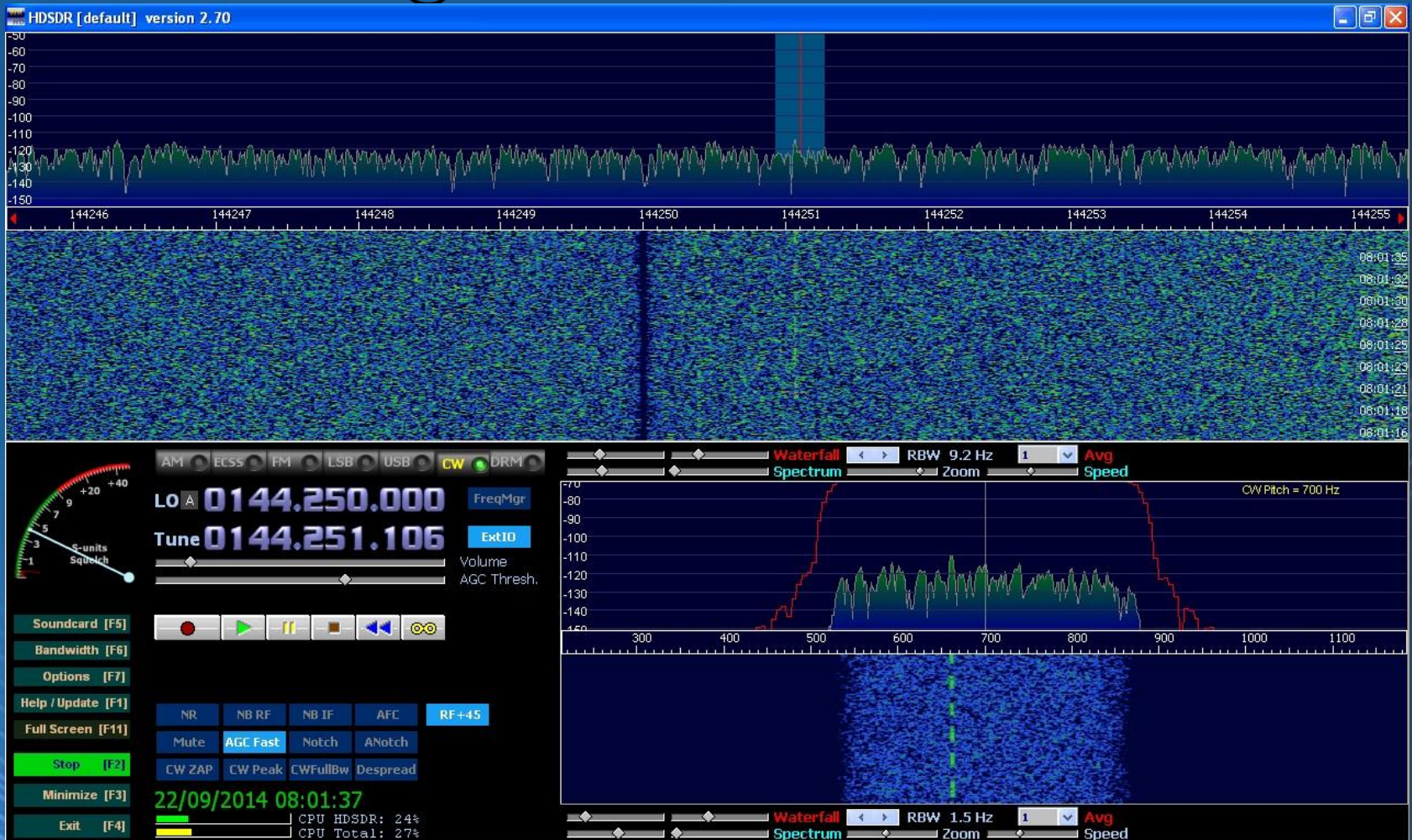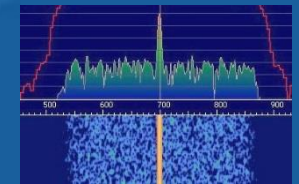

# Supply Switches



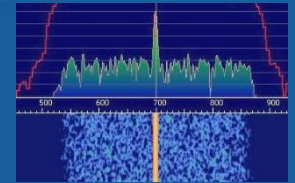


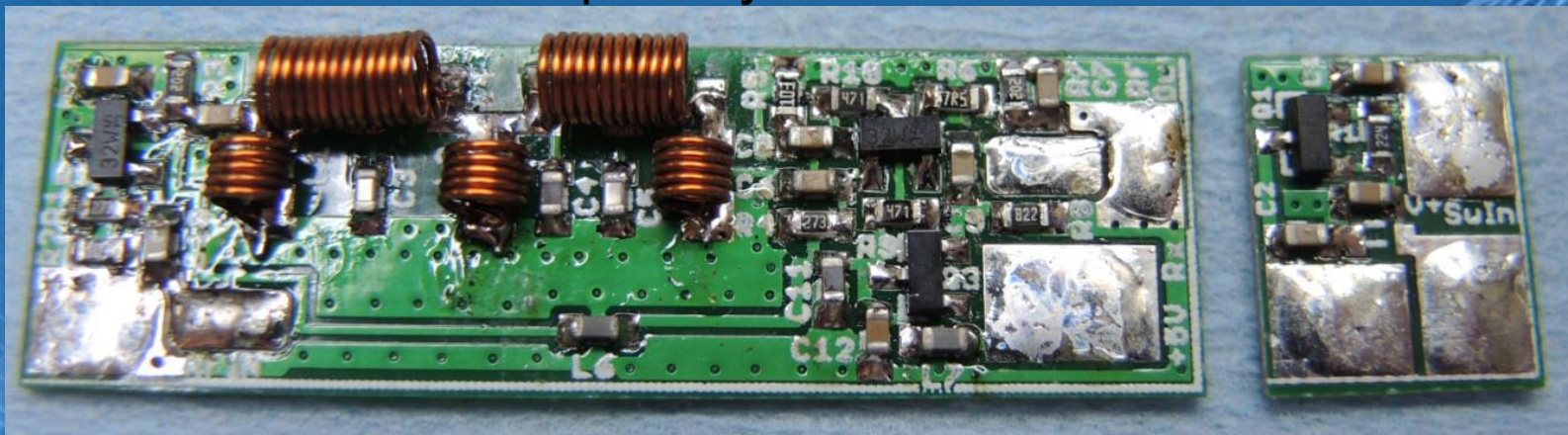- If switched V+ high on Rx isn't available or if it is but isn't capable of supplying the dongle then two switch boards can be used
- Both have the same height as the main PCB
- Simple inverting switch for rigs that have a signal low during receive and high during transmit.
- PCB with an selectable inverting switch that can be used with either control polarity






# Supply Switches (cont'd)

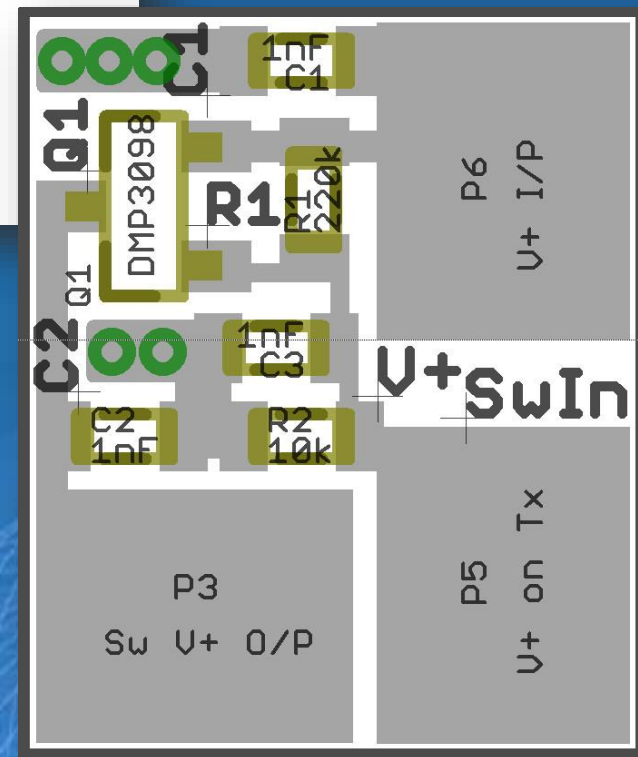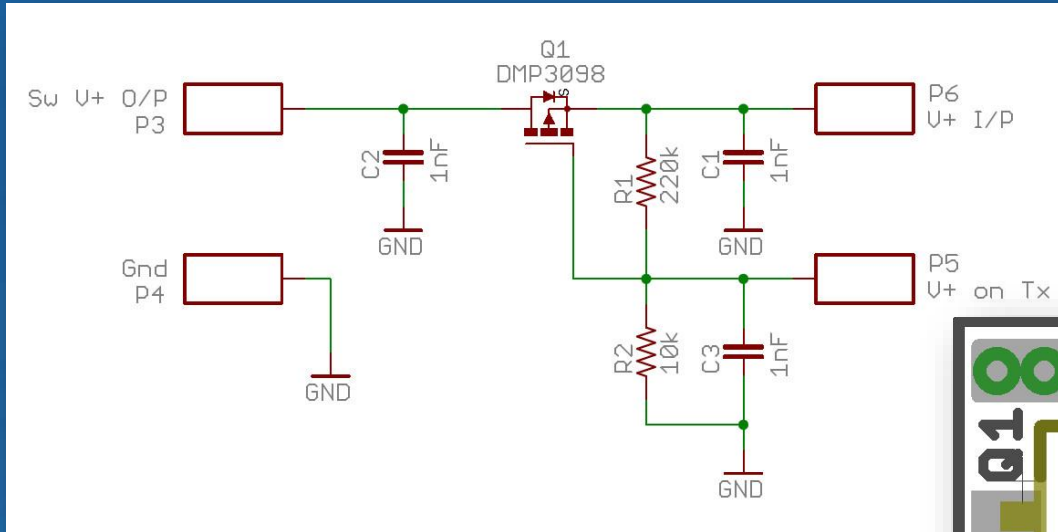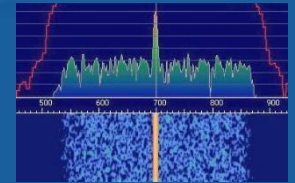
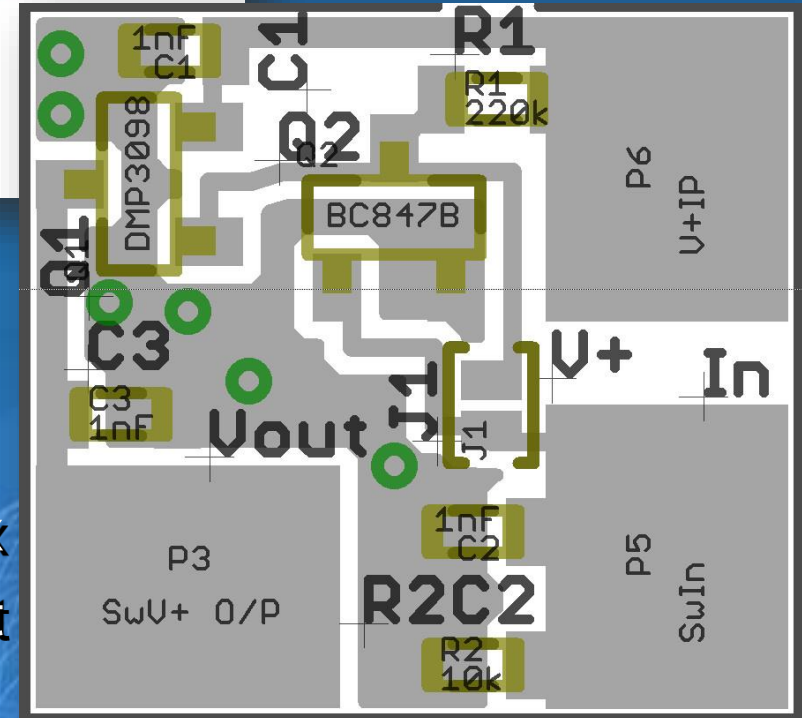
## V+ Tx Switch


- 10 mm wide
- Switch input P5  
Low on Rx &  
high on Tx





- 13mm wide
- J1 Shorted Q2 not installed  
P5 input low on Rx high on Tx
- J1 Open Q2 installed P5 input  
high on Rx low on Tx

# Application Software

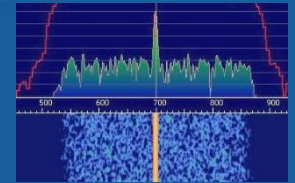

## *HDSDR chosen as the best application*

- Feature rich
- Interfaces smoothly to radio IF's and CAT software
- Not too difficult to install
  - Links to examples can be found on the HDSDR FAQ page

## *SDR#*


- Nicest looking display
- Doesn't handle IQ swap correctly (version early Sept 2014) so wasn't usable with IF for this demo. Constantly updated so problem may have been solved

## *Gqrx*

- Worked well but no time to fully evaluate



# Steps to using HDSDR

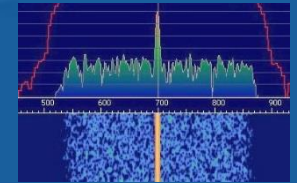

## Install on a computer

- Navigate to the HDSDR Hardware page  
<http://www.hdsdr.de/hardware.html>




- Scroll down to the RTLSDR (DVB-T/DAB with RTL2832) line.

Hardware		Website
RFSPACE SDR-IQ / SDR-14	Download	April 11, 2013
RTLSDR (DVB-T/DAB with RTL2832)	DLL How-To	February 04, 2014
SDR-1	Download	April 05, 2012
SDR MK1 / SDR MK1.5 'Android'	Website	

- Click on the How-To which will download a PDF with good install instructions

# HDSDR -configuration

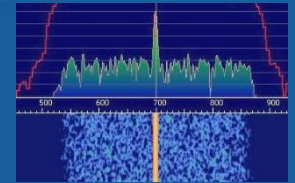

***Start the program***

***HDSDR has a slew of options that can be confusing.***

- Start with the menu items lower left side.
- Leave the Soundcard [F5] alone.






# HDSDR - configuration


- Bandwidth [F4] select the following:

Sampling Rate [Hz]



Input	Output
12000	12000
24000	24000
48000	48000
96000	96000
192000	192000
<hr/>	
11025	11025
22050	22050
44100	44100
88200	
176400	
<hr/>	
8000	4000
16000	8000
32000	
<hr/>	
2400000	<input type="button" value="v"/>

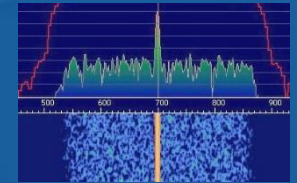

# HDSDR - configuration

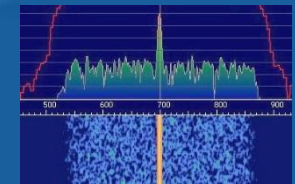


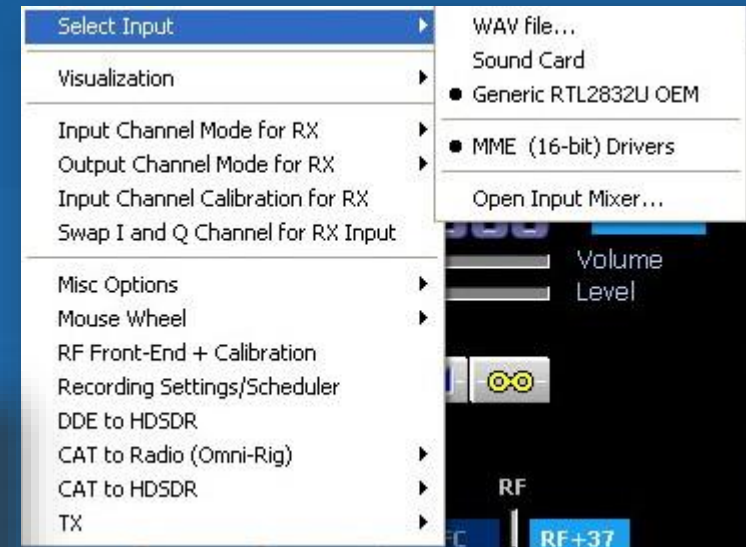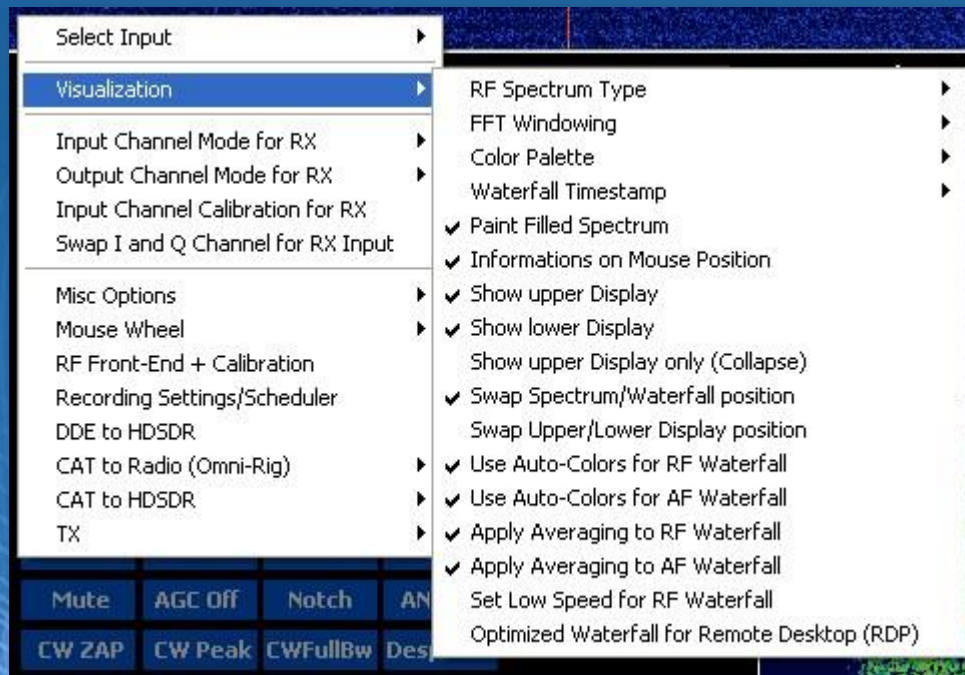- Options [F7]
  - Select Input and visualization should look like the panels on this page
  - Don't change any submenus at this time







# HDSDR - configuration


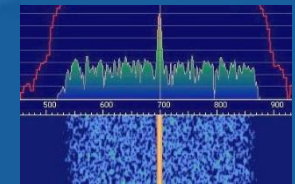


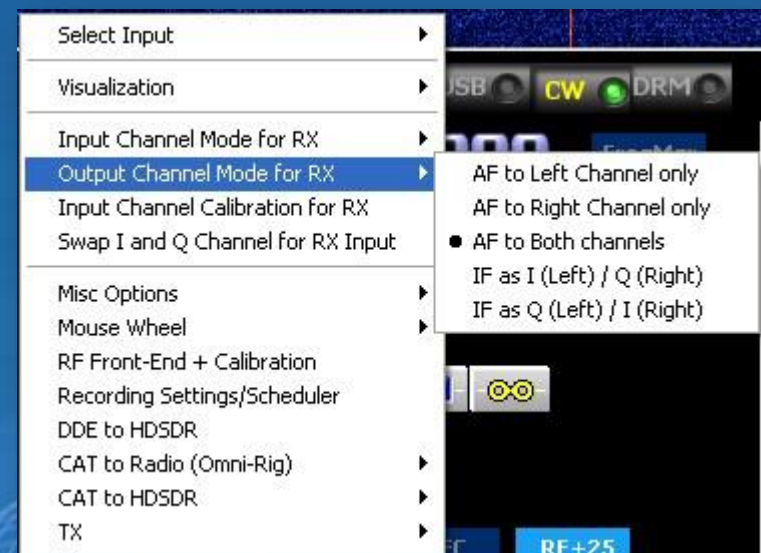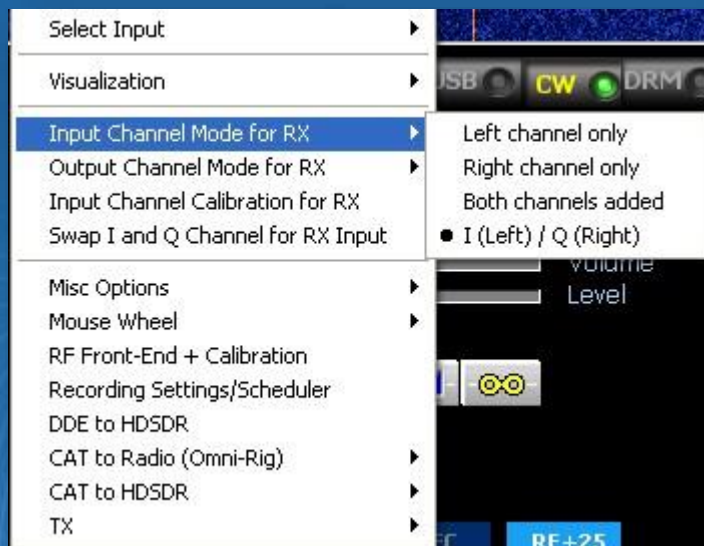- Options [F7]
  - Input channel mode for Rx
  - Output Channel mode for Rx


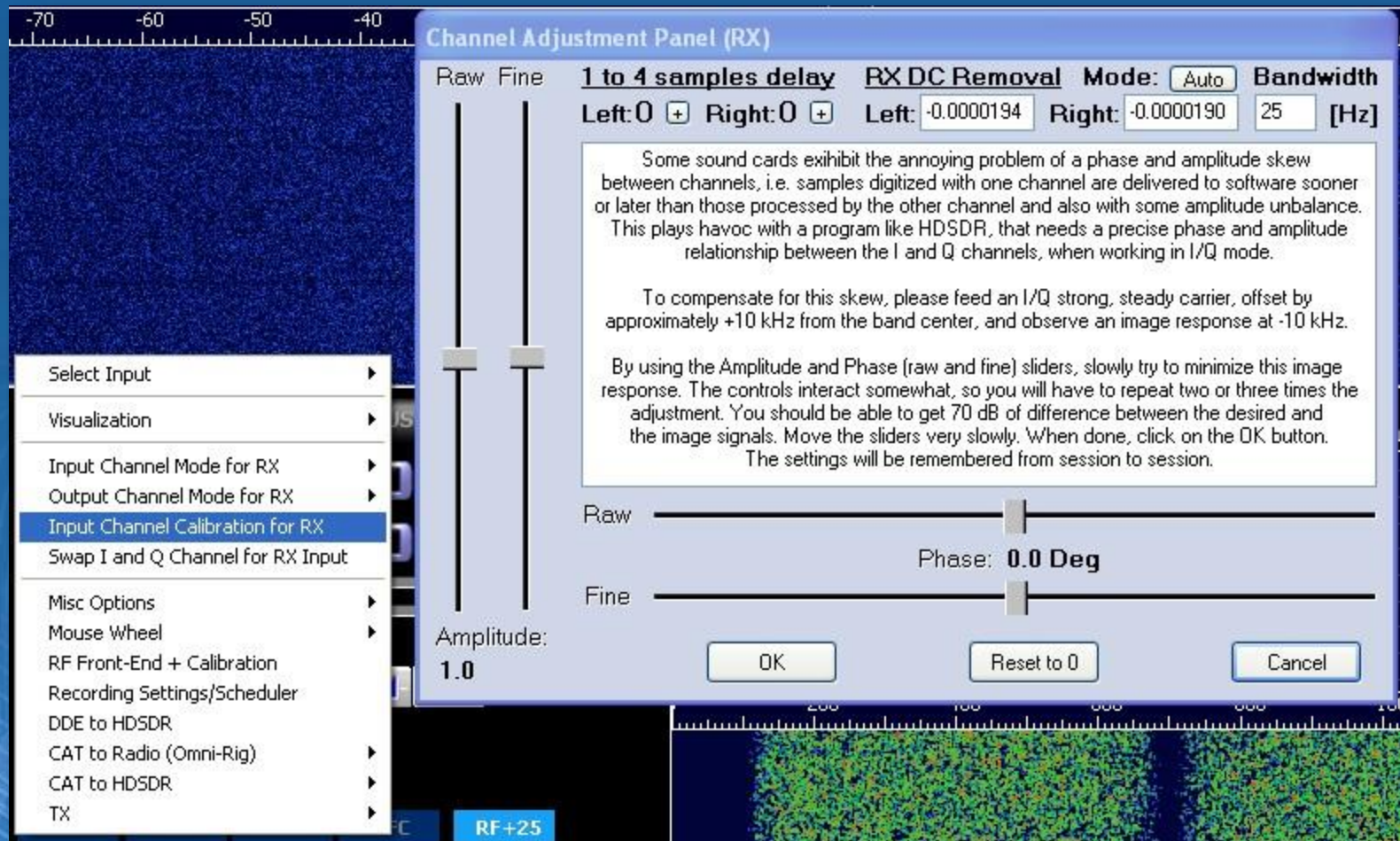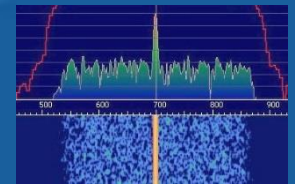
# HDSDR - configuration

- Options [F7] - Input channel mode for Rx
  - Select RX DC Removal Mode: Auto - leave the rest alone



**Channel Adjustment Panel (RX)**

Raw Fine **1 to 4 samples delay** **RX DC Removal Mode:**  **Bandwidth**  [Hz]

Left: 0 + Right: 0 + Left: -0.0000194 Right: -0.0000190

Some sound cards exhibit the annoying problem of a phase and amplitude skew between channels, i.e. samples digitized with one channel are delivered to software sooner or later than those processed by the other channel and also with some amplitude unbalance. This plays havoc with a program like HDSDR, that needs a precise phase and amplitude relationship between the I and Q channels, when working in I/Q mode.

To compensate for this skew, please feed an I/Q strong, steady carrier, offset by approximately +10 kHz from the band center, and observe an image response at -10 kHz.

By using the Amplitude and Phase (raw and fine) sliders, slowly try to minimize this image response. The controls interact somewhat, so you will have to repeat two or three times the adjustment. You should be able to get 70 dB of difference between the desired and the image signals. Move the sliders very slowly. When done, click on the OK button. The settings will be remembered from session to session.

Raw  Fine

Amplitude: 1.0


OK Reset to 0 Cancel

Select Input  
Visualization  
Input Channel Mode for RX  
Output Channel Mode for RX  
**Input Channel Calibration for RX**  
Swap I and Q Channel for RX Input  
Misc Options  
Mouse Wheel  
RF Front-End + Calibration  
Recording Settings/Scheduler  
DDE to HDSDR  
CAT to Radio (Omni-Rig)  
CAT to HDSDR  
TX


RF+25




# HDSDR - configuration

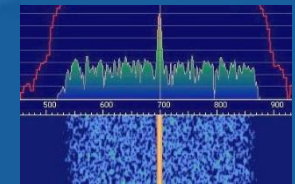

- Options [F7]
  - Misc.
  - Mouse Wheel

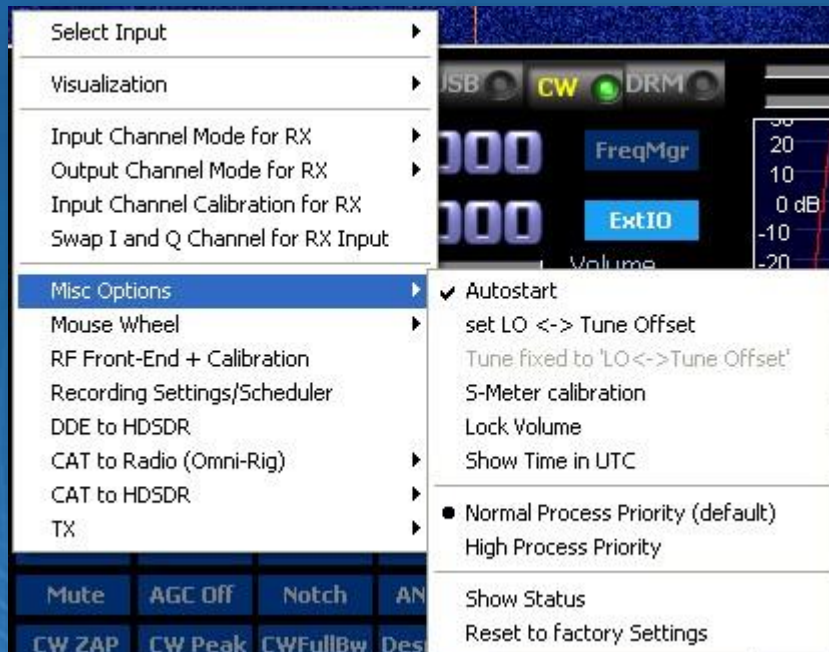

# HDSDR - configuration

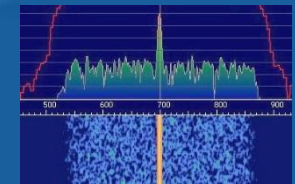

*Now for the really important ones:*

Select Input

Visualization

Input Channel Mode for RX

Output Channel Mode for RX

Input Channel Calibration for RX

Swap I and Q Channel for RX Input

Misc Options

Mouse Wheel

RF Front-End + Calibration

Recording Settings/Scheduler

DDE to HDSDR

CAT to Radio (Omni-Rig)

CAT to HDSDR

TX

Mute

AGC Fast

Notch

ANot

CW ZAP

CW Peak

CWFullBw

Despr

RF front-end frequency options & Calibration

SDR hardware coupling

☒ SDR hardware connected to antenna (default)

☐ SDR on IF output, which is controlled manually

Sync Mode

☐ Full sync in both directions

☒ Independent Tune in HDSDR

☐ Independent Tune, but sync on external change

IF-frequency: 68330000 [Hz]

Global Offset: 0 [Hz]

Additional Offset per Mode in Hz

AM	FM	LSB	USB	CW_U	CW_L	DIG_U	DIG_L
0	0	0	0	0	0	0	0

☒ Mirror RF Spectrum in general

☐ Mirror RF Spectrum for Tune >= 0 kHz

☐ operate CW in lower sideband (LSB)

☐ Swap CW and CWR for Omni-Rig

☐ SDR hardware on Down/Up-Converter

LO Frequency of Down/Up-Converter in Hz: 120000000

☐ SDR hardware in undersampling mode

Samplerate of Analog-Digital Converter in Hz: 80000000

Apply

LO frequency calibration

Current Tune Frequency [Hz]

470309441.00

Correct Tune Frequency [Hz]

470309000

Reset

Calculate

Frequency correction: +0.00 ppm


Hint: Tune to a station with known frequency as reference, e.g. a WWV or RWM time signal. Use ECSS mode with AFC to automatically tune the reference carrier exactly. Use highest possible frequency for best calibration results.

Phase

+0°



# HDSDR - configuration

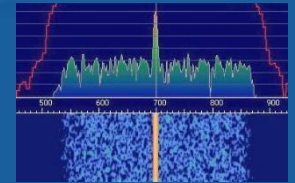


## ExIO



- Click on the ExtIO button
- Increase the tuner gain slider to between 30 and 40dB.
- Turn off all AGC
- Check that the sample rate and buffer size match the window on the right.



# HDSDR – Freq. calibration

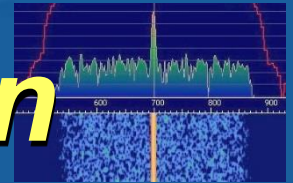

## Frequency correction – Part 1



- Connect an antenna capable of receiving a signal of known frequency to the DVB-T dongle
  - A good choice for this is often a local off air HDTV signal as they are typically quite strong.
  - A pilot tone can be easily identified. It's 309,441 Hz above the lower band edge. The lower band edge frequency for all UHF channels can be found here:

<http://www.csgnetwork.com/tvfreqtable.html>


- Enter the known frequency values in the HDSDR LO and Tune values



# HDSDR – Freq. calibration

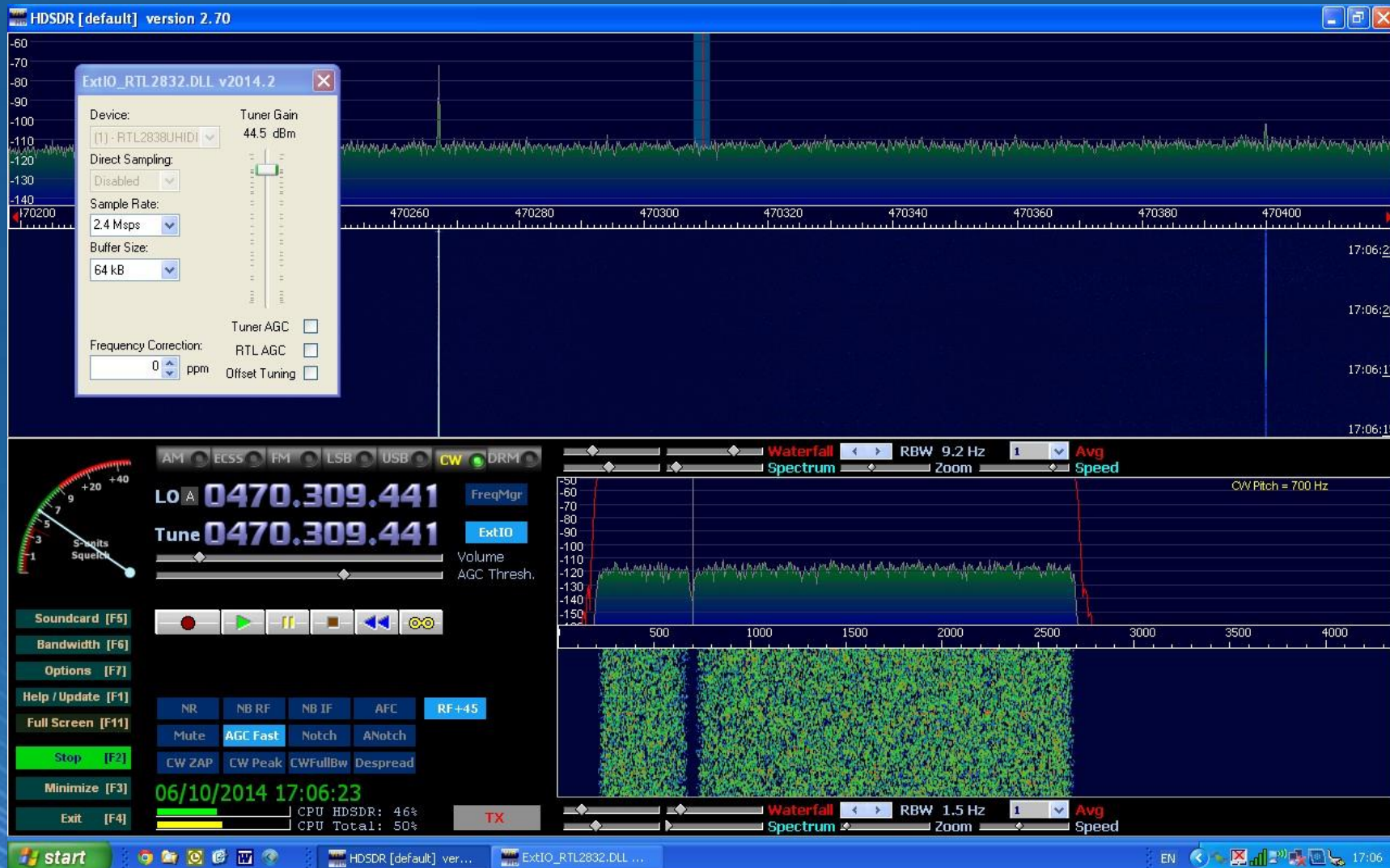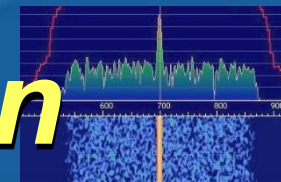


# HDSDR – Freq. calibration

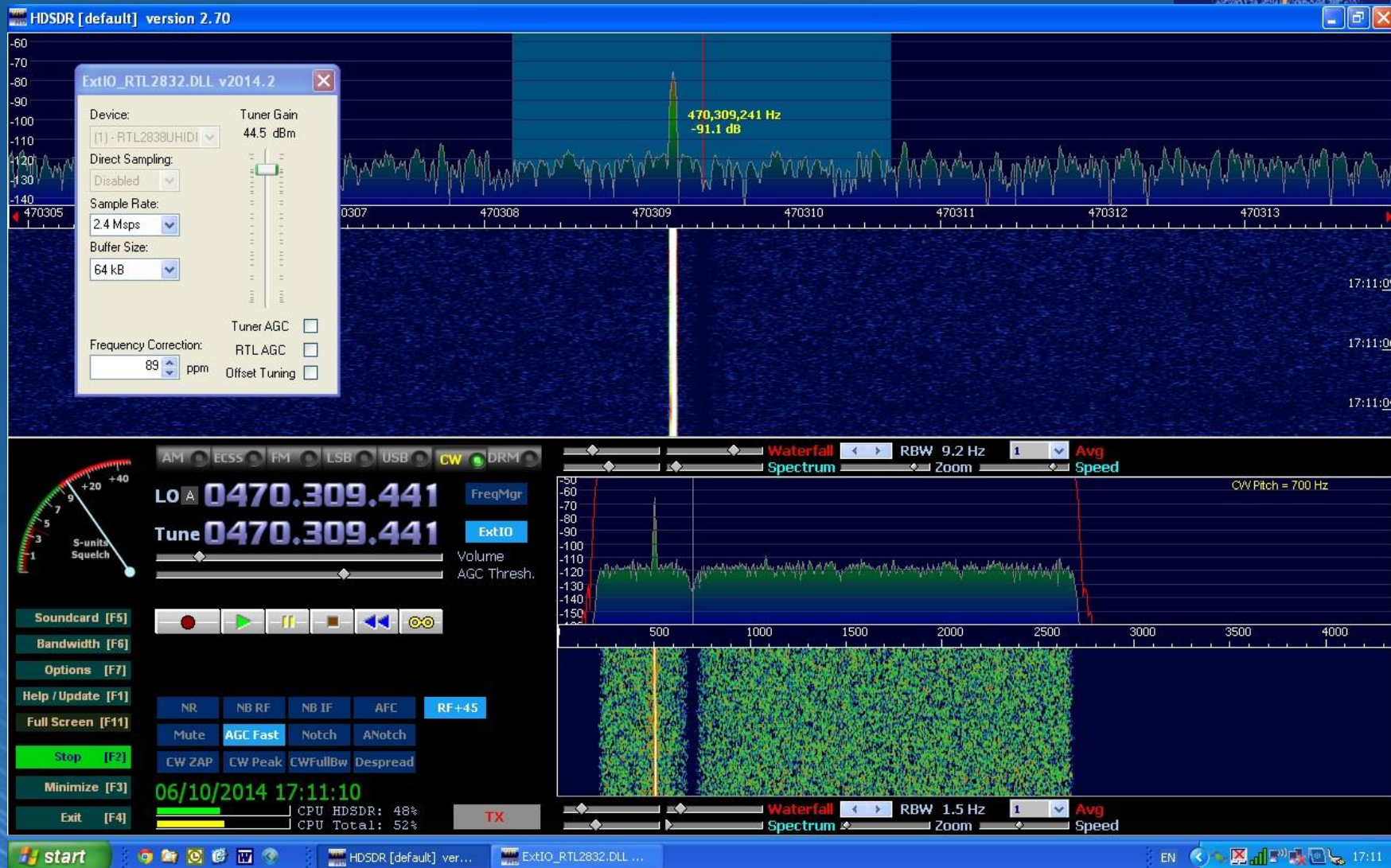




# ***HDSDR – Freq. calibration***

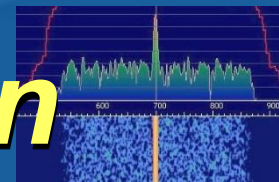

## ***Next account for any transceiver 1<sup>st</sup> IF LO error***

- Connect the DVB-T dongle to the radio's 1<sup>st</sup> IF interface.
- Tune the radio to a known frequency – WWV is good if it can be received. In Ottawa air band information channels can provide a good constant AM carrier. One such beacon is located at 132.950 MHz. Tune the radio to this frequency and set the mode to AM
- Set the HDSDR LO and Tune frequency to zero Hertz and the mode to AM.
- Change the RF gain as necessary to get a good display
- Zoom out if necessary to find the carrier. It should be within a couple kHz of the center frequency.
- Bring up the Options – RF Front-End & Calibration window

# HDSDR – Freq. calibration

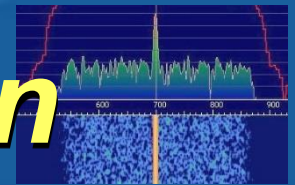

HDSDR [default] version 2.70

521 Hz -92.1 dB

RF front-end frequency options & Calibration

**SDR hardware coupling**

- ☐ SDR hardware connected to antenna (default)
- ☒ SDR on IF output, which is controlled manually

**Sync Mode**

- ☐ Full sync in both directions
- ☒ Independent Tune in HDSDR
- ☐ Independent Tune, but sync on external change

IF-frequency: 68330000 [Hz] Global Offset: 0 [Hz]

Additional Offset per Mode in Hz

AM	FM	LSB	USB	CW_U	CW_L	DIG_U	DIG_L
0	0	0	0	0	0	0	0

- ☒ Mirror RF Spectrum in general
- ☐ Mirror RF Spectrum for Tune >= 0 kHz
- ☐ operate CW in lower sideband (LSB)
- ☐ Swap CW and CWR for Omni-Rig

☐ SDR hardware on Down/Up-Converter  
LO Frequency of Down/Up-Converter in Hz: 120000000

☐ SDR hardware in undersampling mode  
Samplerate of Analog-Digital Converter in Hz: 80000000

Apply

**LO frequency calibration**

Current Tune Frequency [Hz]: 1.00  
Correct Tune Frequency [Hz]: 0

Reset Calculate

Frequency correction: +0.00 ppm

Hint: Tune to a station with known frequency as reference, e.g. a WWV or RWM time signal. Use ECSS mode with AFC to automatically tune the reference carrier exactly. Use highest possible frequency for best calibration results.

Phase: +0°

06/10/2014 16:49:33


CPU HDSDR: 60%  
CPU Total: 64%

TX

Spectrum Zoom Speed



# HDSDR – Freq. calibration

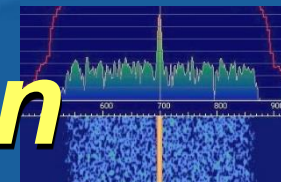

HDSDR [default] version 2.70

RF front-end frequency options & Calibration

**SDR hardware coupling**

- ☐ SDR hardware connected to antenna (default)
- ☒ SDR on IF output, which is controlled manually

**Sync Mode**

- ☐ Full sync in both directions
- ☒ Independent Tune in HDSDR
- ☐ Independent Tune, but sync on external change

**IF-frequency:** 68329480 [Hz] **Global Offset:** 0 [Hz]

**Additional Offset per Mode in Hz**

AM	FM	LSB	USB	CW_U	CW_L	DIG_U	DIG_L
0	0	0	0	0	0	0	0

☒ Mirror RF Spectrum in general  
☐ Mirror RF Spectrum for Tune  $\geq$  0 kHz  
☐ operate CW in lower sideband (LSB)  
☐ Swap CW and CWR for Omni-Rig

☐ SDR hardware on Down/Up-Converter  
LO Frequency of Down/Up-Converter in Hz: 120000000

☐ SDR hardware in undersampling mode  
Samplerate of Analog-Digital Converter in Hz: 80000000

**LO frequency calibration**

Current Tune Frequency [Hz]: 1.00  
Correct Tune Frequency [Hz]: 0

Reset Calculate

Frequency correction: +0.00 ppm

Hint: Tune to a station with known frequency as reference, e.g. a WWV or RWM time signal. Use ECSS mode with AFC to automatically tune the reference carrier exactly. Use highest possible frequency for best calibration results.

Phase: +113°

06/10/2014 16:51:41


CPU HDSDR: 45%  
CPU Total: 48%

TX

Waterfall Spectrum RBW 1.5 Hz Zoom Avg Speed
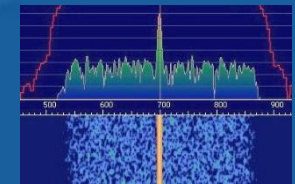
# Use without CAT

- There is no communication between the transceiver and HDSDR
- Set the 'RF front-end frequency options & Calibration. Don't change the IF-Frequency



**RF front-end frequency options & Calibration**

**SDR hardware coupling**

☐ SDR hardware connected to antenna (default)

☒ SDR on IF output, which is controlled manually

**Sync Mode**

☐ Full sync in both directions

☒ Independent Tune in HDSDR

☐ Independent Tune, but sync on external change

IF-frequency: 68331800 [Hz]      Global Offset: 0 [Hz]

Additional Offset per Mode in Hz

AM	FM	LSB	USB	CW_U	CW_L	DIG_U	DIG_L
0	0	0	0	0	0	0	0

☒ Mirror RF Spectrum in general

☐ Mirror RF Spectrum for Tune  $\geq$  0 kHz

☐ operate CW in lower sideband (LSB)

☐ Swap CW and CWR for Omni-Rig

☐ SDR hardware on Down/Up-Converter  
LO Frequency of Down/Up-Converter in Hz: 120000000

☐ SDR hardware in undersampling mode  
Samplerate of Analog-Digital Converter in Hz: 800000000

**Apply**

**LO frequency calibration**

Current Tune Frequency [Hz]: 14000000.00

Correct Tune Frequency [Hz]: 14000000

**Reset**      **Calculate**

Frequency correction: **+0.00 ppm**


Hint: Tune to a station with known frequency as reference, e.g. a WWV or RWM time signal. Use ECSS mode with AFC to automatically tune the reference carrier exactly. Use highest possible frequency for best calibration results.

**Phase**

**+0°**




# *Use Without CAT*

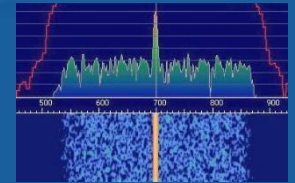

## *Mode 1*


- Tune the transceiver to a band edge i.e. 14,000,000.
- Set the HDSDR LO and Tune to the same frequency.
- Use the HDSDR as the receiver.
- On the HDSDR screen move the band edge to the left of the screen and use the zoom slider to get the desired frequency window.
- Then use the Tune entry or mouse click on the panadapter display to change frequency
- Do not change the LO setting.
- Note if the transceiver frequency is changed the HDSDR LO and Tune must also be set to the same frequency.

# Use Without CAT

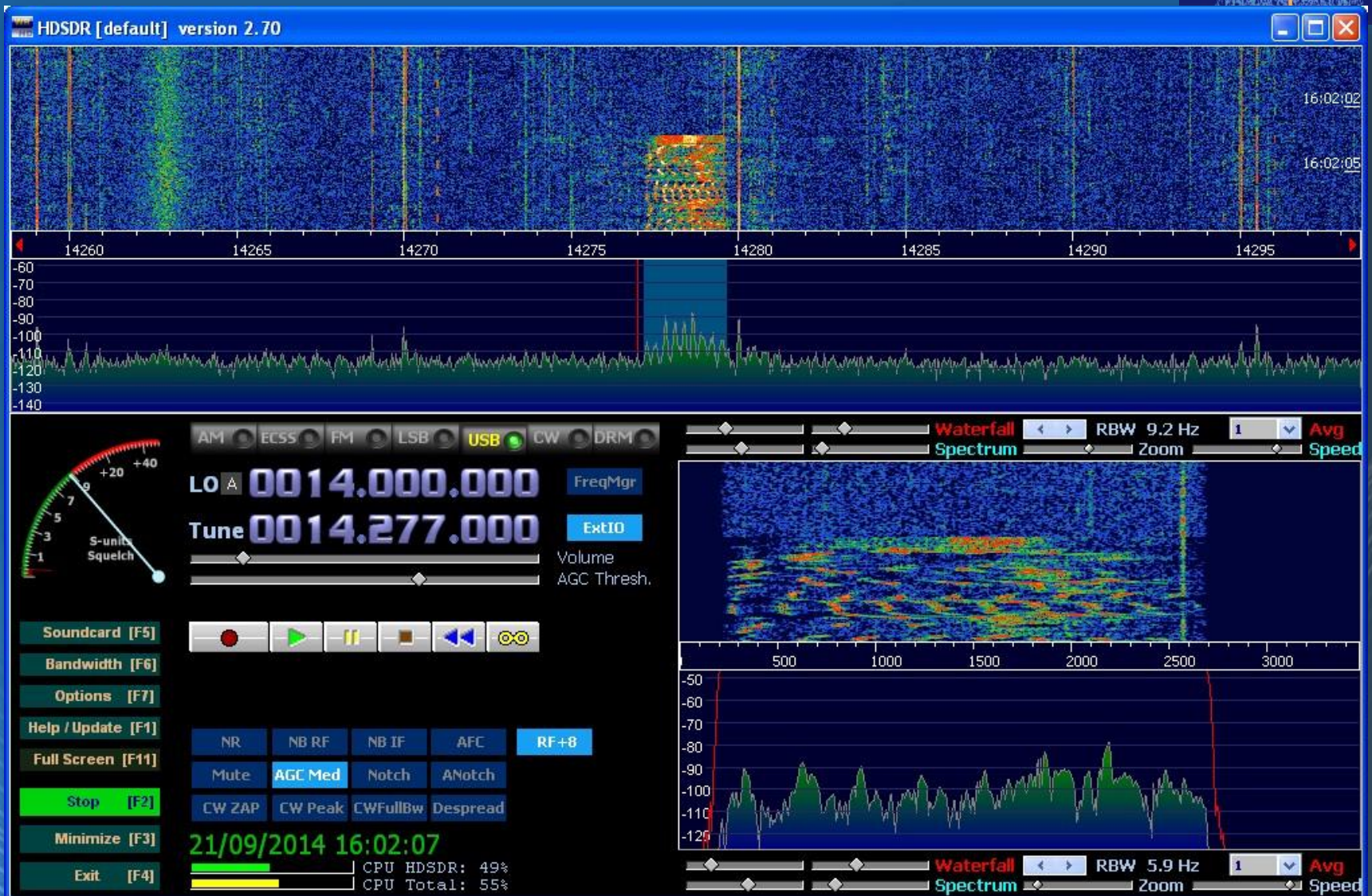




# ***Use Without CAT***

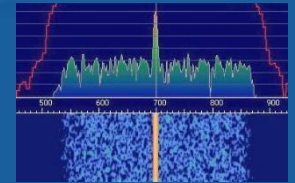


## ***Mode 2 – tune to zero – useful for contesting***

- Tune the transceiver to a frequency of interest say 144.250 MHz
- Set the HDSDR LO and Tune to zero. 144.250 MHz is now the display center
- Set the zoom to a range of frequencies that should be monitored for activity
- When a signal appears on the HDSDR display tune the radio so that the signal is positioned at zero.
- Make a contact, the frequency can be read off of the radio
- Don't forget to retune the radio back to 144.250 after the contact

# Tune to zero example

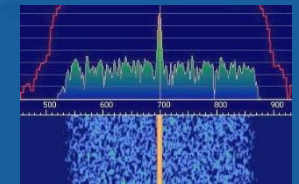

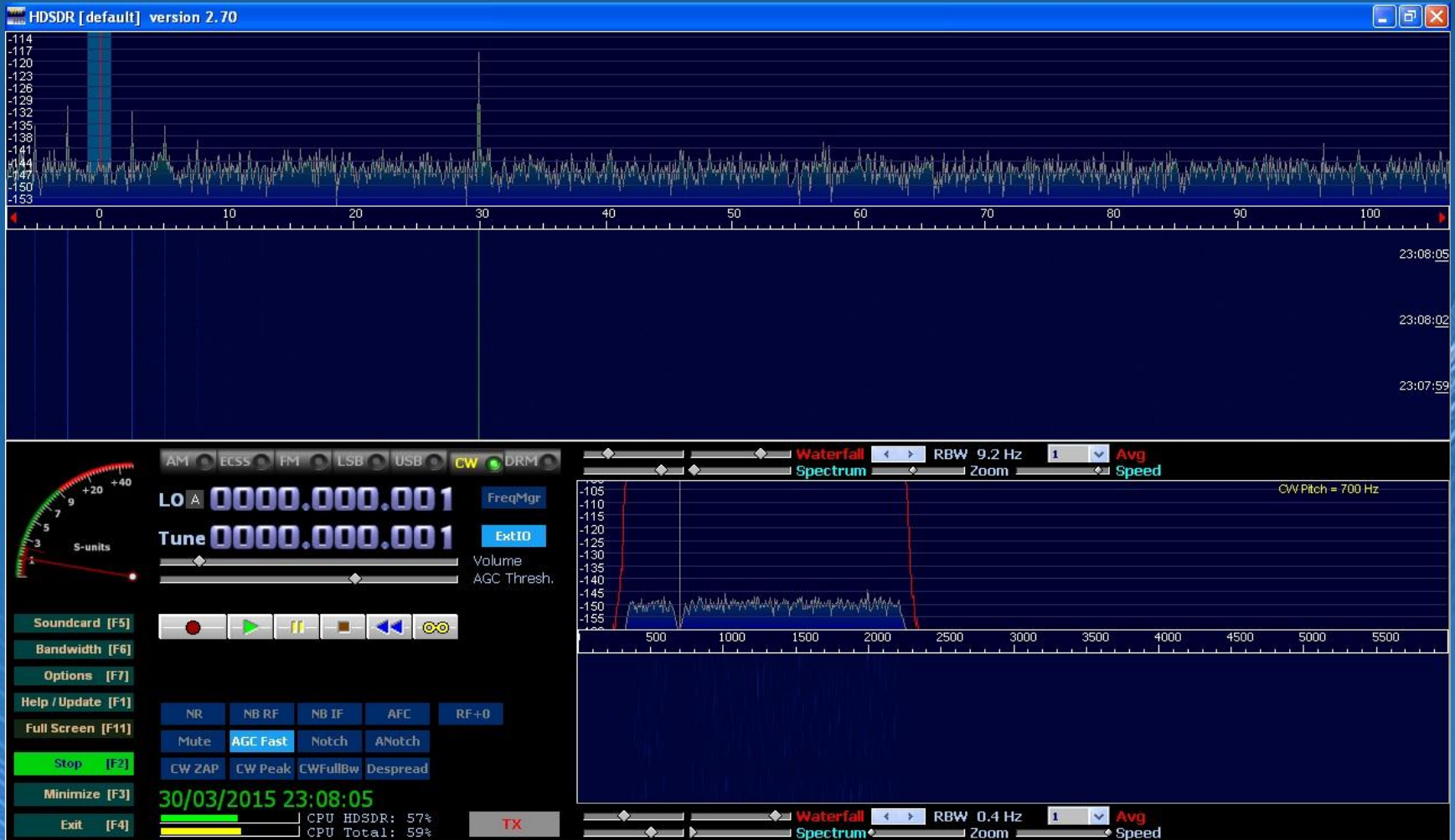0 = 144.250MHz - watching 144.250-144.350 - signal @ 144.280







# CAT-62 Cable
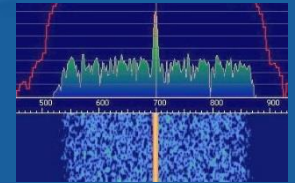
## On the cheap

- Buy one of these along with a male 8 pin mini-DIN connector





### FT232RL FTDI USB to TTL Serial Adapter Module for Arduino

Item condition: **New**

Quantity:  More than 10 available / **102 sold**

Was: **US \$4.59**

You save: **US \$0.96 (20% off)**

Price: **US \$3.63**  
Approximately C \$4.09

[Buy It Now](#)

[Add to cart](#)

25 watchers

[Add to watch list](#)

[Add to collection](#)

<b>Experienced</b> Seller	<b>Free</b> Shipping	<b>102</b> Sold
------------------------------	-------------------------	--------------------


Shipping: **FREE** Economy Int'l Shipping | [See details](#)  
See details about international shipping here.

Item location: **Beijing, China**

Ships to: **Worldwide** | [See exclusions](#)


Delivery: **Estimated Delivery within 12-23 business days**  
Seller ships within 1 day after receiving cleared payment.

# CAT-62 Cable

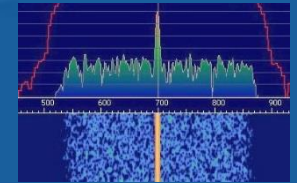

## On the cheap

- Or one of these along with a male 8 pin mini-DIN connector



5V  
GND  
RXD  
TXD  
RTS  
CTS

### 6pin FTDI FT232RL USB to TTL Serial cable Converter Adapter for Arduino

Item condition: **New**

Quantity:  More than 10 available / 32 sold

Price: **US \$5.99**  
Approximately C \$7.54

[Buy It Now](#)

[Add to cart](#)

4 watching

[Add to watch list](#)

[Add to collection](#)

<b>Free shipping</b>	32 sold	New condition
----------------------	---------	---------------

Shipping: **FREE** Economy Int'l Shipping | [See details](#)  
See details about international shipping here. ⓘ

Item location: **Hong Kong, Hong Kong**

Ships to: **Worldwide** | [See exclusions](#)


Delivery: Estimated Delivery within 10-23 business days  
Seller ships within 1 day after receiving cleared payment. ⓘ

Payments: [PayPal](#) [VISA](#) [MasterCard](#) [Discover](#)

Credit cards processed by PayPal  
[See payment information](#)





# CAT-62 Cable

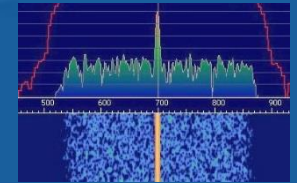


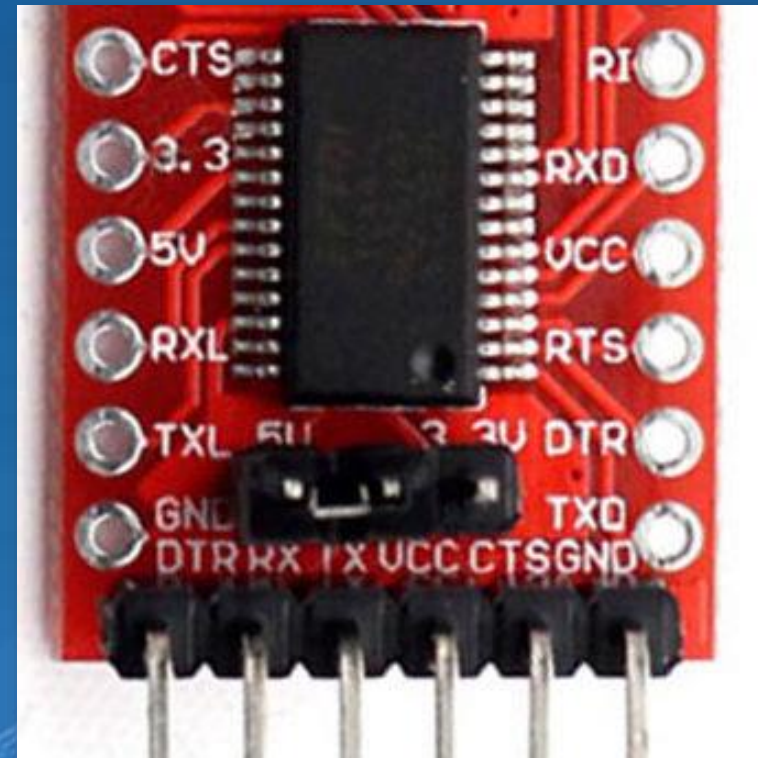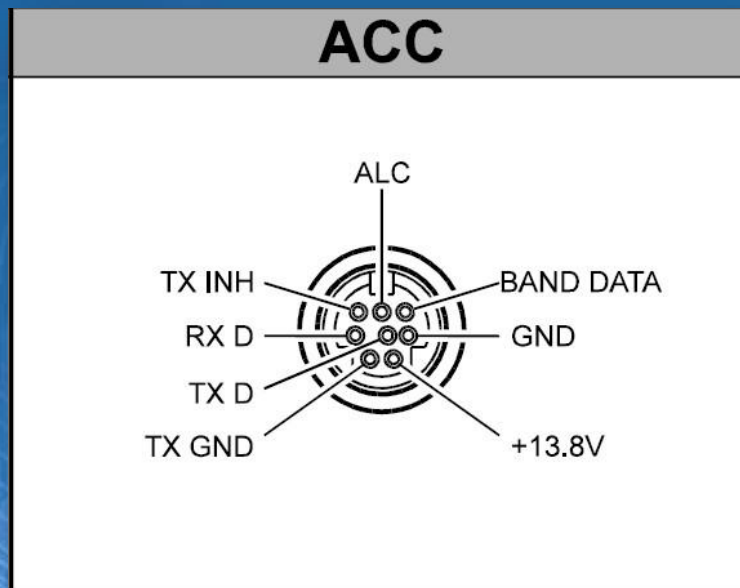***Wire it.... just a 3 wire cable ... no components***

- ACC FT232RL PCB
- RX D TX
- TX D Rx
- GND GND



# Use with CAT

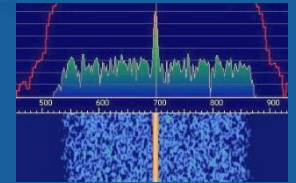


- Set the transceiver baud rate to match the application. The fastest rate reduces delays – 38,400 baud
  - The FT-817 does NOT autobaud, It must be configured manually
  - Download and install Omni-Rig with .ini files for the transceiver. Don't worry about the .ini files they're handled seamlessly during the installation.

<http://www.dxatlas.com/OmniRig/>



- Configure Omni-Rig for use with HDSDR using the following



# Omni-Rig Configuration

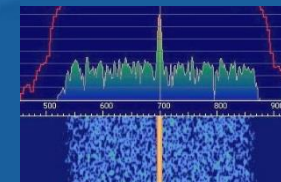


- Click on HDSDR Options [F7] button

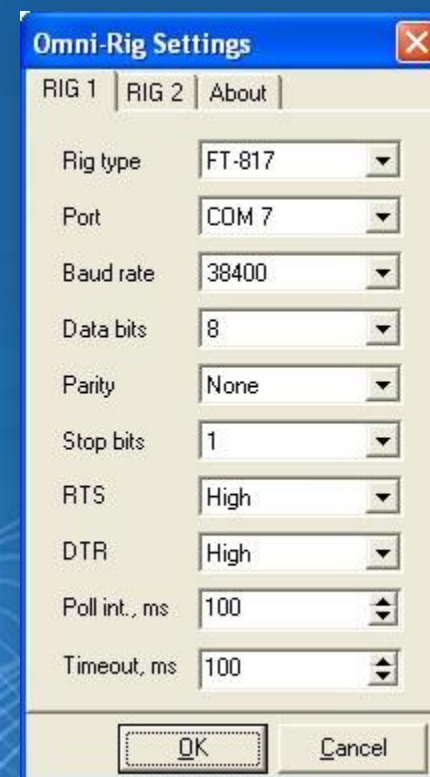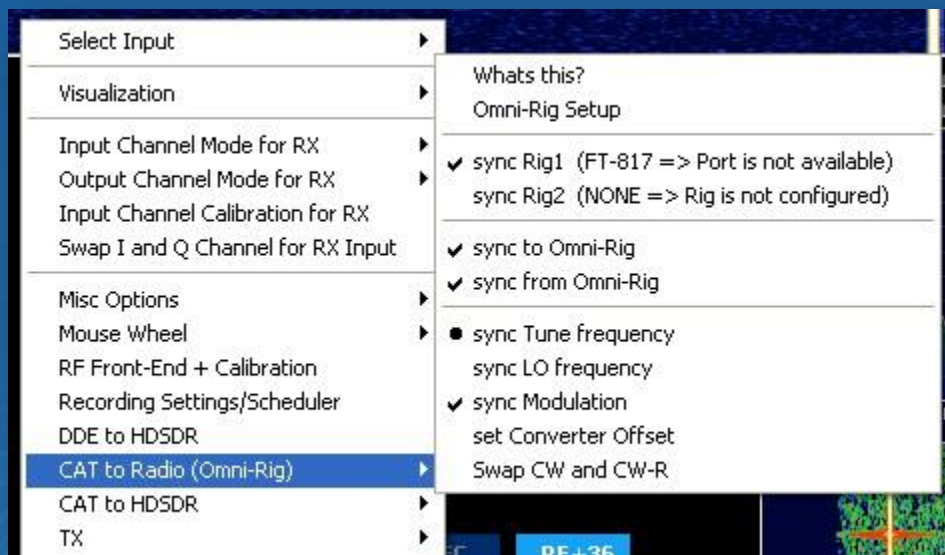

Also select 'Omni-Rig Setup' to bring up the 'Omni-Rig Settings' window and populate it with these values

# Omni-Rig Configuration

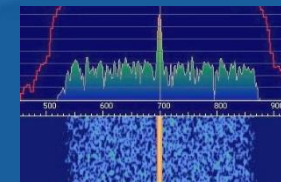


- This choice enables the Tx button within the HDSDR application





# Omni-Rig Configuration

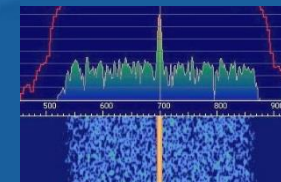

## And finally

- Plug in the CAT-62 cable
- Band change, tune, or Tx from either HDSDR or the FT-817. Either way settings follow you around like a puppy

**RF front-end frequency options & Calibration**

**SDR hardware coupling**

☐ SDR hardware connected to antenna (default)

☒ SDR on IF output, which is controlled by **Omni-Rig1**

**Sync Mode**

☒ Full sync in both directions

☐ Independent Tune in HDSDR

☐ Independent Tune, but sync on external change

IF-frequency:  [Hz] Global Offset:  [Hz]

Additional Offset per Mode in Hz

AM	FM	LSB	USB	CW_U	CW_L	DIG_U	DIG_L
0	0	0	0	0	0	0	0

☒ Mirror RF Spectrum in general

☐ Mirror RF Spectrum for Tune  $\geq$   kHz

☐ operate CW in lower sideband (LSB)

☐ Swap CW and CWR for Omni-Rig

☐ SDR hardware on Down/Up-Converter  
LO Frequency of Down/Up-Converter in Hz:

☐ SDR hardware in undersampling mode  
Sample rate of Analog-Digital Converter in Hz:

**LO frequency calibration**

Current Tune Frequency [Hz]:


Correct Tune Frequency [Hz]:

Frequency correction: **+0.00 ppm**

Hint: Tune to a station with known frequency as reference, e.g. a WWV or RWM time signal. Use ECSS mode with AFC to automatically tune the reference carrier exactly. Use highest possible frequency for best calibration results.

**Phase**

# Add a global offset

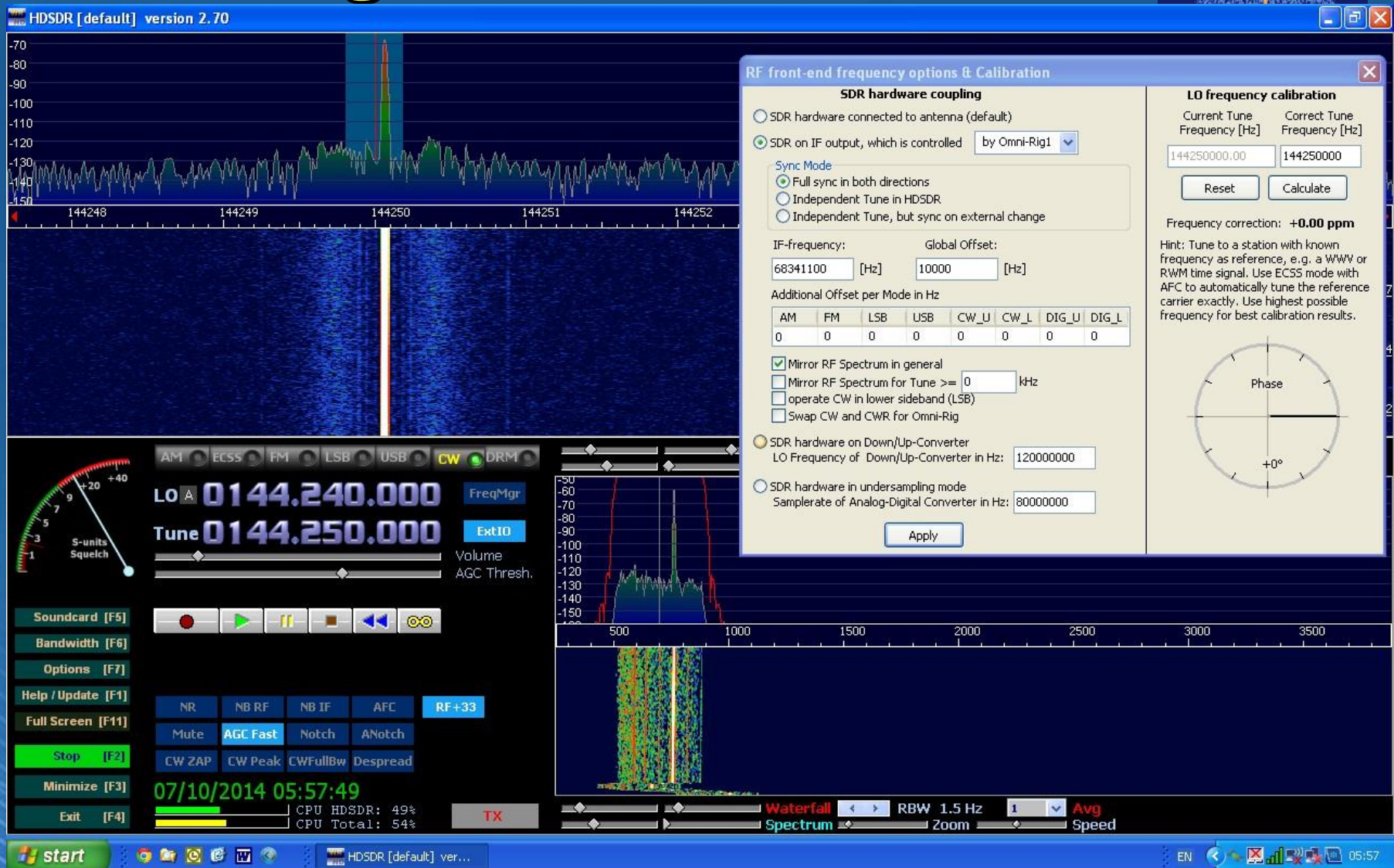

HDSDR [default] version 2.70

**RF front-end frequency options & Calibration**

**SDR hardware coupling**

- ☐ SDR hardware connected to antenna (default)
- ☒ SDR on IF output, which is controlled by **Omni-Rig1**

**Sync Mode**

- ☒ Full sync in both directions
- ☐ Independent Tune in HDSDR
- ☐ Independent Tune, but sync on external change

IF-frequency:  [Hz] Global Offset:  [Hz]

Additional Offset per Mode in Hz

AM	FM	LSB	USB	CW_U	CW_L	DIG_U	DIG_L
0	0	0	0	0	0	0	0

- ☒ Mirror RF Spectrum in general
- ☐ Mirror RF Spectrum for Tune >=  kHz
- ☐ operate CW in lower sideband (LSB)
- ☐ Swap CW and CWR for Omni-Rig

☐ SDR hardware on Down/Up-Converter  
LO Frequency of Down/Up-Converter in Hz:

☐ SDR hardware in undersampling mode  
Samplerate of Analog-Digital Converter in Hz:

**Apply**


**LO frequency calibration**

Current Tune Frequency [Hz]:  Correct Tune Frequency [Hz]:

**Reset** **Calculate**

Frequency correction: **+0.00 ppm**

Hint: Tune to a station with known frequency as reference, e.g. a WWV or RWM time signal. Use ECSS mode with AFC to automatically tune the reference carrier exactly. Use highest possible frequency for best calibration results.

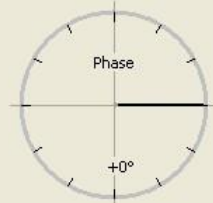Phase: 

**Soundcard [F5]** **Bandwidth [F6]** **Options [F7]** **Help / Update [F1]** **Full Screen [F11]** **Stop [F2]** **Minimize [F3]** **Exit [F4]**

**Lo A 0144.240.000** **Tune 0144.250.000** **FreqMgr** **ExtIO**

**Volume** **AGC Thresh.**

**NR** **NB RF** **NB IF** **AFC** **RF+33**

**Mute** **AGC Fast** **Notch** **ANotch**

**CW ZAP** **CW Peak** **CWFullBw** **Despread**

**07/10/2014 05:57:49**


**CPU HDSDR: 49%** **CPU Total: 54%** **TX**

**Waterfall** **Spectrum** **RBW 1.5 Hz** **1** **Avg** **Speed**

**start** **HDSDR [default] ver...** **EN** **05:57**



# Bibliography

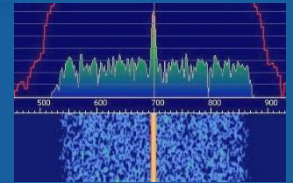

## Web

- W1GHZ panadapter - [http://www.w1ghz.org/small\\_proj/small\\_proj.htm](http://www.w1ghz.org/small_proj/small_proj.htm)
- G4HUP PAT <http://g4hup.com/PAT.htm>
- Elsie Filter design - <http://tonnesoftware.com/elsie.html>
- Linear Technology LT Spice  
<http://www.linear.com/designtools/software>
- NooElec DVB-T dongle  
<http://www.nooelec.com/store/sdr/sdr-receivers/nedr-mini-rtl2832-r820t.html>
- HDSDR <http://www.hdsdr.de/>
- Omni-Rig <http://www.dxatlas.com/OmniRig/>