

N.E.W.S. LETTER

The Publication of the North East Weak Signal Group

March, 2012

Volume 21

Issue 2

*****SAVE THE DATE*****

Combined Mid-Atlantic & Northeast VHF Conference Sat Oct 13

Marriott Courtyard Hotel, Bensalem, PA

Friday night table-top flea mart & Hospitality

Saturday: Conference presentations and Banquet dinner + door prizes

Sunday AM: Parking lot tailgate

\$35 Early Bird registration + \$35 for banquet

Full details to follow soon.

Check the Packrat website: <http://www.packratvhf.com/>

NEXT MEETING: March 17, 2012

BOARD MEETING: 11:30 AM at **Hibachi Grille and Supreme Buffet,**

14 Hazard Ave. Enfield, CT.. I-91 exit 47 Rt.190E. (860)-745-8808

(this is the Old Hometown Buffet location).

<http://www.yelp.com/biz/hibachi-grill-and-supreme-buffet-enfield>

GENERAL MEETING: STORRS LIBRARY - from 1 PM to approximately 3:45 PM

DON'T FORGET

The North East Weak Signal Group

2 Meter VHF and Above Net

Every Thursday at 8:30 PM local 144.250 MHz.

W1COT, WZ1V or K1PXE Net Control

MEMBERSHIP in the N.E.W.S Group is \$15 per year. Apply to Tom Williams, WA1MBA.

Email [tomw\(at\)wa1mba.org](mailto:tomw(at)wa1mba.org) You may download an application from our web page:

<http://www.newsvhf.com/>

The N.E.W.S. LETTER is the publication of the North East Weak Signal Group. Articles may be reprinted with proper credit given to the author and the N.E.W.S. LETTER. Send articles to Tom Filecco W1WSO, 163 Bemis St., Terryville, CT 06786, or preferably via email to w1wso@comcast.net.

Secretary's Report

NEWS Meeting 14 January 2012, Storrs Library, Longmeadow, MA

Vice-President N1JFU called meeting to order at 1327

Treasurer's Report

- 99 paid members, 14 permanent
- Balance \$3991
- Projected \$2500 excess

Correction to minutes - conference donation "up to \$1000"

OLD BUSINESS

- Joint conference Oct 1
 - Swap meet Friday nite
 - conference Saturday
 - flea market Sunday AM
- NEWS Website update in progress - easy to add
- Microwave bandplan K1MAP committee deadline 12/15

NEW BUSINESS

- January contest
- NEWSletter file is too large for dialup - reduce .pdf size
- Club insurance - look into cost
- Transatlantic beacon K1WHS - club should support
 - WA2AAU - should reply or record automatically
- N2GZ has resigned due to business committments
 - special election next meeting
 - Nomination WA2AAU others at election
 - term thru July 2013
 - Secretary to send email

ANNOUNCEMENTS

- Canadian 2meter net 830pm Tuesday 144-240
- KA1ZE 0800AM 144.205 FN01 ON4KST chat page
- ham in Azores has site for 2 meter beacon

MOTION by WA1MBA to reimburse W1FKF \$9 for pointer - UNANIMOUS

Motion by WA1MBA to donate \$100 to Storrs Library - UNANIMOUS


Meeting Adjourned 1425

- Paul, W1GHZ

Treasurer's Report

The treasury remains healthy. Per our last meeting, we have sent a \$100 gift to the Storrs Library. Our membership remains strong at normal levels for this time of year. I expect to be in Florida, watching the Red Sox in Spring Training during the March meeting. I may be able to deliver my spreadsheet to the meeting. In any case, enjoy. I will see you in May.

- Tom WA1MBA

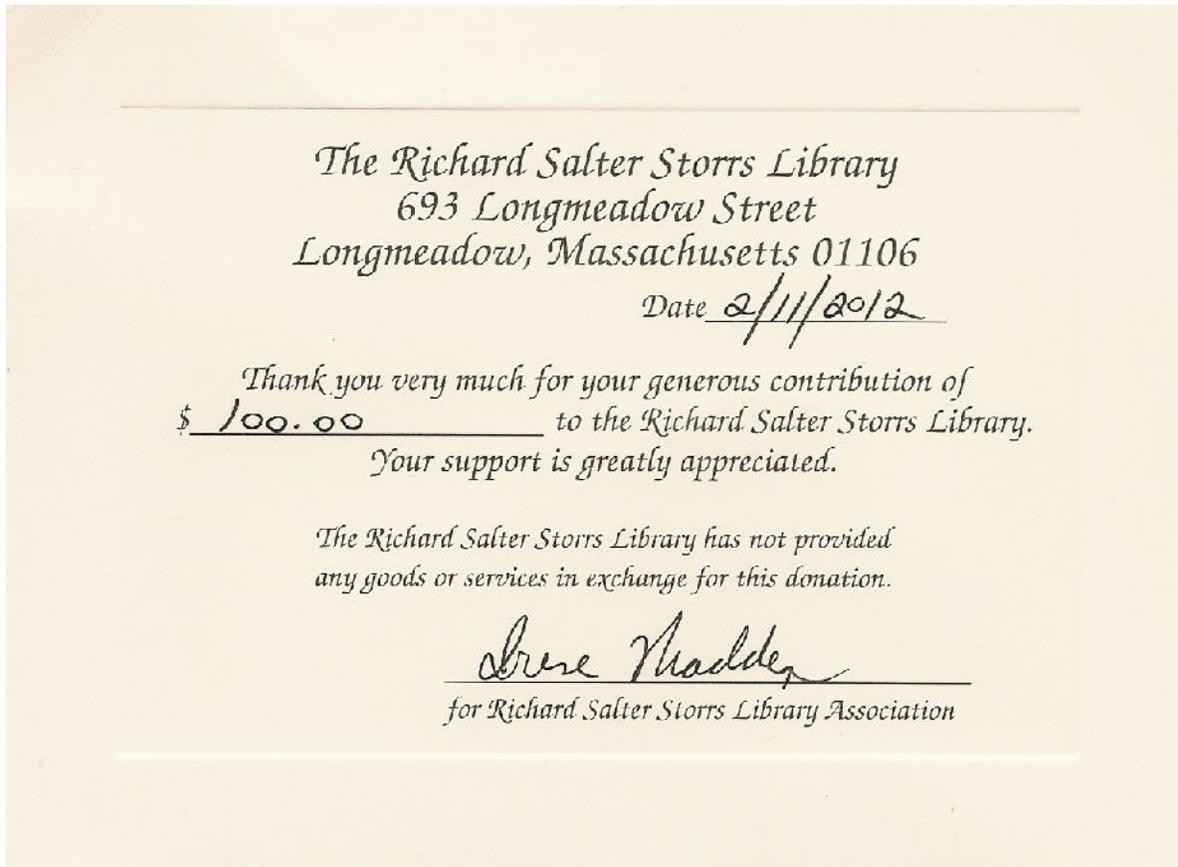

IMPROVING THE LARCAN AMPLIFIER AT 50.0 MHz


By David Olean K1WHS


I purchased one of the LO-HI Larcán television amplifiers from the MMRA group last year and have finally gotten around to actually implementing it into my station. As advertised, these amplifiers will provide 300 watts on the FM part of six meters when not converted, and will make 600 watts output in CW and 1000 watts PEP in SSB if component changes are made to convert a LO-HI amp down to a LO-LO amp. My interest was in using the amplifier at 50.1 MHz for SSB and CW service, not FM, and the additional excursion to the bottom of the band resulted in poor efficiency and lower

gain. Surely there must be a way to squeeze a few more watts out of the circuit.

My first attempt involved tweaking an individual MRF151G stage on the amplifier chassis for better performance at 50.0 MHz. The input side seemed to be pretty optimum and no improvements were noted, but I was able to increase the performance by modifying the output circuit. I experimented with changing values of C-14 and C-16. C-13 seemed OK as is, but I was able to improve the gain by increasing the value of C-16 from the 51 pf specified by Larcan, to 75 pf. You could piggy back a 24 pf capacitor there, or just install a single 75 pf capacitor in place of the original 51 pf. I also found that increasing C-14 and C-15 from the Larcan value of 180 pf to 225 pf increased the performance as well.

I next attacked the output combiner. My changes to each individual amplifier had improved things, but there was still a huge discrepancy between 50.0 MHz and higher frequencies. Max power was still up beyond 70 MHz. I had only marginally improved the performance. Don, W1FKF had also converted a Larcan unit to 50 MHz SSB previously, and had complained about poor efficiency there. He was seeing efficiency values in the order of 24%. I thought that the problem had to lie in the output combiner as well as the output section of the amplifier. I disconnected all of the MRF151G stages and substituted small 50 ohm resistors at the amplifier output. Then I connected a network analyzer there on the output connector. My feeling was that I should see 50 ohms if everything was working properly. I was greeted by a very poor match at 50 MHz with a return loss of about 7 dB, or almost 3:1! Instead of the normal 6 dB of coupling loss, I was seeing 3.5 dB on one port. That meant another port would have had almost 9 dB! Clearly the combiner was not working well. I then started experimenting with the combiner cap values, and ended up changing the values of C-4 & C-5 and also C-1 & C-8. C-4 & C-5 were originally 47 pf and I increased that to about 86 pf by adding a 39 pf capacitor piggyback style on each one. C-1 & C-8 had an added 12 pf for a total of about 27 pf there. Those changes altered the output combiner more to my liking.

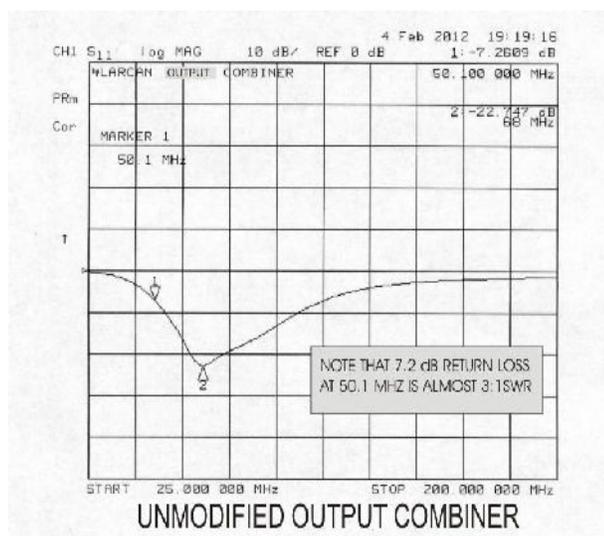

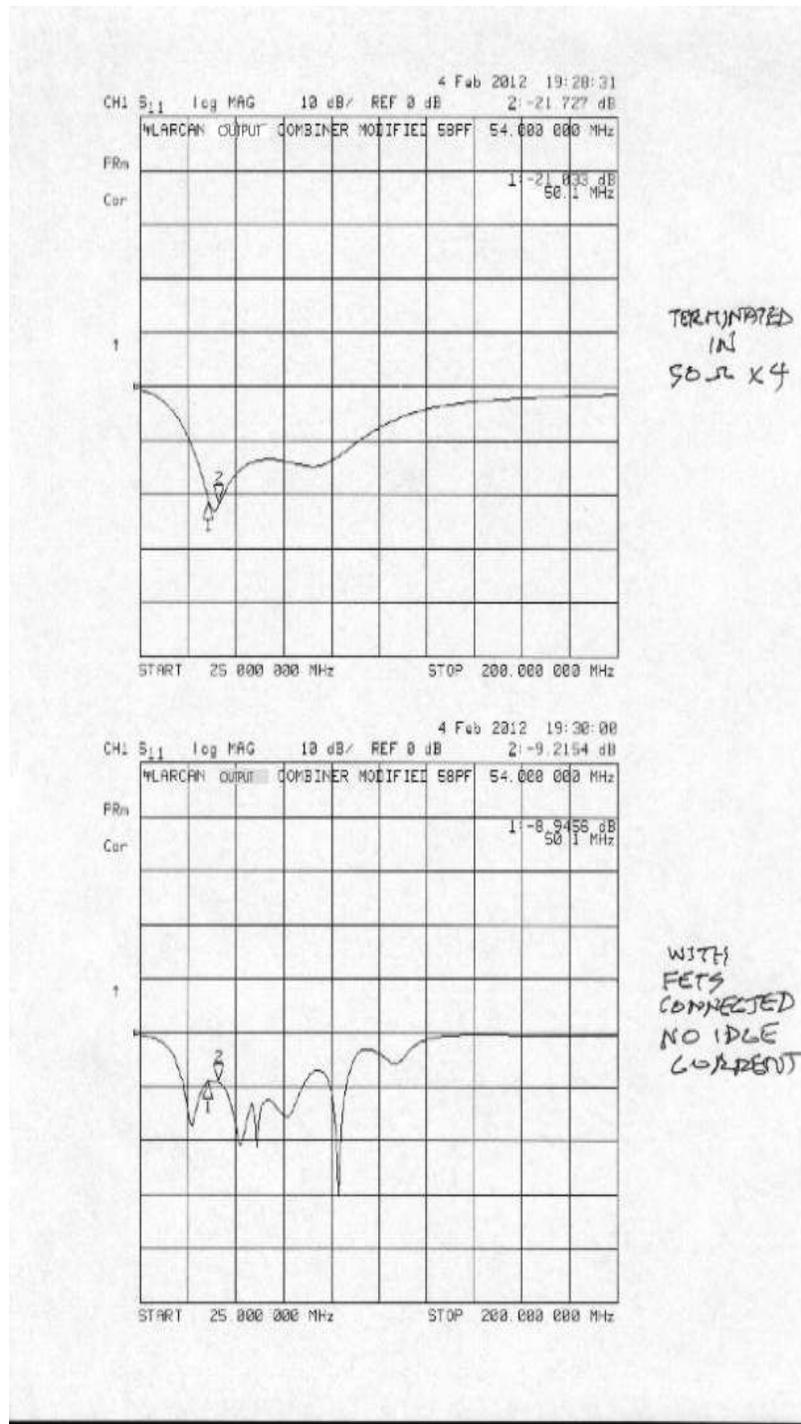


This is the modified output combiner with better than 20 dB return loss between 50 and 54 MHz.

The lower plot is the combiner terminated in the FET amplifiers rather than 50 ohm resistors.

I could see that the input splitter was very similar in construction to the output combiner, so I figured it needed help as well. I tried the same trick on the input by putting 50 ohm resistors at each amplifier

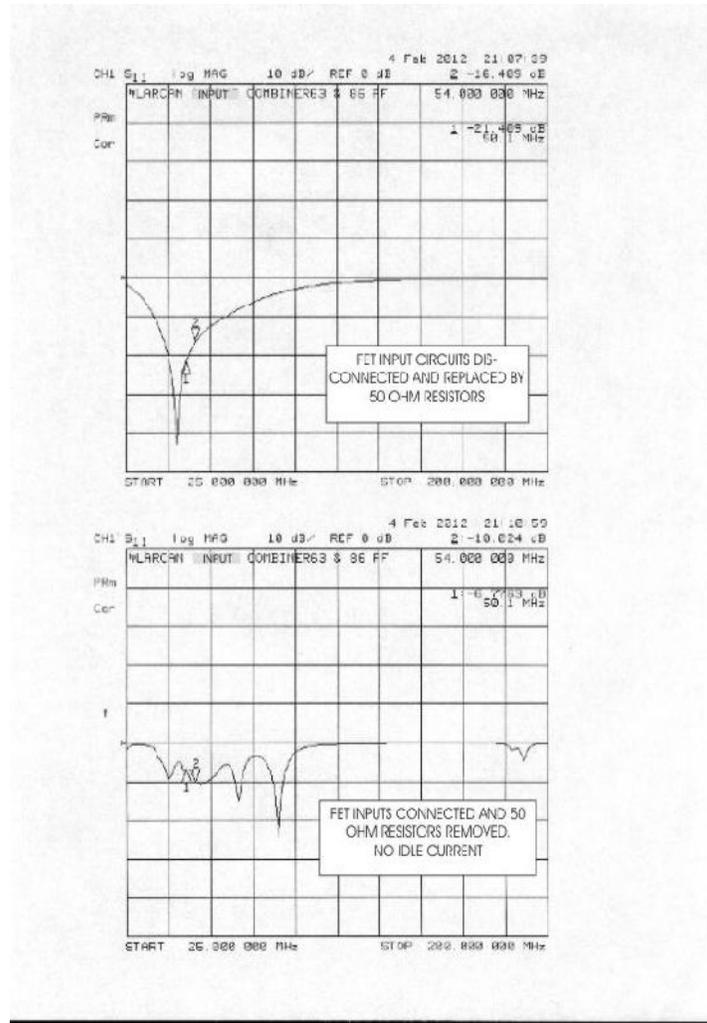input and measuring the input return loss to the splitter. C-5 & C-6 needed more capacitance and I piggybacked another 30 pf across the 39 pf ones for a total of 68 or 69 pf. I left C-3 & C-4 alone. Changes there did not have much effect. I felt a little better knowing that the amplifiers were now running into a more reasonable load.



Converted INPUT splitter

I tried firing up the amplifier and driving it with a laboratory signal generator and instrument amplifier. With 4.0 watts of drive I had the following results:

FREQUENCY	VOLTS DC	AMPS	POWER OUT	EFFICIENCY
50	51	30	540	35.30%
52	51	31	580	36.70%
54	51	32	630	39.20%

I tried running the converted amplifier at 70 MHz at full power, but was greeted by a blue

flash from one of the FETs and a blown fuse. Scratch one \$110 LDMOS! (It failed as an open circuit) With the changes I made to the output stage, the maximum RF output of the amplifier alone is reached at about 60 MHz. I guess full power at 70 MHz into the modified output combiner was a bad idea. Note to self: Operate only between 50 and 54 MHz after making these changes!! I ran the drive up at 54 MHz to a bit over 5 watts to obtain 900 watts of carrier. Current drain was 38 amps for an efficiency of 46.94%. There is one caveat. I used a 1000 watt 100-250 MHz Bird slug which is not rated for 50 MHz. I suspect the power accuracy is pretty close though, as it is a high power element with light coupling. (You would think that K1WHS would have his act together and possess a 1000 watt Bird element for 50 MHz. If you did think that, you would be WRONG!) This is drastically better than the unmodified LO-LO module will do, so I feel that my efforts were effective and make a good amplifier even better. I did not have a peak reading watt meter in my shop, but a scope does show PEP values significantly higher than the CW carrier levels when SSB is employed.

The input combiner still favors higher frequencies and you can see the input power to the FET rising as you raise the frequency. I reasoned that reworking the etched lines was not worth the effort in an attempt to correct this. After all, you need only increase the drive a bit to overcome the roll off in the input combiner. Gain ranges from 21.4 dB at 50 MHz to over 22 dB at 54 MHz.

So here are the changes required for better performance at 50-54 MHz:

INPUT SPLITTER:

C-5, C-6 39 pf to 68 pf ATC100B (You could also use a silver mica cap as the drive level is low)

AMPLIFIER OUTPUT :

C-16 51 pf to 75 pf ATC100B chip cap.

C-14, C-15 180 pf to 230 pf ATC100B chip cap.

COMBINER OUTPUT:

C-4, C-5 39 pf to 86 pf ATC100B chip cap.

C-2, C-3 24 pf to 68 pf ATC100B chip cap.

C-1, C-8 15 pf to 27 pf ATC100B chip cap.

The capacitor reference numbers are the ones specified in the Larcan schematic diagrams as posted on the MMRA website. (See <http://www.mmra.org/larcan/>) This website has a wealth of data on the Larcan amplifiers.


I am sure there is more that can be squeezed out of this unit. In my testing, I was disturbed to see that the isolation between stages, provided by the output combiner was not very good at 50 MHz. I originally tried running a single amplifier stage with the other three terminated in low power 50 ohm

resistors, in an effort to match into the combiner. There was too much power being absorbed in the resistors. I did not measure the isolation, but I think that it is much less than the typical 20 dB obtained with Wilkinson dividers. As a result, I abandoned that plan of matching into the terminated combiner in favor of my “bucket of worms “ approach! What I ended up with is still quite nice and well worth the effort. This amplifier will make a nice addition to the shack. I can drive this amplifier easily with rigs such as the FT-817 at 5 watts, or my low power (8 watt) Elecraft K3 on 50 MHz.


As a side note, I obtained a single MRF151G Larcan PC board (¼ of the full amplifier) and built that up on a new heat sink. This single stage has no input and output combiners. After performing the amplifier mods listed above, I saw pretty constant output from 50 MHz up to about 68 MHz. The FET really took off with drive and I had no trouble getting 300 watts out of a single transistor. In fact I drove it to 400 watts CW output with less than 5 watts of drive. DC Current at 50 volts was about 11.5 amps! This is over the rating for the MRF151G. You should keep the current under 9 amps at the 50 volt level so as not to exceed the safe area of operation. At 300 watts it runs beautifully. The efficiency is way up there too at 68% at 400 watts. I noticed that my Larcan amplifier came from the TV station with 7 amp fuses for each FET. The Larcan schematic calls for 5 amp fuses. It would be a good idea to err on the low side with your fuse selection. Incidentally, all of my testing was done with the Larcan recommended 0.50 amps idling current per FET.

In summary, I believe that most of the added gain and increased efficiency is obtained by cleaning up both combining networks on the inputs and the outputs of this amplifier. Some added output amplifier board tweaks (C-14, 15, and 16) over those specified by Larcan for the LO TV channels (2,3 & 4) increased the gain a bit more. This amplifier is now ready to be buttoned up and installed!

CU on six this summer!

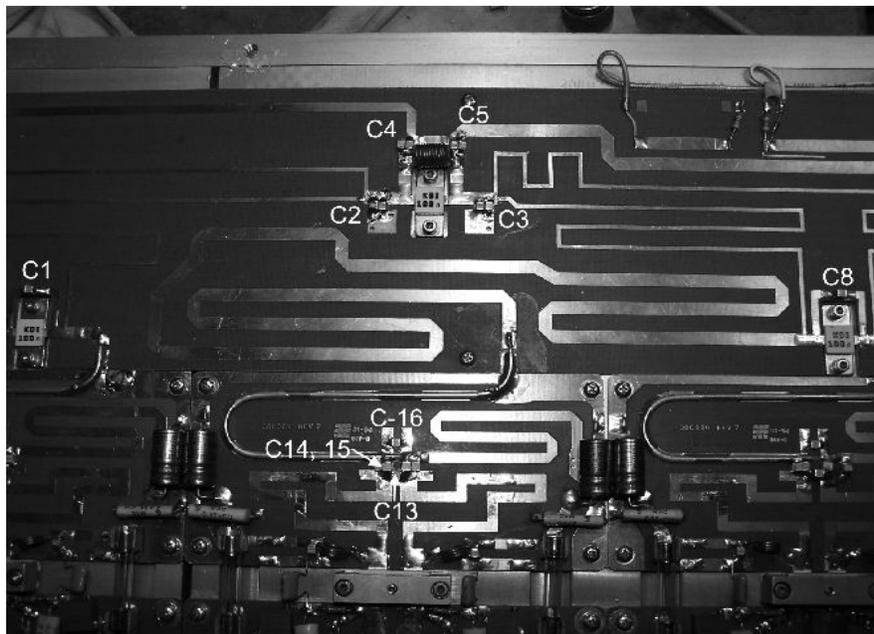

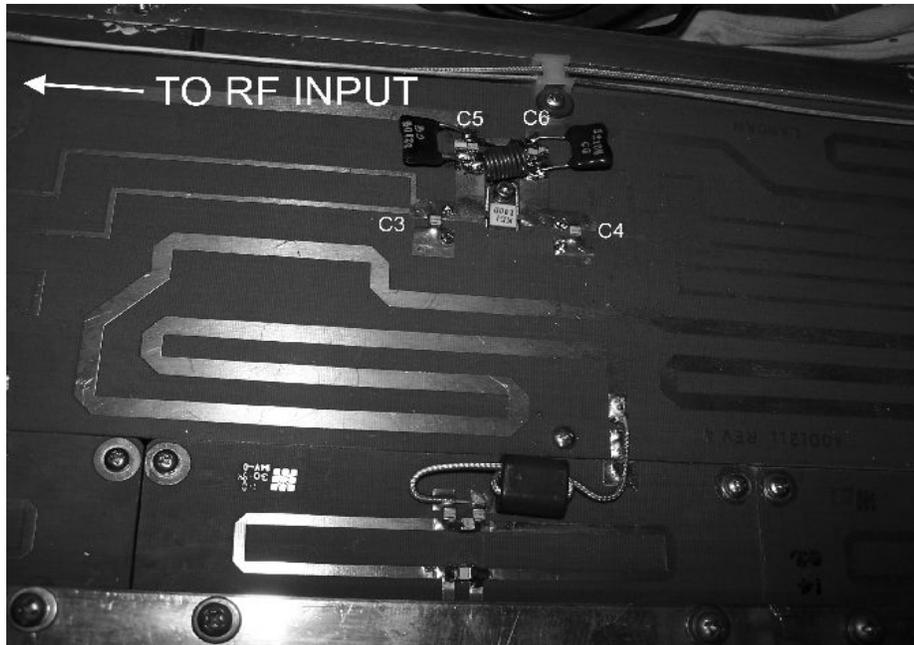Photograph of the capacitor locations used in the modification of the output combiner and FET output stages. C13, 14, 15, and 16 are all changed in each of the four power modules. The other capacitors are all used in the power combiner as shown.



Input splitter photograph, showing the first Wilkinson divider area. C5 and C6 are changed. C3 & C4 are not altered and are shown for reference only. You can see some 5 pf silver mica caps. I took this picture while “fine tuning” the input. Silver micas are OK here as power levels are low.

UPDATE: Since I provided the preliminary info for the newsletter, I have hooked up some accurate power measuring gear and am seeing 1200 watts peak output with 7.3 watts drive at 50.1 MHz and I get more gain at 54 MHz with 1375 watts peak output with about 7.6 watts peak. These numbers correspond to 21.9 dB gain at 50 and 22.9 dB at 54 MHz. Keeping the drive under 8 watts is a good idea as you can overdrive the FETs. I would not want to drive the FETs over 40 amps total. It is easy to run the current up to over 50 or 60 amps. You get lots of RF, but the FETs are out of their safe area, and you know what that means!!

A Modest Power Amplifier for Cheap and Simple Microwave Transverters

Paul Wade W1GHZ ©2012 - w1ghz@arrl.net

My Cheap and Simple Transverters for the Rover typically produce only a few milliwatts, enough for many rover contacts. Higher power amplifiers are available, but not always cheap, and often requiring significant DC power. If we could provide a bit more power without significant difficulty, expense, or DC power expenditure, it might enable more DX for the rover.

A number of devices might provide this power, but many of them would require tuning or more complicated biasing. We would prefer a simple MMIC like the other devices in the transverters, sticking with our design philosophy – gain is cheap. Minicircuits (<http://www.minicircuits.com/>) offers several devices in a three e-lead package with a ground pad capable of 100 milliwatts or so, all at low cost.

I chose the GVA-84, which requires only a 5-volt power and no bias resistor. The bias is supplied through an RF choke.

I had room on a prototype Miniboard from Express PCB (<http://www.expresspcb.com/>) for a small circuit with SMA connectors. The completed board is shown in Figure 1. It's simple enough that no schematic is necessary – just blocking caps, a chip inductor (30 nH) for the RF choke, and decoupling caps. None of the component values is critical. There are several plated-thru holes under the ground pad of the MMIC which provide a thermal path to the ground plane on the far side as well as good grounding. The board needn't be this fancy; one could be cut with an X-Acto knife or Dremel tool, and the RF choke could be a few turns of fine wire.


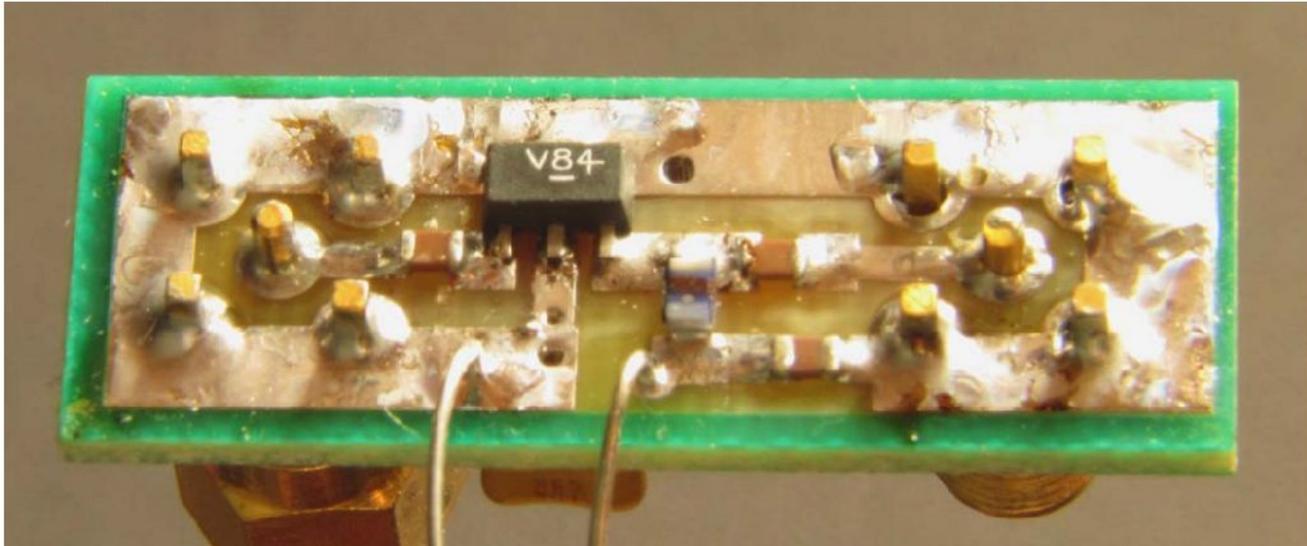


Figure 1- GVA-84 Microwave Amplifier

This simple amplifier worked as expected on all the lower microwave bands. The table below shows the output power with 0 dBm input as well as the saturated output power.

Frequency	Pout linear	Pout max
902 MHz	+19 dBm for 0 dBm in	>+21 dBm
1296	+19 dBm for 0 dBm in	+22.8 dBm
2304	+19 dBm for 3 dBm in	+20.5 dBm
3456	+15 dBm for 3 dBm in	+18.8 dBm
5760	+9 dBm for 3 dBm in	+13 dBm

The gain rolls off with at higher frequencies, but the amplifier can provide a modest power increase for all the simple transverters. A similar device, the GALI-84, should provide similar performance, but requires a bias resistor. This allows operation from higher voltages. The resistor values are relatively small, so an RF choke is still needed to prevent the bias resistor from absorbing most of the RF power. You might notice that the transverter boards have a ground pattern for the final transmit stage, which would also fit the three-lead package – I've intended to try one, but haven't gotten to it yet.

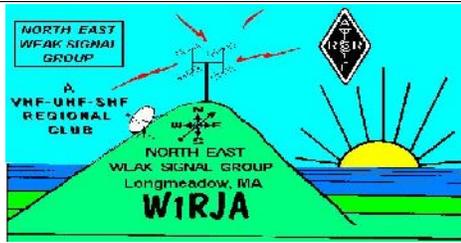

Name: _____ Call sign: _____ Grid: _____

Street: _____

City: _____ State: _____ Zip: _____

Phone (home) _____ - _____ - _____ Optional (work) _____ - _____ - _____

Email _____

ARRL member? Y N Electronic Newsletter Delivery? Y N

Operational Bands (circle) 50 MHz 144 MHz 222 MHz 432 MHz 903 MHz

1.2 GHz 2.3 GHz 3.4 GHz 5.6 GHz 10 GHz 24 GHz 47 GHz

76 GHz Light Other (list)

The North East Weak Signal [N.E.W.S.]Group is being established to form a camaraderie among fellow VHF-UHF-SHF enthusiasts, and support a convenient means to exchange technical information. We currently have 6 meetings per year, held at a centrally located facility, and provide a "NEWSLETTER" that is distributed 2 weeks prior to each meeting. Any contributions to this publication are appreciated and can be sent to: Tom Filecco, W1WSO via email – w1wso@comcast.net. Dues are \$15/year. Remember, this group is formed by VHF'ers for VHF'ers.

Mail to:

North East Weak Signal Group
c/o WA1MBA Tom Williams PO Box 28
Shutesbury, MA 01072

DIRECTIVE SYSTEMS

Now Featuring K1FO 17' Boom Yagis for 144, 222 & 432 MHz!



Dave Olean, K1WHS RR1, Box 282, Lebanon, ME 04027 Phone 207-658-7758

<http://www.directivesystems.com/antenna.htm>

FlexRadio Systems®
 Software Defined Radios

<http://www.flex-radio.com/>





SSB Electronic USA
 manufactures and distributes
 HF, VHF, UHF and SHF
 equipment covering 10 MHz to
 47 GHz
 124 Cherrywood Drive,
 Mountaintop, PA 18707
 USA
 Phone 570-868-5643 FAX
 570-868-6917

<http://www.ssbusa.com/ham.html>



**Chassis Kits &
 Custom Enclosures**
Charles Byers K3IWK
www.k3iwk.net
 5120 Harmony Grove Road
 Dover, PA 17315
 Phone/Fax (717) 292-4901 k3iwk@flash.net
 Phone between 6:00 - 9:30 P.M. EST

Home Products Support Buy Contact Us

West Mountain Radio
 1020 Spring City Drive
 Waukesha, WI 53186
 Phone: 1-262-522-6503
 Fax: 262-522-6504
 Email:
info@westmountainradio.com

Products for DC Power, Amateur Radio and R/C Hobbies

- Robustness and reliability required by public safety agencies and emergency response teams.
- Precision battery analysis suitable for battery pack manufacturers, factories managers and aircraft owners.
- Low pricing attention to amateur radio and R/C hobbyists.

<http://www.westmountainradio.com/index.php>

--	--	--	--	--	--

W2PED
 Specializing in 24GHz
 and above
paul@w2ped.com
<http://w2ped.com/>

LUNAR-LINK SYSTEMS
 818 Emerson Hill Trail Medford, CT 06443-1004 (800) 421-9377

<http://home.cshore.com/lunarlink/>

LeCroy

John D. Seney W4IV
 Sales Engineer
john.seney@lecroy.com
 700 Chestnut Ridge Road
 Chestnut Ridge, NY 10977-6499
 Tel: (800)553-2769 Local: (603)627-6303
 Fax (845)578-5985 www.lecroy.com

DOWN EAST MICROWAVE
 LIVE OAK, FLORIDA

VHF/UHF/SHF EQUIPMENT AND PARTS 50 to 10,368 MHz

Microwave Loop Yagis, VHF/UHF Yagis	No-Tune Linear Transverters
Linear Power Amps	Low Noise Preamps
Coax Relays	Coax Cable Connectors
Chip Components	MMIC's, Transistors
RF Modules	Crystals

Steve Kostro, N2CEI 19519 78th Ter. Live Oak, FL 32060 Tel. 386-364-5529

<http://www.downeastmicrowave.com>